

## ECE 6130 Wilkinson Power Divider

Text Section 7.3


How do you design a Wilkinson Power Divider?  
See for example Chapter 7 Problems 9,10

### Wilkinson Power Divider:


Matched at all ports

Complete isolation between output ports

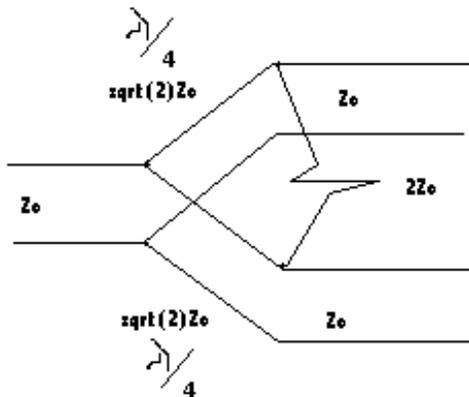Lossless when output ports are matched. Lossy when they are not (only reflected power is lost).



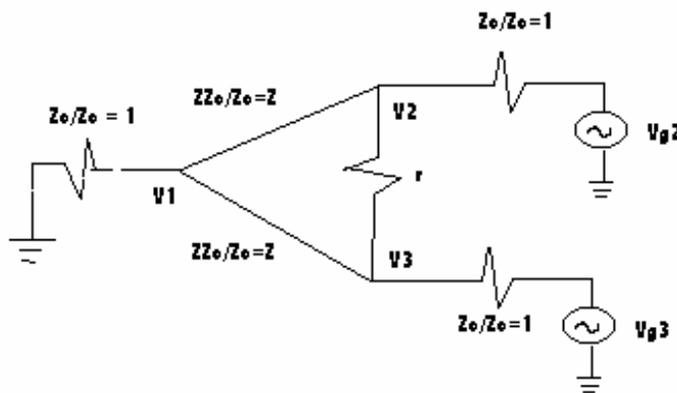
Use normalized impedance values (normalized to  $Z_0$ ), and place sources on output ports:



Split down the center, so that the output ports will act on the circuit separately. This will ensure complete isolation later.



### Bisection of Circuit for Odd Mode:

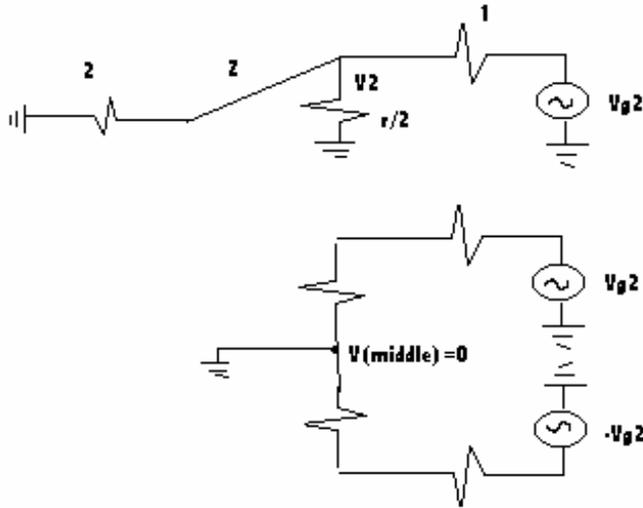

### Even Mode:

We want to find  $V_1$ , so that we can find the S-parameters:

First find impedance looking into port 2 (where  $r$  connects to line)

(matching section looks like a quarter-wave section)

$$Z = \sqrt{(Z_{in}^e)(2)}; \quad \text{So } Z_{in}^e = Z^2 / 2$$

Voltage generator defined as  $2V$ .

For matched conditions  $Z = \sqrt{2}$  and  $Z_{in} = 1$

$V_2 = (2V) (1 / (1+1)) = V$  (voltage divider over  $Z_{in}$  and matched line)

The  $r/2$  resistor has no current flowing because of OC, so is superfluous.

Find  $V_1$ :

- Define  $x=0$  at port 1 (junction),  $x = -\lambda / 4$  at port 2
- Then  $V(x) = V^+ (e^{-j\beta x} + \Gamma e^{j\beta x})$
- $V_2 = V(-\lambda / 4) = j V^+ (1 - \Gamma) = V$  ;  $V^+ = jV / (\Gamma - 1)$
- $V_1 = V(0) = V^+ (1 + \Gamma) = jV^+ (\Gamma + 1) / (\Gamma - 1)$
- At port 1, looking into resistor of value 2:  $\Gamma = (2 - \sqrt{2}) / (2 + \sqrt{2})$  and  $V_1 = -jV / \sqrt{2}$

### Odd Mode:

To match port 2 (looking into source)  $r = 2$

$\lambda / 4$  transmission line shorted at end looks like an open circuit. (think of Smith Chart)

Looking into port 2 (toward line), we see OC and  $r / 2 = 1$  in parallel, so port 2 is matched.

$V_2 = 2V ( 1 / (1+1) ) = V$  (voltage divider over 1 and  $r / 2 = 1$ ) resistors  
 $V_1 = 0$  (shorted)  
All odd-mode power is lost in resistor  $r / 2$  .

**Find  $Z_{in}$**  for Wilkinson Divider (looking into port 1 toward the two quarter-wave transformers -- either mode)

The transformers match the input , so the  $Z_{in} = 1$  is matched.

**Superposition: Find the S-parameters:**

$$S_{11} = (Z_o - Z_{in}) / (Z_o + Z_{in}) = 0$$

$$S_{22} = S_{33} = 0 \text{ (both ports 2 and 3 are matched for both even and odd modes)}$$

$$S_{12} = S_{21} = (V_1^e + V_1^o) / (V_2^e + V_2^o) = -j / \sqrt{2} \text{ (and symmetry due to reciprocity)}$$

$$S_{13} = S_{31} = -j / \sqrt{2} \text{ (symmetry of ports 2 and 3)}$$

$$S_{23} = S_{32} = 0 \text{ (due to short or open at bisection)}$$