

ECE 5180/6180 Microwave Filter Design

Lectures:

- Lumped element filters (also applies to low frequency filters)
- Stub Filters
- Stepped Impedance Filters
- Coupled Line Filters

Lumped Element Filters

Text Section 8.3

Portfolio Question: How do you design a lumped element filter using the Insertion Loss Method

Power Loss Ratio

$$P_{LR} = \frac{\text{Power Available from Source}}{\text{Power Delivered to Load}} = \frac{P_{inc}}{P_{load}}$$

Insertion Loss

$$IL = 10 \log P_{LR}$$

2-port network:



$$\begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$

$$P_{source} = \frac{(V_1^+)^2}{Z_{in}} \quad P_{load} = \frac{(V_2^-)^2}{Z_L}$$

For Matched System $Z_{in} = Z_L = Z_o$

Then

$$\frac{P_{source}}{P_{load}} = \left(\frac{V_1^+}{V_2^-} \right)^2 = \frac{1}{|S_{21}|^2} = \frac{1}{|S_{12}|^2}$$

(For Reciprocal System $S_{21} = S_{12}$)

$$P_{LR} = \frac{1}{1 - |\Gamma_{in}|^2} = \frac{1}{1 - |\Gamma_{in}(\omega)|^2}$$

Filter Design by insertion loss method controls $\Gamma(\omega)$ to control passband and stopband of filter.

Filter parameters:

- Passband -- frequencies that are passed by filter
- Stopband -- frequencies that are rejected
- Insertion loss -- how much power is transferred to load in passband
- Attenuation -- how much power is rejected (not transferred to the load) in the stopband

Cutoff rate or attenuation rate -- how quickly the filter transitions from pass-to-stop or stop-to-passbands
 Phase response -- Linear phase response in the passband means that signal will not be distorted.

Classes of Filters:

Determined by Γ .

We have not proven this yet, but a useful mathematical proof (section 4.1) shows that $|\Gamma(\omega)|^2$ is an even function of ω . So $|\Gamma(\omega)|^2$ can be written as a polynomial in ω^2 .

$$|\Gamma(\omega)|^2 = \frac{M(\omega^2)}{M(\omega^2) + N(\omega^2)}$$

$$P_{LR} = 1 + \frac{M(\omega^2)}{N(\omega^2)}$$

The class of filter is controlled by the type of polynomial used.

Polynomials M and N can be

- Binomial (Butterworth) -- Maximally Flat
- Chebyshev -- Equal Ripple
- Elliptic -- Specified Minimum Stopband Attenuation (faster cutoff)
- Linear Phase

Binomial / Butterworth / Maximally Flat

Low Pass Filter Design:

$$P_{LR} = 1 + k^2 \left(\frac{\omega}{\omega_c} \right)^{2N}$$

N = Filter Order

ω = frequency of interest

ω_c = cutoff frequency

At ω_c , $P_{LR} = 1+k^2$

If the -3dB point is defined to be the cutoff point (common), $k=1$

For $\omega \gg \omega_c$ then $P_{LR} \approx k^2 (\omega/\omega_c)^{2N}$ which means Insertion Loss increases at a rate of 20N dB / decade.

(This allows us to increase the steepness of the cutoff by adding more sections.)

Chebyshev / Equal Ripple Filters

$$P_{LR} = 1 + k^2 T_N^2 \left(\frac{\omega}{\omega_c} \right)$$

Where T_N are Chebyshev polynomials

Ripples are equal-in-size = $1+k^2$

Cutoff Rate is 20N dB/decade, same as binomial.

Insertion loss in the stopband is $(2^{2N})/4$ greater than binomial.

Elliptic and Linear Phase Filters

Other options, see textbook.

Filter Design Method

1. Design a LP filter for normalized Z, ω
2. Scale Z.

3. Convert from LP to HP or BP as desired.
4. Convert from lumped to distributed elements as desired.

1. Binomial Design of LP Filter for Normalized Z, ω

- a. Determine how many elements are needed (N)

Find ω/ω_c and look at the figure for attenuation in the stopband (Fig.8.26, p.450)

Example: How many elements are required to design a maximally-flat filter with a cutoff frequency of 2 GHz if the filter must provide 20 dB of attenuation at 4 GHz?

For this case, $|\omega/\omega_c|-1 = |4/2|-1 = 1.0$ (bottom axis). Find N line on filter that is ABOVE the desired attenuation. $N=4$.


- b. Find resistance or conductance values from Table 8.3

Look at $N=3$.

$g_1 = 1.0$; $g_2 = 2.0$; $g_3 = 1.0$; $g_4 = 1.0$

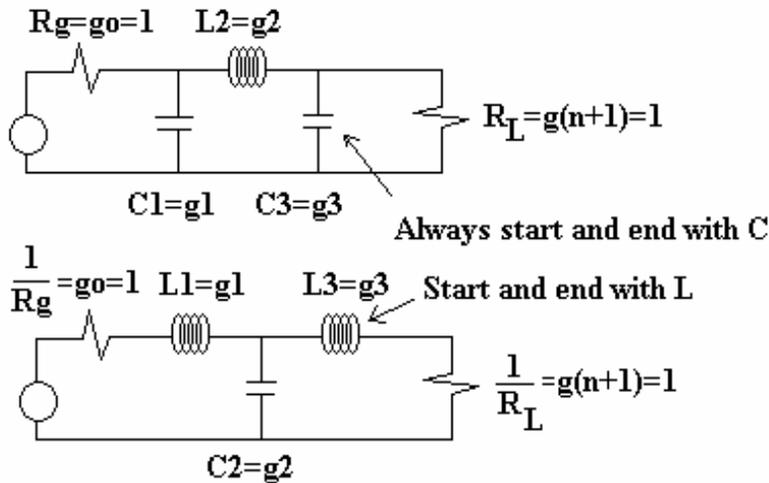- c. Choose LP Filter Prototype

Why choose one over the other? Available components. (Responses of both are identical.)



Notes:

- 1) R_g and R_L must be REAL. What if they aren't? (Add a length of line, resonate, or absorb imaginary part.)
- 2) The designs in our book always have $R_g = R_L$. What if they are not equal? There are other tables... see handout. This is effectively matching and filtering simultaneously.
- 3) Design so far has considered normalized impedances $R_g = R_L = 1$ and normalized frequency ($\omega_c = 1$) ... Use impedance and frequency scaling if they aren't 1.

1. Chebyshev (Equal Ripple) Design of LP Filter for Normalized Z, ω

Same steps as for binomial. There are only a few differences....

- (a) Determine number of elements (N). This will always be less than or equal to binomial. Use Figure 8.27, with choice of size of ripple.
- (b) Use table 8.4, with same choice of ripple as used in part a.
- (c) Same as binomial.

2. Impedance and Frequency Scaling (normalization)

To build the same filter for $Z_0 = R_g = R_L$ and a given cutoff frequency ω_c
 Use the same filter prototypes but scale the values:

(a) *Top filter prototype*

$$R_g = (Z_0)(g_0) =$$

$$C_1 = g_1 / (Z_0 \omega_c)$$

$$L_2 = (Z_0)(g_2) / \omega_c$$

$$C_3 = g_3 / (Z_0 \omega_c)$$

$$R_L = (Z_0)(g_4)$$

(b) *Bottom filter prototype*

$$R_g = 1 / (Z_0 g_0)$$

$$L_1 = (Z_0)(g_1) / \omega_c$$

$$C_2 = g_2 / (Z_0 \omega_c)$$

$$L_3 = (Z_0)(g_3) / \omega_c$$

$$R_L = 1 / (Z_0 g_4)$$

Binomial and Chebyshev are the same here, except for one difference:

R_L for binomial is always matched.

R_L for odd-order Chebyshev filters is NOT matched. Use a quarter-wave transformer to match.



Example:

For 0.5 dB ripple and $N=3$, $g_3=1.9841$. For top prototype, $R_L=1.9841 Z_0$, which is not matched.

Quarterwave transformer would have $Z_q = (\sqrt{1.9841}) Z_0$

3. Convert from LP to HP

High Pass Configurations

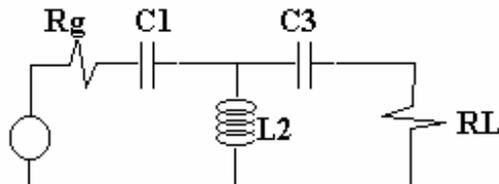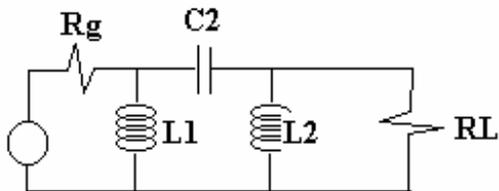

For both prototypes:

$$C_k = 1 / (Z_0 \omega_c g_k)$$

$$L_k = Z_0 / (\omega_c g_k)$$

For top prototype:

$$R_g = Z_0 g_0$$

$$R_L = Z_0 / g_{n+1}$$

For bottom prototype:

$$R_g = 1 / (Z_0 g_0)$$

$$R_L = 1 / (Z_0 g_{n+1})$$

3. Convert from LP to Bandpass or Bandstop

Normalized bandwidth

$$\Delta = \frac{\omega_2 - \omega_1}{\omega_o}$$

ω_1 = lower limit

ω_2 = upper limit

$\omega_o = \sqrt{\omega_1 \omega_2}$

See Table 8.6 p. 461 for conversions.

To use for unnormalized filters:

$L \rightarrow L Z_o$

$C \rightarrow C / Z_o$