

Mini-MIPS

From Weste/Harris
CMOS VLSI Design

Based on MIPS

- ◆ In fact, it's based on the multi-cycle MIPS from Patterson and Hennessy
 - Your CS/EE 3810 book...
- ◆ 8-bit version
 - 8-bit data and address
 - 32-bit instruction format
 - 8 registers numbered \$0-\$7
 - \$0 is hardwired to the value 0

Instruction Set

Table 1.7 MIPS instruction set (subset supported)

Instruction	Function	Encoding	op	funct
add \$1, \$2, \$3	addition: $\$1 \leftarrow \$2 + \$3$	R	000000	100000
sub \$1, \$2, \$3	subtraction: $\$1 \leftarrow \$2 - \$3$	R	000000	100010
and \$1, \$2, \$3	bitwise and: $\$1 \leftarrow \$2 \text{ and } \$3$	R	000000	100100
or \$1, \$2, \$3	bitwise or: $\$1 \leftarrow \$2 \text{ or } \$3$	R	000000	100101
slt \$1, \$2, \$3	set less than: $\$1 \leftarrow 1 \text{ if } \$2 < \$3$ $\$1 \leftarrow 0 \text{ otherwise}$	R	000000	101010
addi \$1, \$2, imm	add immediate: $\$1 \leftarrow \$2 + \text{imm}$	I	001000	n/a
beq \$1, \$2, imm	branch if equal: $\text{PC} \leftarrow \text{PC} + \text{imm}^a$	I	000100	n/a
j destination	jump: $\text{PC} \leftarrow \text{destination}^a$	J	000010	n/a
lb \$1, imm(\$2)	load byte: $\$1 \leftarrow \text{mem}[\$2 + \text{imm}]$	I	100000	n/a
sb \$1, imm(\$2)	store byte: $\text{mem}[\$2 + \text{imm}] \leftarrow \1	I	101000	n/a

a. Technically, MIPS addresses specify bytes. Instructions require a four-byte word and must begin at addresses that are a multiple of four. To most effectively use instruction bits in the full 32-bit MIPS architecture, branch and jump constants are specified in words and must be multiplied by four (shifted left two bits) to be converted to byte addresses.

CS/EE 3710

Instruction Encoding

 


FIG 1.49 Instruction encoding formats

CS/EE 3710

Fibonacci C-Code

```
int fib(void)
{
    int n = 8;           /* compute nth Fibonacci number */
    int f1 = 1, f2 = -1; /* last two Fibonacci numbers */

    while (n != 0) {    /* count down to n = 0 */
        f1 = f1 + f2;
        f2 = f1 - f2;
        n = n - 1;
    }
    return f1;
}
```

FIG 1.50 C code for Fibonacci program

CS/EE 3710

Fibonacci C-Code

```
int fib(void)
{
    int n = 8;           /* compute nth Fibonacci number */
    int f1 = 1, f2 = -1; /* last two Fibonacci numbers */

    while (n != 0) {    /* count down to n = 0 */
        f1 = f1 + f2;
        f2 = f1 - f2;
        n = n - 1;
    }
    return f1;
}
```

FIG 1.50 C code for Fibonacci program

Cycle 1: $f1 = 1 + (-1) = 0$, $f2 = 0 - (-1) = 1$

Cycle 2: $f1 = 0 + 1 = 1$, $f2 = 1 - 1 = 0$

Cycle 3: $f1 = 1 + 0 = 1$, $f2 = 1 - 0 = 1$

Cycle 4: $f1 = 1 + 1 = 2$, $f2 = 2 - 1 = 1$

Cycle 5: $f1 = 2 + 1 = 3$, $f2 = 3 - 1 = 2$

Cycle 6: $f1 = 3 + 2 = 5$, $f2 = 5 - 2 = 3$

Fibonacci Assembly Code

```

# fib.asm
# Register usage: $3: n $4: f1 $5: f2
# return value written to address 255
fib:  addi $3, $0, 8      # initialize n=8
      addi $4, $0, 1      # initialize f1 = 1
      addi $5, $0, -1     # initialize f2 = -1
loop: beq $3, $0, end    # Done with loop if n = 0
      add $4, $4, $5      # f1 = f1 + f2
      sub $5, $4, $5      # f2 = f1 - f2
      addi $3, $3, -1     # n = n - 1
      j loop              # repeat until done
end:  sb $4, 255($0)     # store result in address 255
    
```

FIG 1.51 Assembly language code for Fibonacci program

Compute 8th Fibonacci number (8'd13 or 8'h0D)
Store that number in memory location 255

CS/EE 3710

Fibonacci Machine Code

Instruction	Binary Encoding	Hexadecimal Encoding
addi \$3, \$0, 8	001000 00000 00011 0000000000001000	20030008
addi \$4, \$0, 1	001000 00000 00100 0000000000000001	20040001
addi \$5, \$0, -1	001000 00000 00101 1111111111111111	2005ffff
beq \$3, \$0, end	000100 00011 00000 0000000000000101	1060000 4
add \$4, \$4, \$5	000000 00100 00101 00100 00000 100000	00852020
sub \$5, \$4, \$5	000000 00100 00101 00101 00000 100010	00852822
addi \$3, \$3, -1	001000 00011 00011 1111111111111111	2063ffff
j loop	000010 000000000000000000000000000011	08000003
sb \$4, 255(\$0)	101000 00000 00100 0000000011111111	a00400ff

FIG 1.52 Machine language code for Fibonacci program


Assembly Code


Machine Code

CS/EE 3710

Architecture

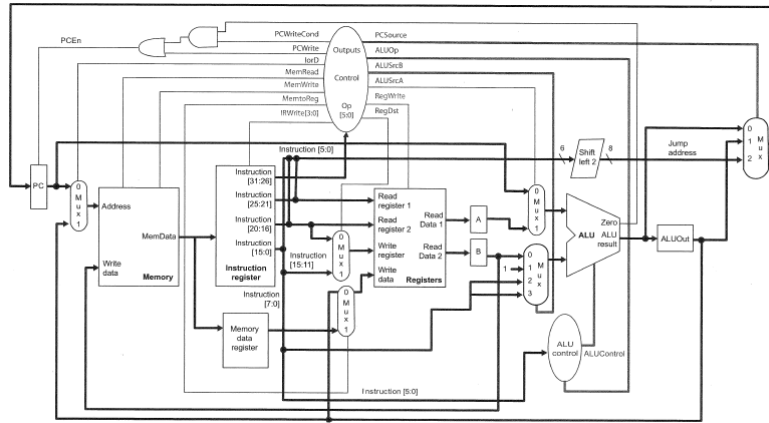


FIG 1.53 Multicycle MIPS microarchitecture. Reprinted from [Patterson04] with permission from Elsevier.

CS/EE 3710

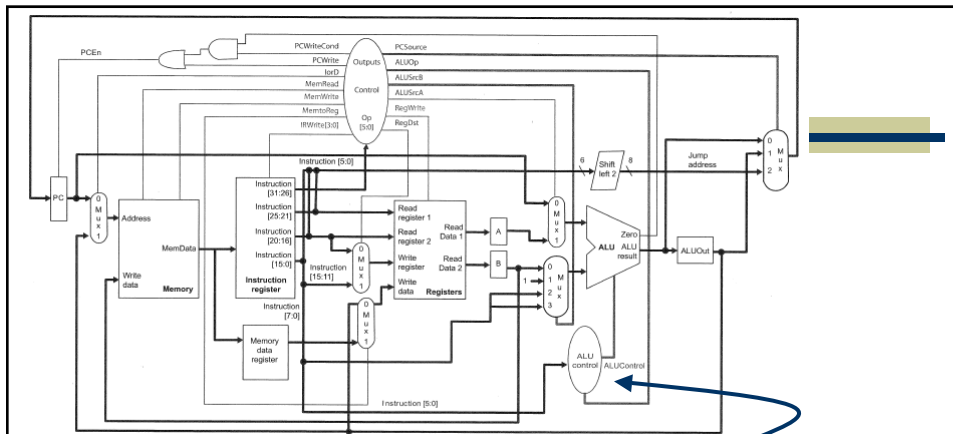



FIG 1.53 Multicycle MIPS microarchitecture. Reprinted from [Patterson04]

Table 1.8 ALUControl determination


aluop	funct	alucontrol	Meaning
00	x	010	ADD
01	x	110	SUB
10	100000	010	ADD
10	100010	110	SUB
10	100100	000	AND
10	100101	001	OR
10	101010	111	SLT
11	x	x	undefined

CS/EE 3710

Another View

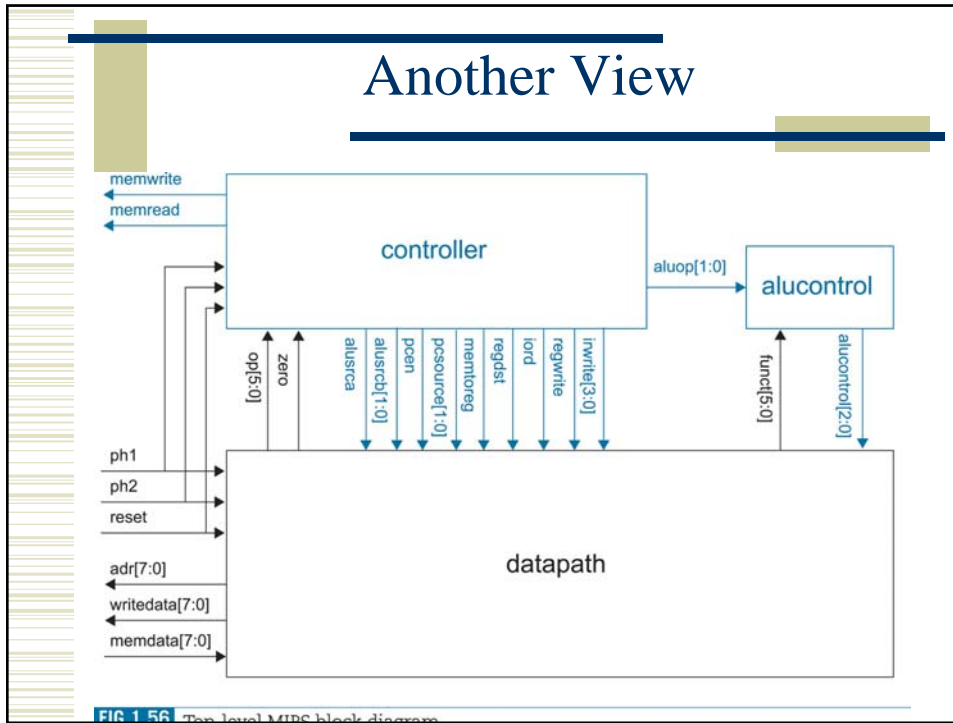

Control FSM

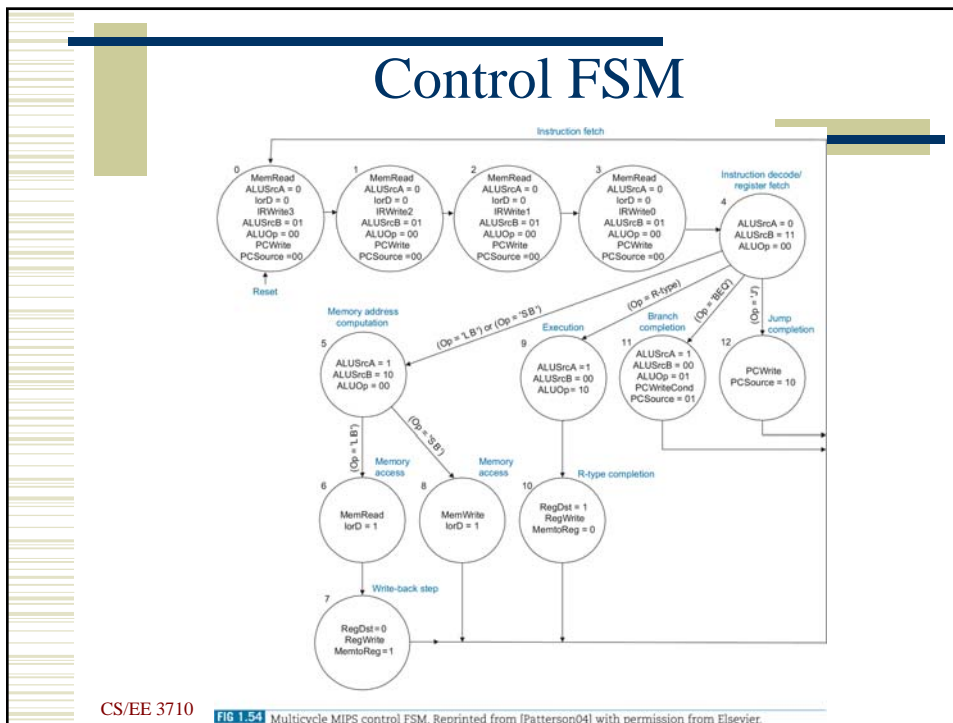

Connection to External Memory

Table 1.9 Top-level inputs and outputs

Inputs	Outputs
ph1	adr[7:0]
ph2	writedata[7:0]
reset	memread
memdata[7:0]	memwrite

 


FIG 1.55 MIPS computer system

External Memory from Book

```
// external memory accessed by MIPS
module exmemory #(parameter WIDTH = 8)
  (input      clk,
   input      memwrite,
   input  [WIDTH-1:0] adr, writedata,
   output reg [WIDTH-1:0] memdata);

  reg [31:0] RAM [(1<<WIDTH-2)-1:0];
  wire [31:0] word;

  // Initialize memory with program
  initial $readmemh("memfile.dat",RAM);

  // read and write bytes from 32-bit word
  always @(posedge clk)
    if(memwrite)
      case (adr[1:0])
        2'b00: RAM[adr>>2][7:0] <= writedata;
        2'b01: RAM[adr>>2][15:8] <= writedata;
        2'b10: RAM[adr>>2][23:16] <= writedata;
        2'b11: RAM[adr>>2][31:24] <= writedata;
      endcase
endmodule
```

```
assign word = RAM[adr>>2];
always @(*)
  case (adr[1:0])
    2'b00: memdata <= word[7:0];
    2'b01: memdata <= word[15:8];
    2'b10: memdata <= word[23:16];
    2'b11: memdata <= word[31:24];
  endcase
endmodule
```

Notes:

- Endianness is fixed here
- Writes are on posedge clk
- Reads are asynchronous
- This is a 32-bit wide RAM
- With 64 locations
- But with an 8-bit interface...

Exmem.v

```
module exmem #(parameter WIDTH = 8, RAM_ADDR_BITS = 8)
  (input clk, en,
   input memwrite,
   input [RAM_ADDR_BITS-1:0] adr,
   input [WIDTH-1:0] writedata,
   output reg [WIDTH-1:0] memdata);
  reg [WIDTH-1:0] mips_ram [(2**RAM_ADDR_BITS)-1:0];

  initial $readmemb("fib.dat", mips_ram);

  always @(posedge clk)
    if (en) begin
      if (memwrite)
        mips_ram[adr] <= writedata;
      memdata <= mips_ram[adr];
    end

endmodule
```

CS/EE 3710

- This is synthesized to a Block RAM on the Spartan3e FPGA
- It's 8-bits wide
- With 256 locations
- Both writes and reads are clocked

Exmem.v

```
module exmem #(parameter WIDTH = 8, RAM_ADDR_BITS = 8)
  (input clk, en,
   input memwrite,
   input [RAM_ADDR_BITS-1:0] adr,
   input [WIDTH-1:0] writedata,
   output reg [WIDTH-1:0] memdata);
  reg [WIDTH-1:0] mips_ram [(2**RAM_ADDR_BITS)-1:0];

  initial $readmemb("fib.dat", mips_ram);

  always @(posedge clk)
    if (en) begin
      if (memwrite)
        mips_ram[adr] <= writedata;
      memdata <= mips_ram[adr];
    end


endmodule
```

CS/EE 3710


This is synthesized to a Block RAM on the Spartan3e FPGA

Note clock!

Block RAM

 


(b) Single-Port

 

WRITE_MODE = WRITE_FIRST 3443_11_262503

 Byte-wide Block RAM is really 9-bits – parity bit...



WRITE_MODE = READ_FIRST 3443_11_262503

Write Mode	Effect on Same Port
WRITE_FIRST Read After Write (Default)	Data on DI, DIP inputs written into specified RAM location and simultaneously appears on DO, DOP outputs.
READ_FIRST Read Before Write (Recommended)	Data from specified RAM location appears on DO, DOP outputs. Data on DI, DIP inputs written into specified location.
NO_CHANGE No Read on Write	Data on DO, DOP outputs remains unchanged. Data on DI, DIP inputs written into specified location.

(Actually dual ported too!)

Our Block Ram

◆ Read-first or Write-first?

```

always @(posedge clk)
  if (en) begin
    if (memwrite)
      mips_ram[adr] <= writedata;
    memdata <= mips_ram[adr];
  end
  
```

Read_First Template

```

parameter RAM_WIDTH = <ram_width>;
parameter RAM_ADDR_BITS = <ram_addr_bits>;


reg [RAM_WIDTH-1:0] <ram_name> [(2**RAM_ADDR_BITS)-1:0];
reg [RAM_WIDTH-1:0] <output_data>;

<reg_or_wire> [RAM_ADDR_BITS-1:0] <address>;
<reg_or_wire> [RAM_WIDTH-1:0] <input_data>;

// The following code is only necessary if you wish to initialize the RAM
// contents via an external file (use $readmemb for binary data)
initial
    $readmemb("<data_file_name>", <rom_name>, <begin_address>, <end_address>);

always @(posedge <clock>)
    if (<ram_enable>) begin
        if (<write_enable>) begin
            <ram_name>[<address>] <= <input_data>;
            <output_data> <= <ram_name>[<address>];
        end
    end
end

```

 

CS/EE 3710

3443_13_262803

Write_First Template

```

parameter RAM_WIDTH = <ram_width>;
parameter RAM_ADDR_BITS = <ram_addr_bits>;


reg [RAM_WIDTH-1:0] <ram_name> [(2**RAM_ADDR_BITS)-1:0];
reg [RAM_WIDTH-1:0] <output_data>;

<reg_or_wire> [RAM_ADDR_BITS-1:0] <address>;
<reg_or_wire> [RAM_WIDTH-1:0] <input_data>;

// The following code is only necessary if you wish to initialize the RAM
// contents via an external file (use $readmemb for binary data)
initial
    $readmemb("<data_file_name>", <rom_name>, <begin_address>, <end_address>);

always @(posedge <clock>)
    if (<ram_enable>) begin
        if (<write_enable>) begin
            <ram_name>[<address>] <= <input_data>;
            <output_data> <= <input_data>;
        end
        else
            <output_data> <= <ram_name>[<address>];
    end
end

```

 

CS/EE 3710

3443_11_262803

Read_First waveforms

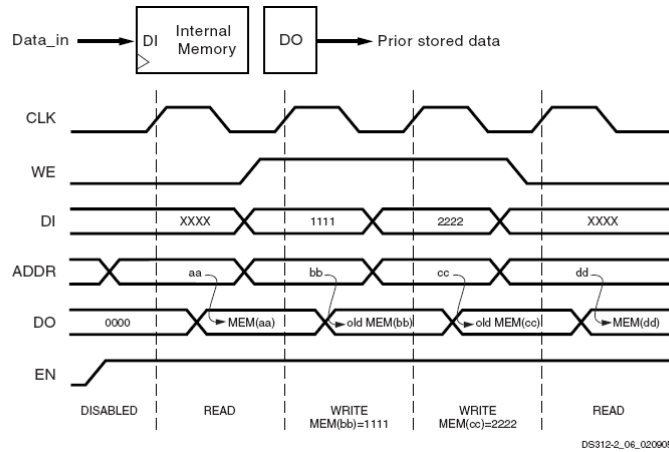


Figure 34: Waveforms of Block RAM Data Operations with READ_FIRST Selected

CS/EE 3710

Write_First Waveforms

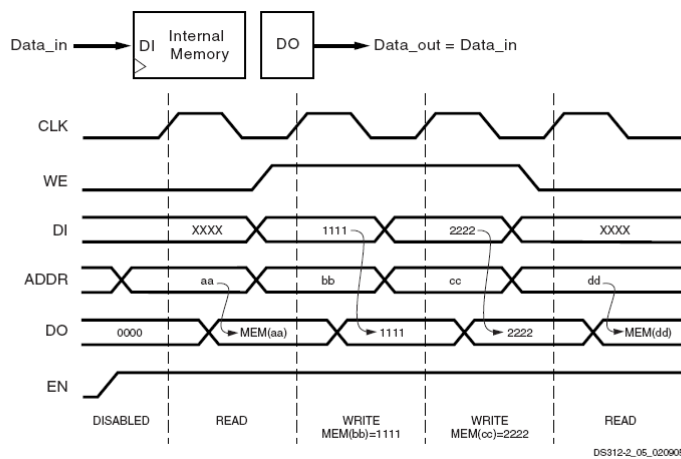


Figure 33: Waveforms of Block RAM Data Operations with WRITE_FIRST Selected

CS/EE 3710

Block RAM Organization

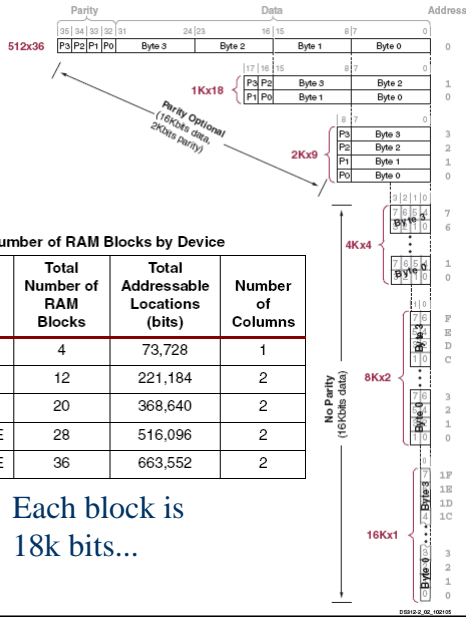



Table 21: Number of RAM Blocks by Device

Device	Total Number of RAM Blocks	Total Addressable Locations (bits)	Number of Columns
XC3S100E	4	73,728	1
XC3S250E	12	221,184	2
XC3S500E	20	368,640	2
XC3S1200E	28	516,096	2
XC3S1600E	36	663,552	2

Each block is 18k bits...

Block RAM is Single or Dual ported

 1. Write to and read from Port A
2. Write to and read from Port B
3. Data transfer from Port A to Port B
4. Data transfer from Port B to Port A



Recall – Overall System

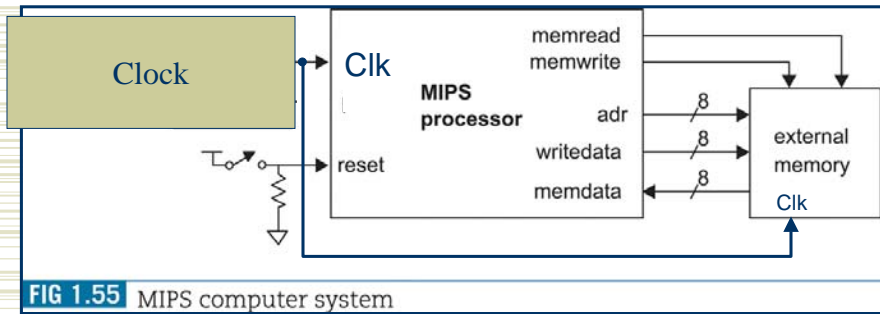


FIG 1.55 MIPS computer system

Recall – Overall System

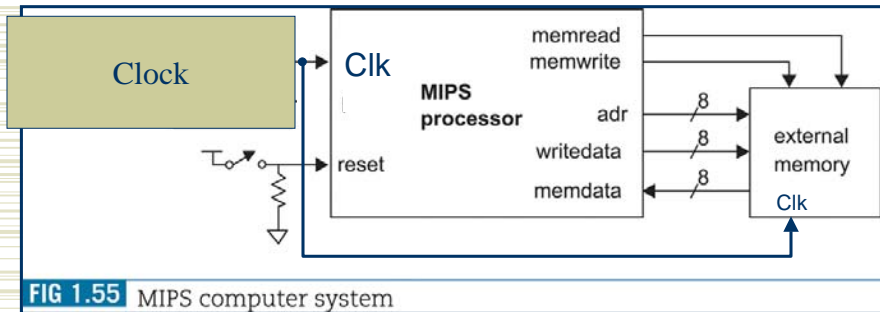


FIG 1.55 MIPS computer system

So, what are the implications of using a RAM that has both clocked reads and writes instead of clocked writes and async reads? (we'll come back to this question...)

CS/EE 3710

mips Block Diagram

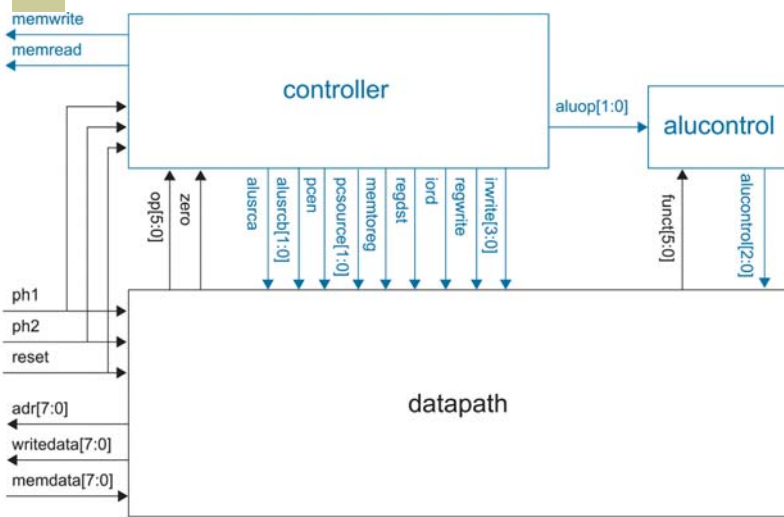


FIG 1.56 Top-level MIPS block diagram

mips.v

```
// simplified MIPS processor
module mips #(parameter WIDTH = 8, REGBITS = 3)
  (input      clk, reset,
   input [WIDTH-1:0] memdata,
   output     memread, memwrite,
   output [WIDTH-1:0] adr, writedata);

  wire [31:0] instr;
  wire  zero, alusrc, memtoreg, iord, pcen, regwrite, regdst;
  wire [1:0] aluop, pcsourc, alusrcb;
  wire [3:0] irwrite;
  wire [2:0] alucont;

  controller cont(clk, reset, instr[31:26], zero, memread, memwrite,
                 alusrc, memtoreg, iord, pcen, regwrite, regdst,
                 pcsourc, alusrcb, aluop, irwrite);
  alucontrol ac(aluop, instr[5:0], alucont);
  datapath dp(clk, reset, memdata, alusrc, memtoreg, iord, pcen,
              regwrite, regdst, pcsourc, alusrcb, irwrite, alucont,
              zero, instr, adr, writedata);
endmodule
```

Controller

```
module controller(input clk, reset,
                 input [5:0] op,
                 input zero,
                 output reg memread, memwrite, alusrc, memtoreg, iord,
                 output reg pcen,
                 output reg regwrite, regdst,
                 output reg [1:0] pcsourc, alusrcb, aluop,
                 output reg [3:0] irwrite);

  parameter FETCH1 = 4'b0001;
  parameter FETCH2 = 4'b0010;
  parameter FETCH3 = 4'b0011;
  parameter FETCH4 = 4'b0100;
  parameter DECODE = 4'b0101;
  parameter MEMADR = 4'b0110;
  parameter LBRD = 4'b0111;
  parameter LBWR = 4'b1000;
  parameter SBWR = 4'b1001;
  parameter RTYPEEX = 4'b1010;
  parameter RTYPEWR = 4'b1011;
  parameter BEQEX = 4'b1100;
  parameter JEX = 4'b1101;

  parameter LB = 6'b100000;
  parameter SB = 6'b101000;
  parameter RTYPE = 6'b0;
  parameter BEQ = 6'b000100;
  parameter J = 6'b000010;

  reg [3:0] state, nextstate;
  reg pcwrite, pcwritecond;


  // state register
  always @(posedge clk)
    if(reset) state <= FETCH1;
    else state <= nextstate;
```

State Codes

Useful constants to compare against

State Register

Control FSM

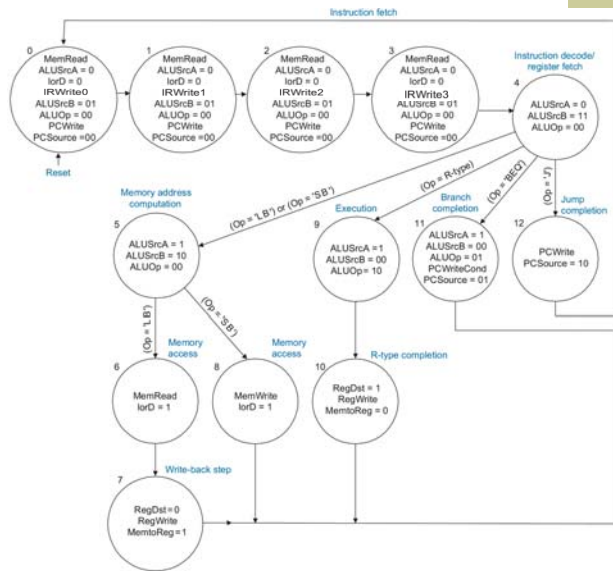

CS/EE 3710

FIG. 1.54 Multicycle MIPS control FSM. Reprinted from [Patterson04] with permission from Elsevier

Next State Logic

```
// next state logic
always @(*)
begin
  case(state)
    FETCH1: nextstate <= FETCH2;
    FETCH2: nextstate <= FETCH3;
    FETCH3: nextstate <= FETCH4;
    FETCH4: nextstate <= DECODE;
    DECODE: case(op)
      LB: nextstate <= MEMADR;
      SB: nextstate <= MEMADR;
      RTYPE: nextstate <= RTYPEEX;
      BEQ: nextstate <= BEQEX;
      J: nextstate <= JEX;
      default: nextstate <= FETCH1; // should never happen
    endcase
    MEMADR: case(op)
      LB: nextstate <= LBRD;
      SB: nextstate <= SBWR;
      default: nextstate <= FETCH1; // should never happen
    endcase
    LBRD: nextstate <= LBWR;
    LBWR: nextstate <= FETCH1;
    SBWR: nextstate <= FETCH1;
    RTYPEEX: nextstate <= RTYPEWR;
    RTYPEWR: nextstate <= FETCH1;
    BEQEX: nextstate <= FETCH1;
    JEX: nextstate <= FETCH1;
    default: nextstate <= FETCH1; // should never happen
  endcase
end
```

CS/EE 3710

Output Logic

```

always @(*)
begin
    // set all outputs to zero, then conditionally assert
    // just the appropriate ones
    irwrite <= 4'b0000;
    pcwrite <= 0; pcwritecond <= 0;
    regwrite <= 0; regdst <= 0;
    memread <= 0; memwrite <= 0;
    alusrca <= 0; alusrcb <= 2'b00; aluop <= 2'b00;
    pcsource <= 2'b00;
    iord <= 0; memtoreg <= 0;
    case(state)
        FETCH1:
            begin
                memread <= 1;
                irwrite <= 4'b0001; // changed to reflect new memory and
                alusrcb <= 2'b01; // get the IR bits in the right spots
                pcwrite <= 1; // FETCH 2,3,4 also changed...
            end
        FETCH2:
            begin
                memread <= 1;
                irwrite <= 4'b0010;
                alusrcb <= 2'b01;
                pcwrite <= 1;
            end
        FETCH3:
            begin
                memread <= 1;
                irwrite <= 4'b0100;
                alusrcb <= 2'b01;
                pcwrite <= 1;
            end
    endcase
end

```

Very common way
to deal with default
values in combinational
Always blocks

Continued for the other states...

Output Logic

```

        SBWR:
            begin
                memwrite <= 1;
                iord <= 1;
            end
        RTYPEEX:
            begin
                alusrca <= 1;
                aluop <= 2'b10;
            end
        RTYPEWR:
            begin
                regdst <= 1;
                regwrite <= 1;
            end
        BEQEX:
            begin
                alusrca <= 1;
                aluop <= 2'b01;
                pcwritecond <= 1;
                pcsource <= 2'b01;
            end
        JEX:
            begin
                pcwrite <= 1;
                pcsource <= 2'b10;
            end
    endcase
end
assign pcen = pcwrite | (pcwritecond & zero); // program counter enable
endmodule

```

Two places to update the PC
pcwrite on jump
pcwritecond on BEQ

Why AND these two?

ALU Control

```

module alucontrol(input      [1:0] aluop,
                 input      [5:0] funct,
                 output reg [2:0] alucont);

always @(*)
  case(aluop)
    2'b00: alucont <= 3'b010; // add for lb/sb/addi
    2'b01: alucont <= 3'b110; // sub (for beq)
    default: case(funct) // R-Type instructions
      6'b100000: alucont <= 3'b010; // add (for add)
      6'b100010: alucont <= 3'b110; // subtract (for sub)
      6'b100100: alucont <= 3'b000; // logical and (for and)
      6'b100101: alucont <= 3'b001; // logical or (for or)
      6'b101010: alucont <= 3'b111; // set on less (for slt)
      default: alucont <= 3'b101; // should never happen
    endcase
  endcase
endmodule

```

Table 1.8 ALUControl determination

aluop	funct	alucontrol	Meaning
00	x	010	ADD
01	x	110	SUB
10	100000	010	ADD
10	100010	110	SUB
10	100100	000	AND
10	100101	001	OR
10	101010	111	SLT
11	x	x	undefined

CS/EE 3710

ALU

```

module alu #(parameter WIDTH = 8)
  (input  [WIDTH-1:0] a, b,
   input  [2:0]      alucont,
   output reg [WIDTH-1:0] result);

  wire [WIDTH-1:0] b2, sum, slt;

  assign b2 = alucont[2] ? ~b:b;
  assign sum = a + b2 + alucont[2];
  // slt should be 1 if most significant bit of sum is 1
  assign slt = sum[WIDTH-1];

  always@(*)
    case(alucont[1:0])
      2'b00: result <= a & b;
      2'b01: result <= a | b;
      2'b10: result <= sum;
      2'b11: result <= slt;
    endcase
endmodule

```

Invert b if subtract...

add is a + b
sub is a + ~b + 1

subtract on slt
then check if answer is negative

CS/EE 3710

zerodetect

```
module zerodetect #(parameter WIDTH = 8)
    (input [WIDTH-1:0] a,
     output          y);

    assign y = (a==0);
endmodule
```

CS/EE 3710

Register File

```
module regfile #(parameter WIDTH = 8, REGBITS = 3)
    (input          clk,
     input          regwrite,
     input [REGBITS-1:0] ra1, ra2, wa,
     input [WIDTH-1:0] wd,
     output [WIDTH-1:0] rd1, rd2);

    reg [WIDTH-1:0] RAM [(1<<REGBITS)-1:0];

    // three ported register file
    // read two ports combinationaly
    // write third port on rising edge of clock
    // register 0 hardwired to 0
    always @(posedge clk)
        if (regwrite) RAM[wa] <= wd;

    assign rd1 = ra1 ? RAM[ra1] : 0;
    assign rd2 = ra2 ? RAM[ra2] : 0;
endmodule
```

What is this synthesized into?

CS/EE 3710

Synthesis Report

HDL Synthesis Report

Macro Statistics

```
# RAMs : 3
  256x8-bit single-port RAM : 1
  8x8-bit dual-port RAM : 2
# Adders/Subtractors : 1
  8-bit adder carry in : 1
# Registers : 10
  8-bit register : 10
# Multiplexers : 3
  8-bit 4-to-1 multiplexer : 3
```

CS/EE 3710

Synthesis Report

Synthesizing (advanced) Unit <exmem>.

INFO:Xst - The RAM <Mram_mips_ram> will be implemented as a BLOCK RAM, absorbi

ram_type	Block		
Port A			
aspect ratio	256-word x 8-bit		
mode	read-first		
clkA	connected to signal <clk>	rise	
enA	connected to signal <en>	high	
weA	connected to signal <memwrite>	high	
addrA	connected to signal <adr>		
diA	connected to signal <writedata>		
doA	connected to signal <memdata>		
optimization	speed		

CS/EE 3710

Synthesis Report

Synthesizing (advanced) Unit <regfile>.

INFO:Xst - The small RAM <Mram_RAM> will be implemented on LUTs in order to max

ram_type	Distributed	
Port A		
aspect ratio	8-word x 8-bit	
clkA	connected to signal <clk>	rise
weA	connected to signal <regwrite>	high
addrA	connected to signal <wa>	
diA	connected to signal <wd>	
Port B		
aspect ratio	8-word x 8-bit	
addrB	connected to signal <ra1>	
doB	connected to internal node	

Two register files? Why?

INFO:Xst - The small RAM <Mram_RAM_ren> will be implemented on LUTs in order to

ram_type	Distributed	
Port A		
aspect ratio	8-word x 8-bit	
clkA	connected to signal <clk>	rise
weA	connected to signal <regwrite>	high
addrA	connected to signal <wa>	
diA	connected to signal <wd>	
Port B		
aspect ratio	8-word x 8-bit	
addrB	connected to signal <ra2>	
doB	connected to internal node	

CS/EE 3710

Datapath

```

module datapath #(parameter WIDTH = 8, REGBITS = 3)
    (input
        clk, reset,
        input [WIDTH-1:0] memdata,
        input alusrca, memtoereg, iord,
        input pcen, regwrite, regdst,
        input [1:0] pcsource, alusrca,
        input [3:0] irwrite,
        input [2:0] alucont,
        output zero,
        output [31:0] instr,
        output [WIDTH-1:0] adr, writedata);

    // the size of the parameters must be changed to match the WIDTH parameter
    localparam CONST_ZERO = 8'b0;
    localparam CONST_ONE = 8'b1;

    wire [REGBITS-1:0] ra1, ra2, wa;
    wire [WIDTH-1:0] pc, nextpc, md, rd1, rd2, wd, a, src1, src2, aluresult,
        aluout, constx4;

    // shift left constant field by 2
    assign constx4 = {instr[WIDTH-3:0], 2'b00};

    // register file address fields
    assign ra1 = instr[REGBITS+20:24];
    assign ra2 = instr[REGBITS+15:16];
    mux2 #(REGBITS) regmux(instr[REGBITS+15:16], instr[REGBITS+10:11], regdst, wa);

    // independent of bit width, load instruction into four
    // 8-bit registers over four cycles
    flopen #(8) ir0(clk, irwrite[0], memdata[7:0], instr[7:0]);
    flopen #(8) ir1(clk, irwrite[1], memdata[7:0], instr[15:8]);
    flopen #(8) ir2(clk, irwrite[2], memdata[7:0], instr[23:16]);
    flopen #(8) ir3(clk, irwrite[3], memdata[7:0], instr[31:24]);
    
```

Fairly complex...

Not really, but it does have lots of registers instantiated directly


It also instantiates muxes...

Instruction Register

Datapath continued

```
// datapath
flopnr  #(WIDTH) pcreg(clk, reset, pcen, nextpc, pc);
flop    #(WIDTH) ndr(clk, mndata, md);
flop    #(WIDTH) areg(clk, rd1, a);
flop    #(WIDTH) wrd(clk, rd2, writedata);
flop    #(WIDTH) res(clk, aluresult, aluout);
mux2    #(WIDTH) admux(pc, aluout, iord, adr);
mux2    #(WIDTH) src1mux(pc, a, alusrca, src1);
mux4    #(WIDTH) src2mux(writedata, CONST_ONE, instr[WIDTH-1:0],
                        constx4, alusrca, src2);
mux4    #(WIDTH) pcmux(aluresult, aluout, constx4, CONST_ZERO, pcsource, nextpc);
mux2    #(WIDTH) wdmux(aluout, md, mentoreg, wd);
regfile #(WIDTH,REGBITS) rf(clk, regwrite, ra1, ra2, wa, wd, rd1, rd2);
alu     #(WIDTH) alunit(src1, src2, alucont, aluresult);
zerodetect #(WIDTH) zd(aluresult, zero);
endmodule
```

Flops and
muxes...

 

RF and
ALU

CS/EE 3710

FIG. 1.63 Multi-cycle MIPS microarchitecture. Reprinted from [Patterson04] with permission from Elsevier.

Flops and MUXes

```
module flop #(parameter WIDTH = 8)
    (input      clk,
     input  [WIDTH-1:0] d,
     output reg [WIDTH-1:0] q);

    always @(posedge clk)
        q <= d;
endmodule

module flopen #(parameter WIDTH = 8)
    (input      clk, en,
     input  [WIDTH-1:0] d,
     output reg [WIDTH-1:0] q);

    always @(posedge clk)
        if (en) q <= d;
endmodule

module flopnr #(parameter WIDTH = 8)
    (input      clk, reset, en,
     input  [WIDTH-1:0] d,
     output reg [WIDTH-1:0] q);

    always @(posedge clk)
        if (reset) q <= 0;
        else if (en) q <= d;
endmodule

module mux2 #(parameter WIDTH = 8)
    (input  [WIDTH-1:0] d0, d1,
     input      s,
     output [WIDTH-1:0] y);

    assign y = s ? d1 : d0;
endmodule

module mux4 #(parameter WIDTH = 8)
    (input  [WIDTH-1:0] d0, d1, d2, d3,
     input  [1:0] s,
     output reg [WIDTH-1:0] y);

    always @(*)
        case(s)
            2'b00: y <= d0;
            2'b01: y <= d1;
            2'b10: y <= d2;
            2'b11: y <= d3;
        endcase
endmodule
```

CS/EE 3710

Back to the Memory Question

- ◆ What are the implications of using RAM that is clocked on both write and read?
 - Book version was async read
 - So, let's look at the sequence of events that happen to read the instruction
 - Four steps – read four bytes and put them in four slots in the 32-bit instruction register (IR)

CS/EE 3710

Instruction Fetch


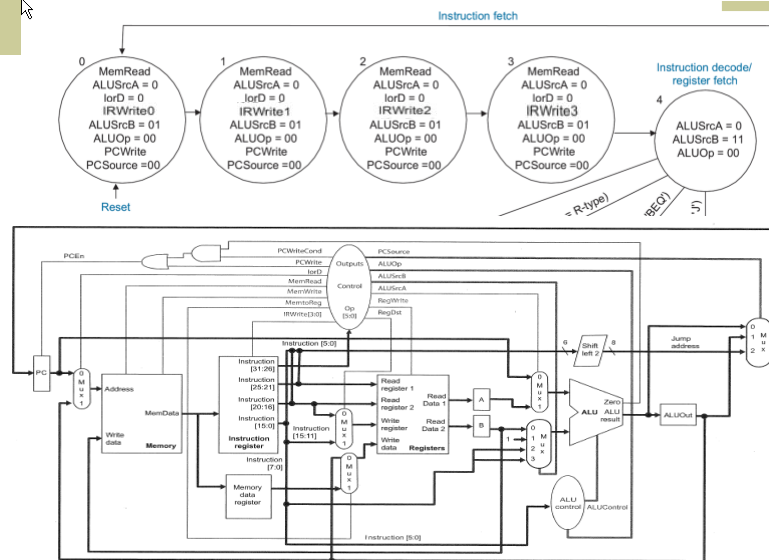


FIG 1.53 Multicycle MIPS microarchitecture. Reprinted from [Patterson04] with permission from Elsevier.

Instruction Fetch

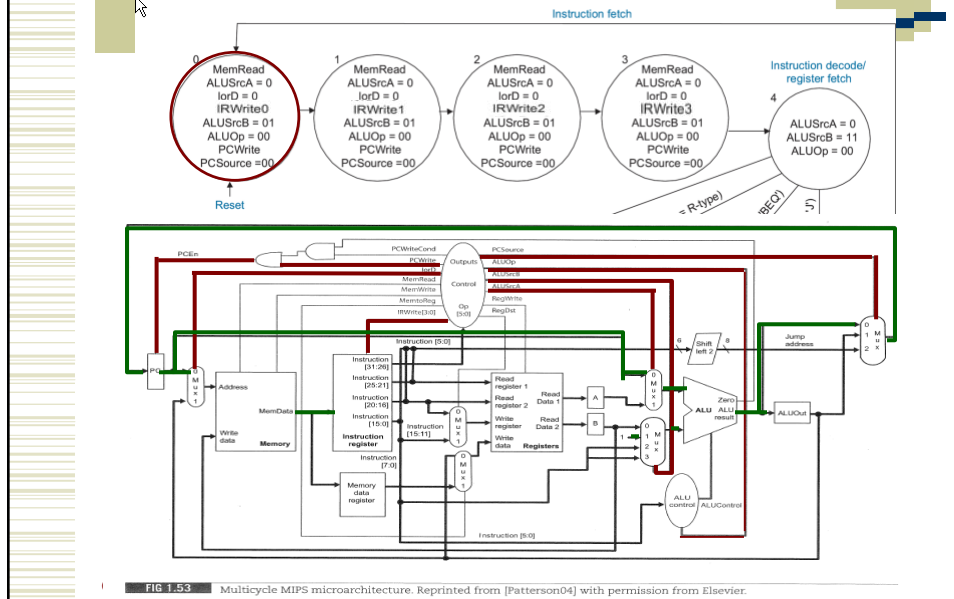

Instruction Fetch

```
// independent of bit width, load instruction into four
// 8-bit registers over four cycles
flopen #(8) ir0(clk, irwrite[0], memdata[7:0], instr[7:0]);
flopen #(8) ir1(clk, irwrite[1], memdata[7:0], instr[15:8]);
flopen #(8) ir2(clk, irwrite[2], memdata[7:0], instr[23:16]);
flopen #(8) ir3(clk, irwrite[3], memdata[7:0], instr[31:24]);
```

Instruction Register


```
module flopen #(parameter WIDTH = 8)
    (input clk, en,
     input [WIDTH-1:0] d,
     output reg [WIDTH-1:0] q);

    always @(posedge clk)
        if (en) q <= d;
endmodule
```

- Memread, irwrite, addr, etc are set up just after clk edge
- Data comes back sometime after that (async)
- Data is captured in ir0 – ir3 on the next rising clk edge
- **How does this change if reads are clocked?**

CS/EE 3710

mips + exmem

 

mips is expecting async reads

exmem has clocked reads

One of those rare cases where using both edges of the clock is useful!


CS/EE 3710

Memory Mapped I/O

- ◆ Break memory space into pieces (ranges)
 - For some of those pieces: regular memory
 - For some of those pieces: I/O
 - That is, reading from an address in that range results in getting data from an I/O device
 - Writing to an address in that range results in data going to an I/O device


CS/EE 3710

Mini-MIPS Memory Map

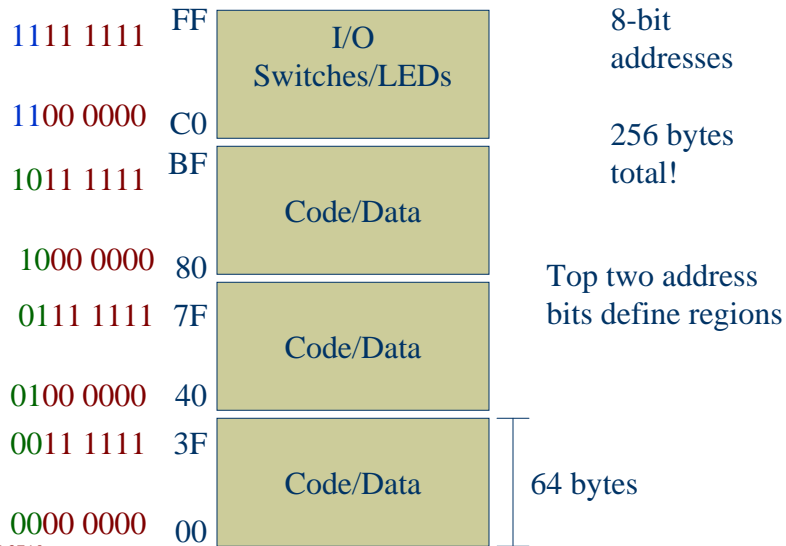

CS/EE 3710

Enabled Devices

 

Only write to that device (i.e. enable it) if you're in the appropriate memory range.

Check top two address bits!

```

module flopen #(parameter WIDTH = 8)
    (input          clk, en,
     input  [WIDTH-1:0] d,
     output reg [WIDTH-1:0] q);

    always @(posedge clk)
        if (en) q <= d;
endmodule
    
```

CS/EE 3710

MUXes for Return Data

```

module mux2 #(parameter WIDTH = 8)
  (input [WIDTH-1:0] d0, d1,
   input s,
   output [WIDTH-1:0] y);


  assign y = s ? d1 : d0;
endmodule

```

Use MUX to decide if data is coming from memory or from I/O

Check address bits!

CS/EE 3710

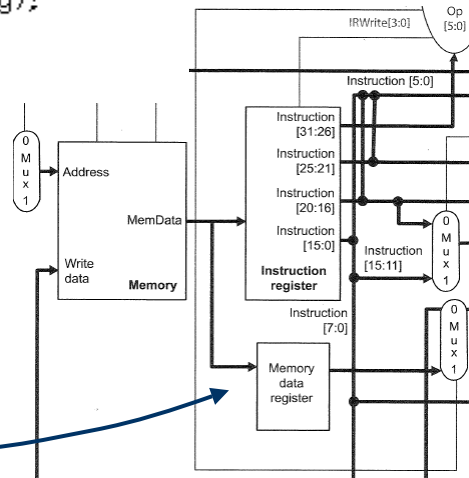

Lab2 in a Nutshell

- ◆ Understand and simulate mips/exmem
 - Add **ADDI** instruction
 - Fibonacci program – correct if 8'0d is written to memory location 255
- ◆ Augment the system
 - Add memory mapped I/O to switches/LEDs
 - Write new Fibonacci program
 - Simulate in ISE
 - Demonstrate on your board

CS/EE 3710

My Initial Testbench...


```

2
3 `timescale 1ns / 1ps
4
5 module mips_mem_mips_mem_sch_tb();
6
7 // Inputs
8 reg clk;
9 reg reset;
10
11 // Output
12 wire memread;
13
14 // Bidirs
15
16 // Instantiate the UUT
17 mips_mem UUT (
18     .clk(clk),
19     .memread(memread),
20     .reset(reset)
21 );
22 // Initialize Inputs
23 initial begin
24     reset <= 1;
25     #22 reset <= 0;
26     end
27
28 // Generate clock to sequence tests
29 always
30 begin
31     clk <= 1; # 5; clk <= 0; # 5;
32 end
33
34 // check the data on the memory interface between mips and exmem
35 // If you're writing, and the address is 255, then the data should
36 // be 8'h0d if you've computed the correct 8th Fibonacci number
37 always@(negedge clk)
38 if (UUT.memwrite)
39     if (UUT.addr == 8'd255 & UUT.wdata == 8'h0d)
40         $display("Yay - Fibonacci completed successfully!");
41     else $display("Oops - wrong value written to addr 255: %h", UUT.wdata);
42

```

CS/EE 3710

My Initial Results

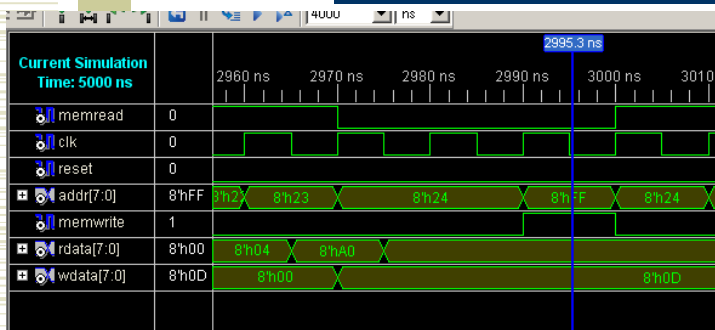

```

Processes Options Sim Objects
What's New in ISE Design

This is a Lite version of ISE Simulator (ISim).
Simulator is doing circuit initialization process.
Finished circuit initialization process.
run 4000 ns
Yay - Fibonacci completed successfully!
%

```