

## CS/ECE 6780/5780

AI Davis

### Today's topics:


- Debouncing switches
- e.g. matrix keypad
- lab4 issues

## Basic Concepts

- Switches are often mechanical
  - move something and
    - » contact is made or broken
  - In either case
    - » metal rebounds
      - causing "hash" oscillations in the observed signal
      - source of massive ISR confusion if you're not careful
- Problem
  - make multiple events look like one event
  - usual solution
    - » hardware debounce
      - extra logic
    - » software debounce
      - focus for this weeks lab
- See "debouncing.pdf" on the class web site
  - figures in the next few slides come from this document
  - » thanks to Jack Ganssle for an interesting read

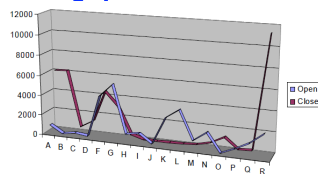
## Switch Anatomy

- Lots of types
  - SPST, SPDT, DPDT, and beyond
- How long does a switch bounce
  - varies with switch type and often assymetric w/ open vs. close
  - » typical a few ms but can be as bad as 100's of ms
  - » also varies even for a single switch
    - min to max can vary by 2x or so
- Ganssle's findings (bounce times in usec)



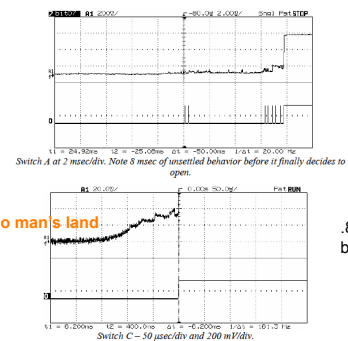
## Switches and TTL Sampling Levels

- Aliasing happens in the analog to digital transition




### Switch G

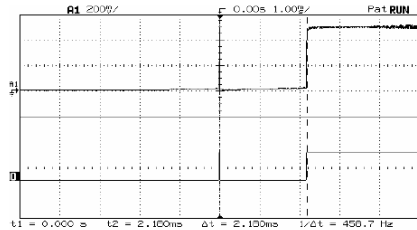


Switch G. One super narrow pulse followed by 2 msec of nothingness. A sure-fire ISR confuser.

### Switch O

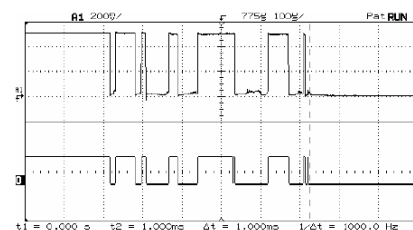

Switch O, which zaps around enough to confuse dumb debouncers.

### Switch Q

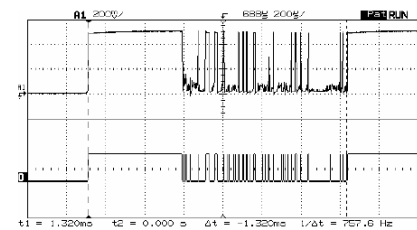


Switch Q – when released, it goes high for 480  $\mu$ sec before generating 840  $\mu$ sec of hash, a sure way to blow an interrupt system mad if poorly designed.

### Bottom Line

- In general
  - characterize the switches before you use them
    - » a thorough test takes a lot of time
      - vary how you activate
      - take scope traces
      - use multiple versions of the same switch
  - PCB mounted switches are often better than these somewhat pathological examples
    - » but it is wise to check
  - weird behavior or intermittent failure
    - » suspect your debounce method

## SR Latch HW Debouncer

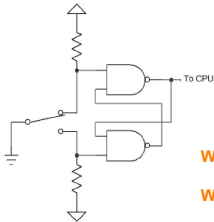

Why does it work?

What switch property is required?

Downside?

## SR Software Equivalent

### • Simplest possible code

#### ▪ examine both inputs

- » one will bounce the other won't
- » simple loop

```
if (switch_hi()) state=ON;
if (switch_lo()) state=OFF;
```

#### » problems


- 2 input capture pins required
- SPDT switches are more costly and bulky
  - rarely found on PCB's these days

## RC Debouncer

### • Simple


- but hides a lot of complexity
- need to characterize hash time to know desired RC time constant

What's tricky here?

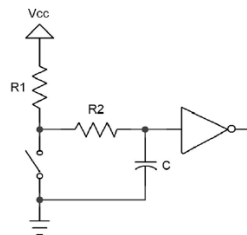


## A Better RC Debouncer


### • Why is this one better?

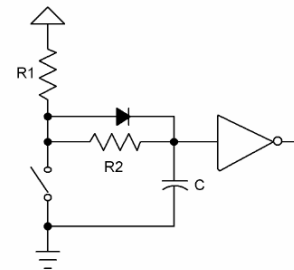

## Schmitt Trigger Debounce

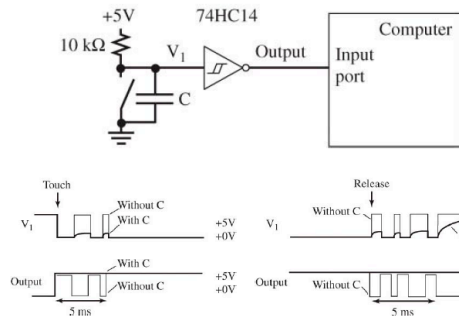


## 2R Schmitt Debounce

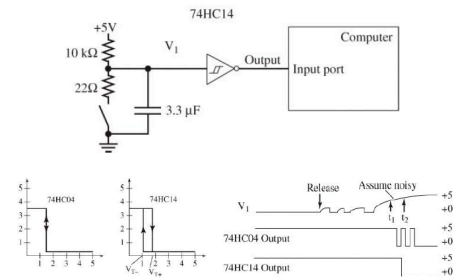

Similar slew decoupling issue but w/ hysteresis
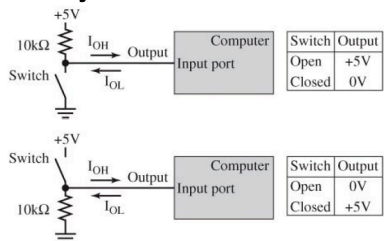
## Switch Interfaces


- HW debouncers make SW's life easier
  - but adds to cost
  - so let's consider a direct SPST interface w/ SW debounce
    - 6812 style



## 6812 Ports

- Ports AD, J, M, P, S and T
  - support both internal pull-ups and pull-down resistors
    - note to use port AD as a digital port
      - corresponding bits in ATDDIEN must be set
  - Port Pull Select Register must be set
    - PPSAD, PPSJ, PPSF, PPSM, PPSS, PPST
      - pull-up = 0, pull-down = 1
  - Pull Enable Register
    - PERAD, PERJ, PERP, PERM, PERS, PERT
      - enables the pull-up or pull-down function
  - Note
    - first set PPSx then PERx
    - if enable happens before select then get signals in possibly the wrong polarity


## Port AD Initialization Example

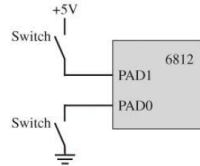

```
void PortAD_Init(void){
    ATDDIEN |= 0x03; // PAD1-0 digital I/O
    DDRAD &= ~0x03; // PAD1-0 inputs
    PPSAD |= 0x02; // pull-down on PAD1
    PPSAD &= ~0x01; // pull-up on PAD0
    PERAD |= 0x03; // enable pull-up and pull-down
}
```

## Software Debounce Model


- Assume bounce time <10ms

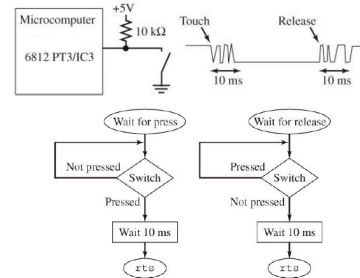

## Software Debounce w/ Gadfly Timer

```
void Key_WaitPress(void){
    while(PTT&0x08); // PT3=0 when pressed
    Timer_Wait10ms(1); // debouncing
}
void Key_WaitRelease(void){
    while((PTT&0x08)==0); // PT3=1 -> released
    Timer_Wait10ms(1); // debouncing
}
void Key_Init(void){
    Timer_Init();
    DDRT &= ~0x08; // PT3 is input
}
```

## SW Debounce Version 2

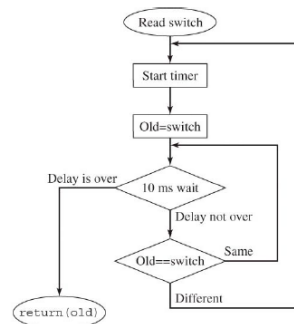

This version returns a new value every time switch position changes

Unified press and release functions

Same <10ms hash assumption

## Timer Control & Output Compare

- **Use**
  - create squarewaves, generate pulses, implement time delays, generate periodic interrupts
- **6812 has 8 output compare modules**
  - Each module has
    - » external output pin (OCn)
    - » flag bit, interrupt mask bit, and 16-bit output compare register
    - » force output compare bit (FOCn)
    - » two mode bits (OMn OIn)

Table 15-9. Compare Result Output Action

OMx	OLx	Action
0	0	Timer disconnected from output pin logic
0	1	Toggle OCx output line
1	0	Clear OCx output line to zero
1	1	Set OCx output line to one

MC9S12 reference manual

## Output Compare Process Example

- **Basic steps**
  - read the current 16-bit TCNT
  - calculate TCNT+delay
  - set output compare register to TCNT+delay
  - clear the output compare flag
  - wait for the output compare flag to be set
- **Essentially another SW debounce approach**

## Output Compare

```
void Key_Init(void) {
    TIOS |= 0x20;    // enable OC5 (see Chapter 6)
    TSCR1 = 0x80;    // enable
    TSCR2 = 0x01;    // 500 ns clock
    DDRT &=~0x08;    // PT3 is input
}

unsigned char Key_Read(void){
    unsigned char old;
    old = PTT&0x08;    // Current value
    TC5 = TCNT+20000;    // 10ms delay
    TFLG1 = 0x20;    // Clear C5F
    while((TFLG1&0x20)==0){ // 10ms
        if(old!=(PTT&0x08)){ // changed?
            old = PTT&0x08;    // New value
            TC5 = TCNT+20000;    // restart delay
        }
    }
    return(old); }

```

## Debouncing Multiple Switches

```
#define MAX_CHECKS 10
uint8_t Debounced_State;
uint8_t State[MAX_CHECKS];
uint8_t Index;

void DebounceSwitches(void) {
    uint8_t i,j;
    State[Index] = ReadKeys();
    Index++;
    j = 0xff;
    for(i=0;i<MAX_CHECKS-1;i++) {
        j &= State[i];
    }
    Debounced_State ^= j;
    if(Index >= MAX_CHECKS) { Index = 0; }
}

```

Based on "My favorite software debouncers" by Jack Ganssle.

## Interfacing Multiple Keys

### • 3 basic methods

#### ▪ direct – input pin per switch

- » downside is what happens if you have more switches than input pins
- » upside – you can recognize every possible switch combination
  - note this doesn't matter in a keyboard where one switch is pressed at a time
    - or very few – e.g. Shift, CTL, FN, ...


#### ▪ scanned

- » keys belong to a matrix
  - know the row and column and you know which key
  - 6812 drives one row low at each step (enables the row)
    - column values indicate which key in that row was pushed


#### ▪ multiplexed

- » same idea but uses less pins (e.g.  $\log_2 n$ )
  - put out binary value of the row
  - demux generates the one-hot code similar to the scanned mode
  - mux on the way back in does the symmetric function

## 3 Approach View

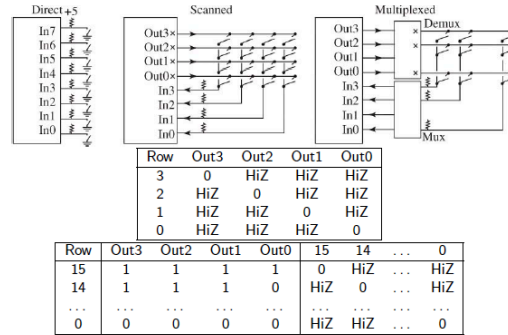

## 4x4 Scanned Keypad

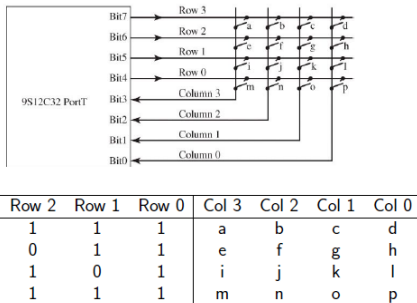

## 4x4 Keypad

### • Two steps to scan a particular row:

- select row by driving it low
  - » other rows stay Hi-Z
- read the columns to discover which key is pressed
  - » 0 → pressed in this case due to pull-up

### • Works If

- no key is pressed
- 1 key is pressed
- 2 keys are pressed
  - » note general case would allow up to 4

## 4x4 Handler Code

```
const struct Row
{ unsigned char direction;
  unsigned char keycode[4];}
typedef const struct Row RowType;
RowType ScanTab[5]={
{ 0x80, "abcd" }, // row 3
{ 0x40, "efgh" }, // row 2
{ 0x20, "ijkl" }, // row 1
{ 0x10, "mnop" }, // row 0
{ 0x00, "    " }};
void Key_Init(void){
  DDRT = 0x00; // PT3-PT0 inputs
  PTT = 0;     // PT7-PT4 oc output
  PPST = 0;    // pull-up on PT3-PT0
  PERT = 0x0F;}
```

continued next slide

## 4x4 Code (cont'd)

```
/* Returns ASCII code for key pressed,
   Num is the number of keys pressed
   both equal zero if no key pressed */
unsigned char Key_Scan(short *Num){
  RowType *pt; unsigned char column,key;
  short j;
  (*Num)=0; key=0; // default values
  pt=&ScanTab[0];
  while(pt->direction){
    DDRT = pt->direction; // one output
    column = PTT; // read columns
    for(j=3; j>=0; j--){
      if((column&0x01)==0){
        key = pt->keycode[j];
        (*Num)++;}
      column>>=1; // shift into position
      pt++; }
    return key;}
```

## Concluding Remarks

- **Controller sits in a sea of I's and O's**
  - might be a tight connection – e.g. keypad
    - » O's say what we care about
    - » I's say given what you care about this is what happened
- **Output compare tied to inputs are useful**
  - 6812 supports them
- **All switches are not created equal**
  - need to understand what you're working with
    - » then you'll know the debounce strategy
  - fortunately the 6812 understands most of this inequality
    - » and provides relatively simple & useful interface options
- **Non-switch interfaces**
  - analog input values
    - » must convert to digital via AD port
  - digital inputs – these are the simple ones