
CS/ECE 6780/5780

Al Davis

Today's topics:

- **Relays & Motors**
 - prelude to 5780 Lab 9

Relays

- **Common embedded system problem**
 - **digital control: relatively small I & V levels**
 - **controlled device requires significantly higher power**
- **Solution**
 - **amplify the control power**
 - **use the control signal to activate a switch**
 - » **switch turns on/off bigger power source**
- **Electrically controlled switches**
 - **transistor**
 - » **can be used as a switch but it's really an amplifier since it has gain**
 - **MOS – voltage controlled, BIPOLAR – current controlled**
 - **relay**
 - » **control induces magnetic field in coil**
 - » **magnetic field moves a mechanical switch**
 - **bounce problem?**
 - usually not a concern for outputs to non-digital gizmos like motors

Poles and Throws

- **Terminology used for switches**


- **relay is just an electrically controlled switch**

- » **pole – controlled**

- » **throw – contact point**

- » **relay difference – magnetic movement of pole**

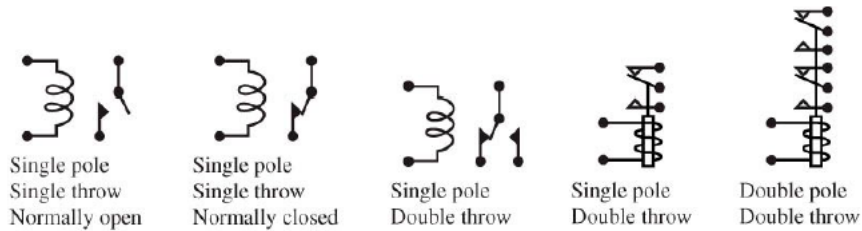- **difference in where the switch is when switch/magnet is off**
 - **off state usually controlled by a spring**



Relay Types

- **Basic issue is size**


- **control power**

- » **reed relays – smallish power**

- **common in ES designs**


- » **general purpose – large'ish power**

- **you have lots of them in your car**

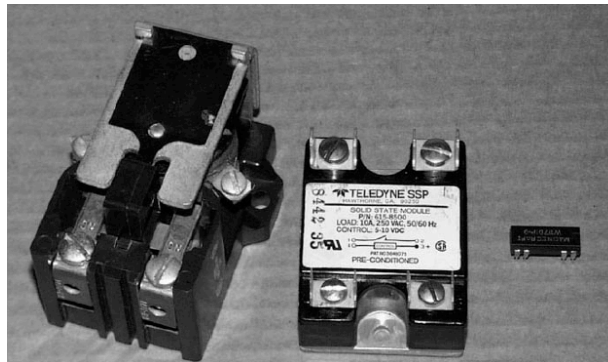


Mechanical DPDT Illustrated

Double Pole Double Throw (DPDT)

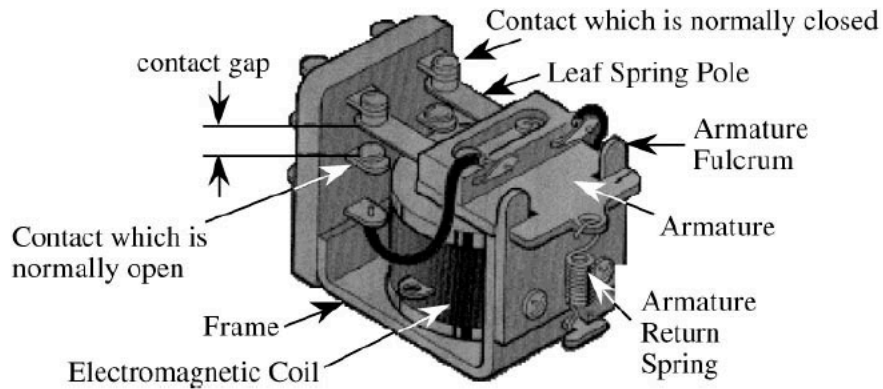


Solid State Relays

- **Improvement on mechanical relay problems**
 - **contact bounce and arcing limit lifetime**
 - **sensitive to vibrations, EMI issues**
 - **slow movement of large mechanical pole**
- **Optocoupler**
 - **provides electrical isolation between input (pseudocoil) and output triac (pseudocontact)**
 - » **particularly important in driving large inductive loads**
 - **zero-voltage detector triggers triac**
 - » **reduces surge currents when triac is switched**
 - **once triggered**
 - » **triac conducts until next zero crossing**

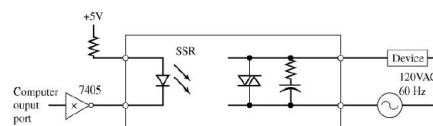


Reed Relays

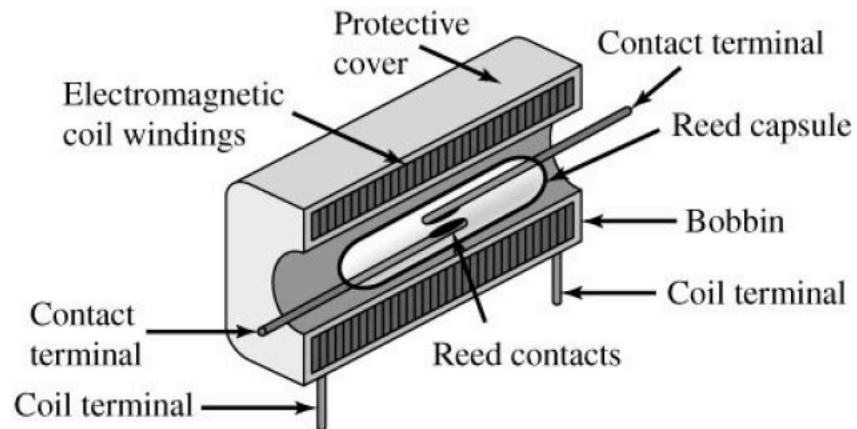Single Pole Single Throw (SPST) Reed Relay



Solenoids

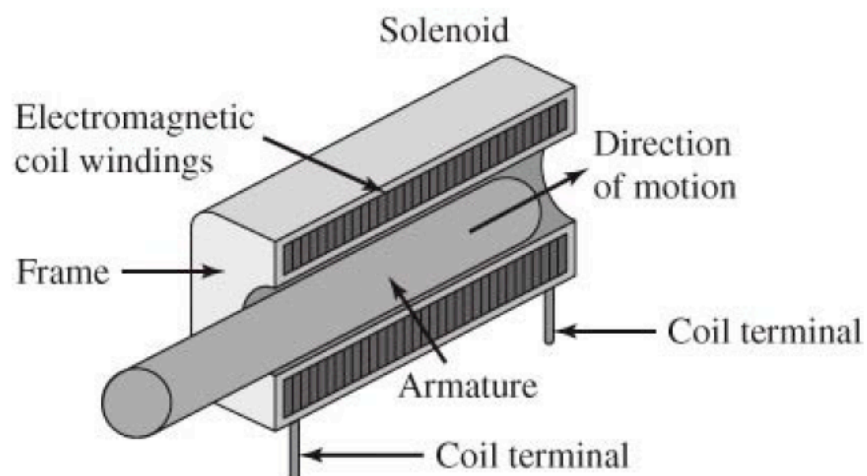


Interfacing to Inductive Loads

- **Interface circuit**
 - **must provide sufficient current and voltage to activate the device**
 - » **common error**
 - “my microcontroller puts out 5v but at the device it’s only 200 mV”
 - **what’s the problem?**


Interfacing to Inductive Loads

- **Interface circuit**
 - **must provide sufficient current and voltage to activate the device**
 - » **common error**
 - “my microcontroller puts out 5v but at the device it’s only 200 mV”
 - **what’s the problem?**
 - **Ohm’s law**
 - current, impedance and voltage are related
 - microcontroller can’t provide enough current so voltage is similarly low
 - **In off state current should be zero**
 - **BEWARE**
 - » **large L → huge back EMF when coil is turned off**
 - fast digital switch causes large di/dt
 - 50 – 200V back is common
 - » **it will destroy your controller**
 - **isolation or buffering is required**
 - optoisolator
 - or snub diode
 - etc.


Relay Control Examples

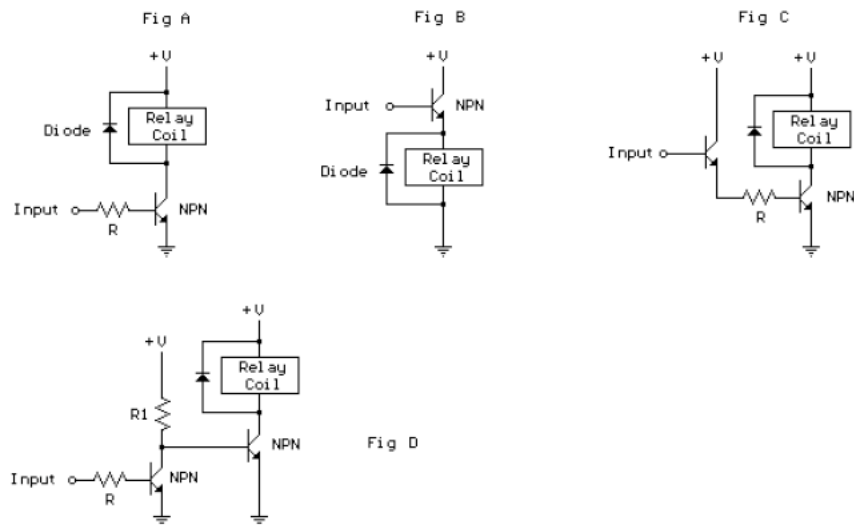


Relay & Motor Interfaces

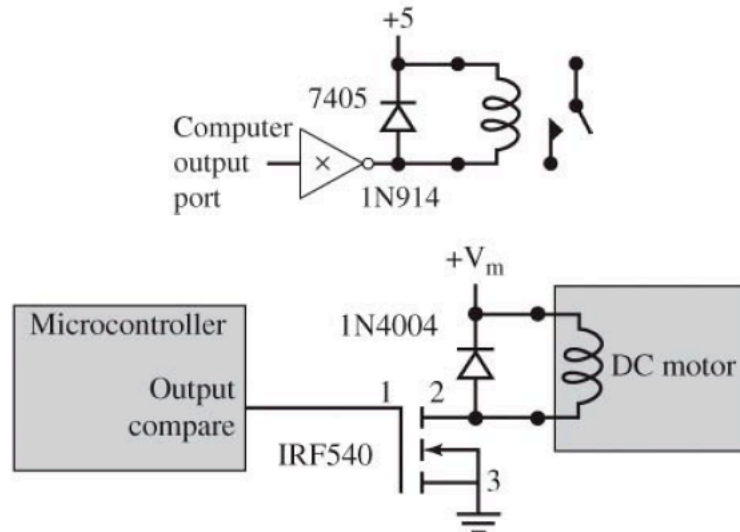

Typical H-Bridge Motor Control

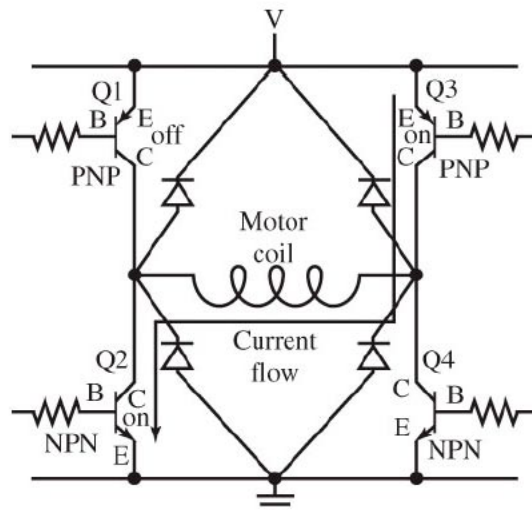


Isolated H-Bridge w/ Direction Control

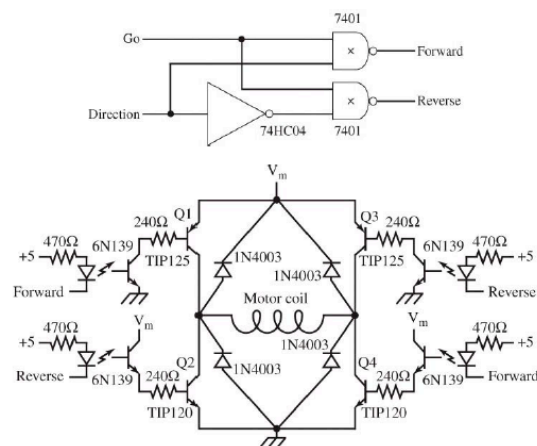


Stepper Motors

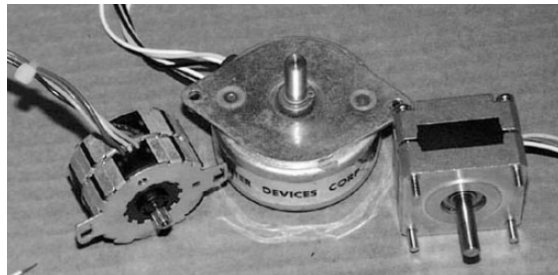- **Popular due to inherent digital interface**
 - **easy to control both position and velocity in an open-loop fashion**
 - **more expensive than simple DC motor**
 - » **still not too bad since may not require feedback sensors**
 - **can be used as shaft encoders**
 - » **measure both position and speed**




Stepper Motor Basics

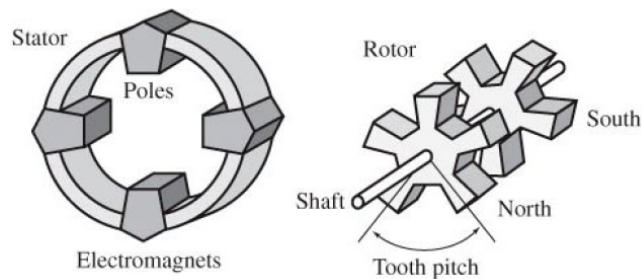- **Stator**
 - **stationary frame with electromagnet poles**
- **Rotor**
 - **teeth are permanent magnets alternating south and north pole teeth**




$$360 \text{ degrees} / (4 \text{ poles} * 5 \text{ teeth}) = 18 \text{ degrees per step}$$


2 Phase Operation

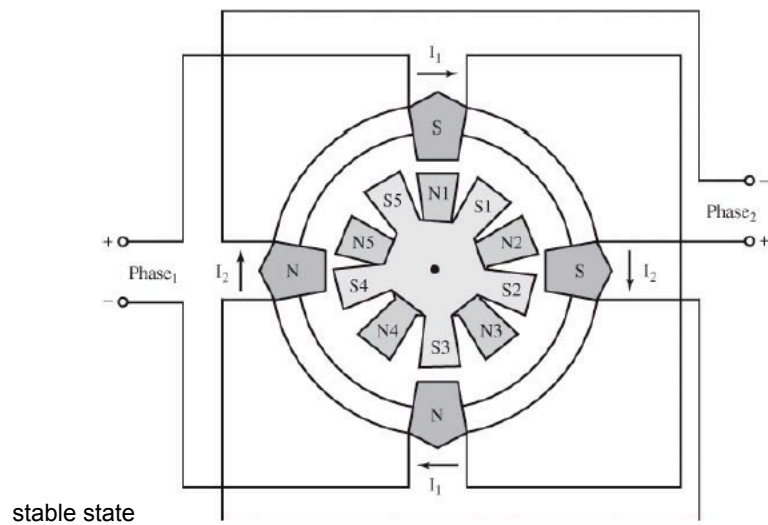


2 Phase Operation

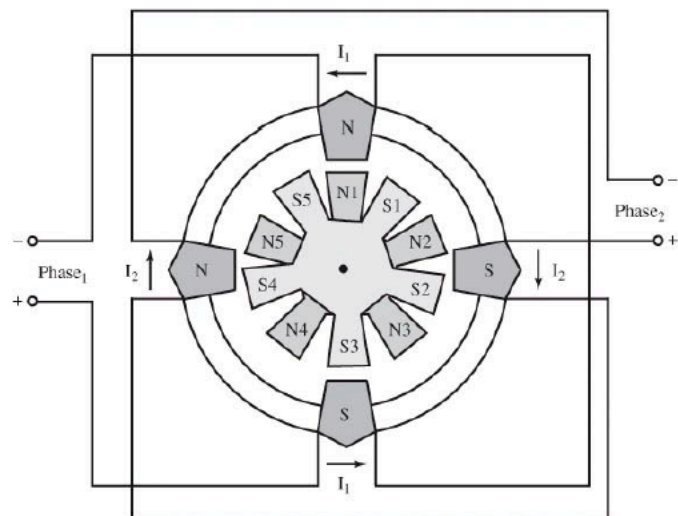


2 Phase Operation

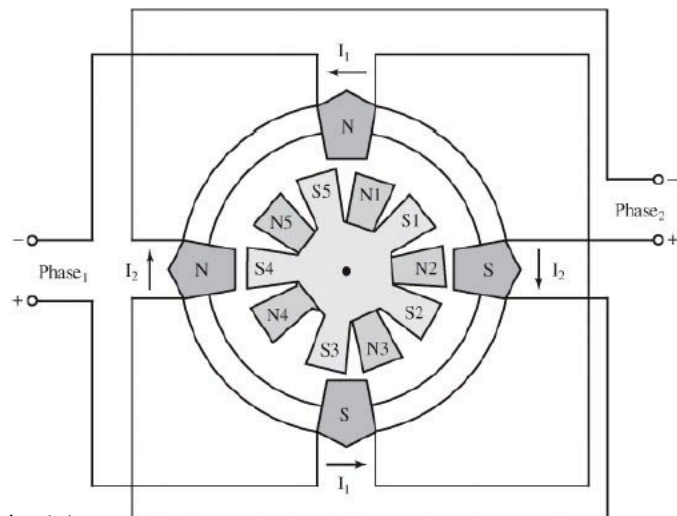


2 Phase Operation

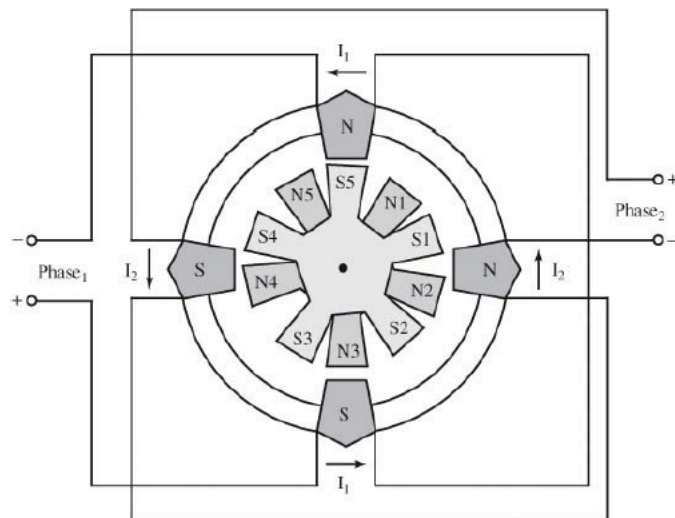

Continue by Reversing Phase 1

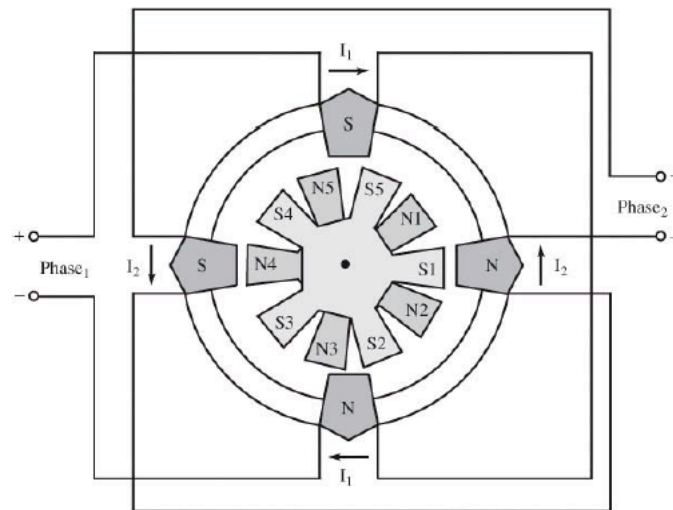

Simple Interface

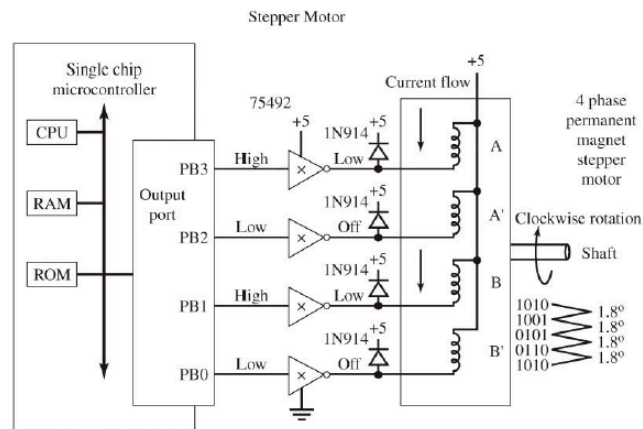


note this motor has 200 steps – hence 1.8 degrees
Port B output is (10, 9, 5, 6)*
reverse direction? (6, 5, 9, 10)*

Slip & Torque Issues

- **Slip**
 - **command issued but motor doesn't move**
 - **causes**
 - » **motor torque insufficient to drive mechanical load**
 - » **or if computer change is too fast**
 - → **magnetic field is too weak**
- **IF no slip can be guaranteed**
 - **then computer knows the shaft position**
 - » **and doesn't need a sensor**

Stepper Motor Sequence

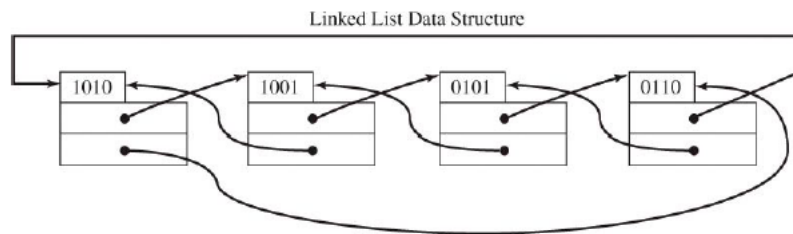

Control Data Structures (FSM)

```
const struct State{
    unsigned char Out;           // Output
    const struct State *Next[2]; // CW/CCW
};
typedef struct State StateType;
typedef StateType *StatePtr;
#define clockwise 0           // Next index
#define counterclockwise 1 // Next index
StateType fsm[4]={
    {10,{&fsm[1],&fsm[3]}},
    { 9,{&fsm[2],&fsm[0]}},
    { 5,{&fsm[3],&fsm[1]}},
    { 6,{&fsm[0],&fsm[2]}},
};
unsigned char Pos; // between 0 and 199
StatePtr Pt;      // Current State
```

Init Ritual

```
void Init(void){
    Pos = 0;
    Pt = &fsm[0];
    DDRB = 0xFF;
}
```

Helper Functions

```
void CW(void){
    Pt = Pt->Next[clockwise]; // circular
    PORTB = Pt->Out;           // step motor
    if(Pos==199){              // shaft angle
        Pos = 0;               // reset
    }else{
        Pos++;}                // CW
}
void CCW(void){
    Pt = Pt->Next[counterclockwise];
    PORTB = Pt->Out;           // step motor
    if(Pos==0){                // shaft angle
        Pos = 199;            // reset
    }else{
        Pos--;}               // CCW
}
```

High Level Control

```
void Seek(unsigned char desired){
    short CWsteps;
    if((CWsteps=desired-Pos)<0){
        CWsteps+=200;
    } // CW steps is 0 to 199
    if(CWsteps>100){
        while(desired!=Pos){
            CCW();
        }
    }
    else{
        while(desired!=Pos){
            CW();
        }
    }
}
```

Concluding Remarks

- **Lots of types of electrical motors**
 - **stepper & DC are most common in inexpensive ES's**
- **Beware when driving inductive loads**
 - **back EMF has to be controlled**
 - » **snub diode is cheap**
 - » **optical isolation is even more secure**
- **5780 students**
 - **lab 9 will get you provide an introduction**
 - **stepper motor kits available for checkout**