

CS/ECE 6780/5780

AI Davis

Today's topics:

- Relays & Motors
 - prelude to 5780 Lab 9

Relays

- Common embedded system problem
 - digital control: relatively small I & V levels
 - controlled device requires significantly higher power
- Solution
 - amplify the control power
 - use the control signal to activate a switch
 - » switch turns on/off bigger power source
- Electrically controlled switches
 - transistor
 - » can be used as a switch but it's really an amplifier since it has gain
 - MOS – voltage controlled, BIPOLAR – current controlled
 - relay
 - » control induces magnetic field in coil
 - » magnetic field moves a mechanical switch
 - bounce problem?
 - usually not a concern for outputs to non-digital gizmos like motors

Poles and Throws

- Terminology used for switches
 - relay is just an electrically controlled switch
 - » pole – controlled
 - » throw – contact point
 - » relay difference – magnetic movement of pole
 - difference in where the switch is when switch/magnet is off
 - off state usually controlled by a spring



Single pole
Single throw
Normally open



Single pole
Single throw
Normally closed



Single pole
Double throw



Single pole
Double throw



Double pole
Double throw


Relay Types

- Basic issue is size
 - control power
 - » reed relays – smallish power
 - common in ES designs
 - » general purpose – large-ish power
 - you have lots of them in your car




Mechanical DPDT Illustrated

Double Pole Double Throw (DPDT)

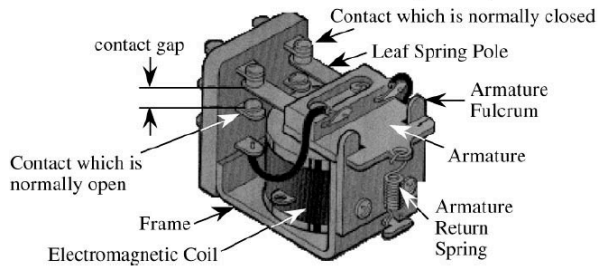


Solid State Relays

- **Improvement on mechanical relay problems**
 - contact bounce and arcing limit lifetime
 - sensitive to vibrations, EMI issues
 - slow movement of large mechanical pole
- **Optocoupler**
 - provides electrical isolation between input (pseudocoll) and output triac (pseudocontact)
 - » particularly important in driving large inductive loads
 - zero-voltage detector triggers triac
 - » reduces surge currents when triac is switched
 - once triggered
 - » triac conducts until next zero crossing

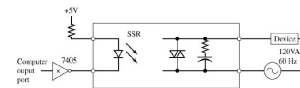


Reed Relays

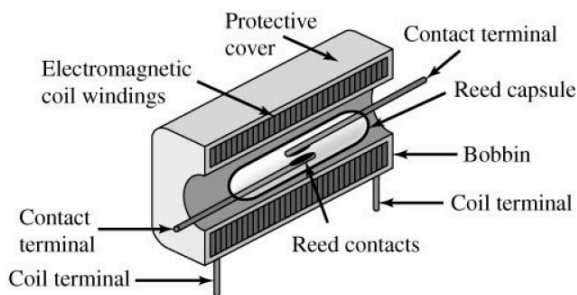Single Pole Single Throw (SPST) Reed Relay



Solenoids

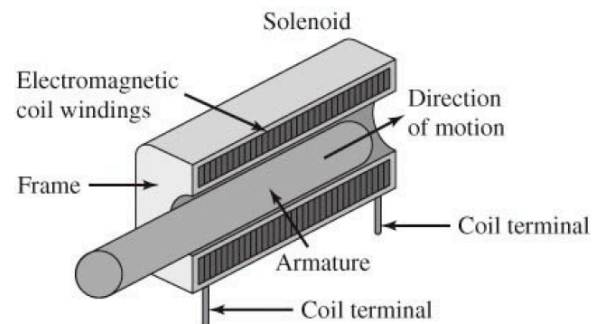


Interfacing to Inductive Loads

- **Interface circuit**
 - **must provide sufficient current and voltage to activate the device**
 - » **common error**
 - "my microcontroller puts out 5v but at the device it's only 200 mV"
 - **what's the problem?**


Interfacing to Inductive Loads

- **Interface circuit**
 - **must provide sufficient current and voltage to activate the device**
 - » **common error**
 - "my microcontroller puts out 5v but at the device it's only 200 mV"
 - **what's the problem?**
 - **Ohm's law**
 - current, impedance and voltage are related
 - microcontroller can't provide enough current so voltage is similarly low
 - **In off state current should be zero**
 - **BEWARE**
 - » **large L → huge back EMF when coil is turned off**
 - fast digital switch causes large dI/dt
 - 50 – 200V back is common
 - » **it will destroy your controller**
 - **isolation or buffering is required**
 - optoisolator
 - or snub diode
 - etc.

Relay Control Examples

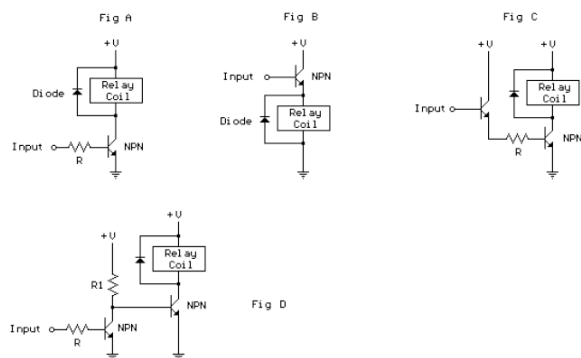


Relay & Motor Interfaces

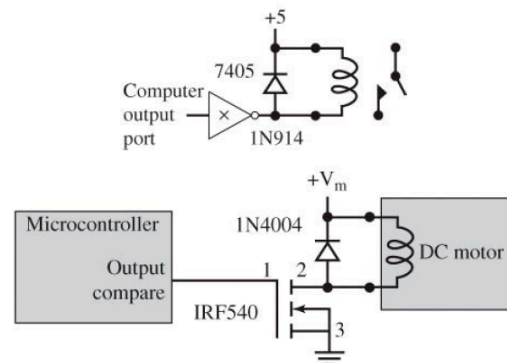

IRF 540 Power Transistor

SYMBOL

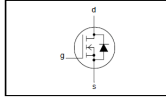


QUICK REFERENCE DATA

$V_{DS} = 100\text{ V}$
 $I_D = 23\text{ A}$
 $R_{DS(on)} \leq 77\text{ m}\Omega$


PINNING

PIN	DESCRIPTION
1	gate
2	drain ¹
3	source
tab	drain


SOT78 (TO220AB)

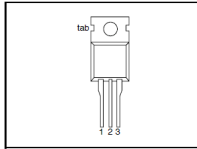


Isolated Interfaces

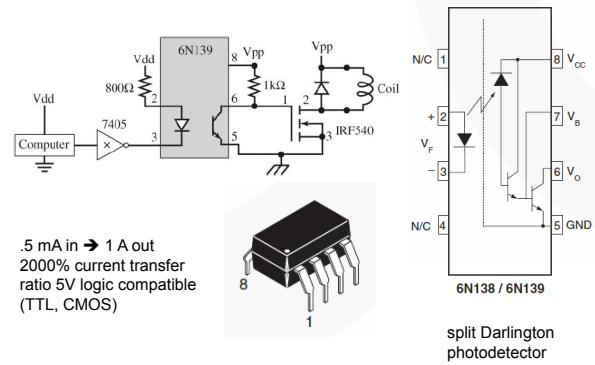

Typical H-Bridge Motor Control

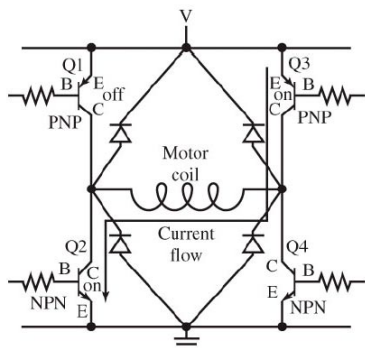

Isolated H-Bridge w/ Direction Control

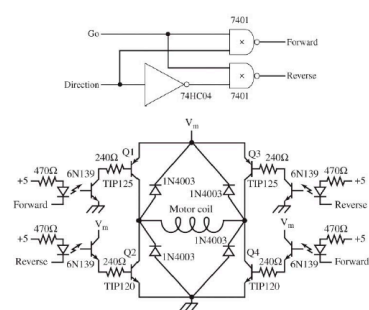


Stepper Motors

- **Popular due to inherent digital interface**
 - **easy to control both position and velocity in an open-loop fashion**
 - **more expensive than simple DC motor**
 - » **still not too bad since may not require feedback sensors**
 - **can be used as shaft encoders**
 - » **measure both position and speed**




Stepper Motor Basics

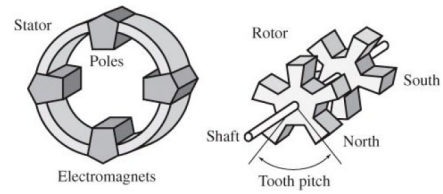- **Stator**
 - **stationary frame with electromagnet poles**
- **Rotor**
 - **teeth are permanent magnets alternating south and north pole teeth**




$$360 \text{ degrees} / (4 \text{ poles} * 5 \text{ teeth}) = 18 \text{ degrees per step}$$


2 Phase Operation

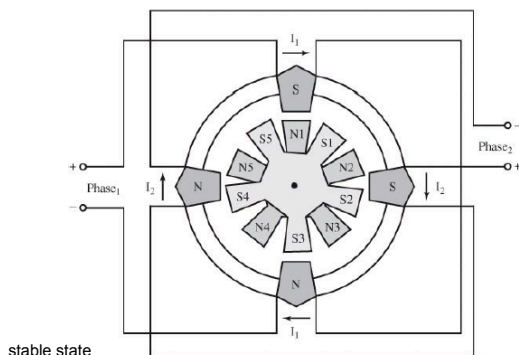

2 Phase Operation

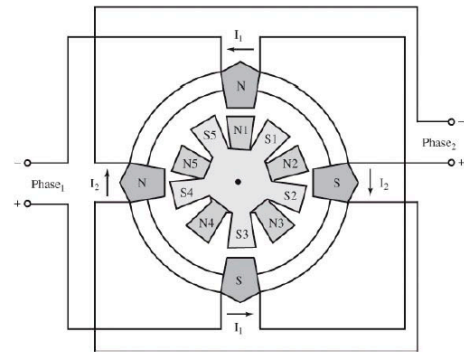


2 Phase Operation

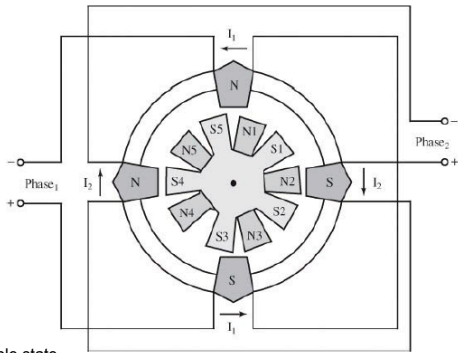


next stable state

2 Phase Operation

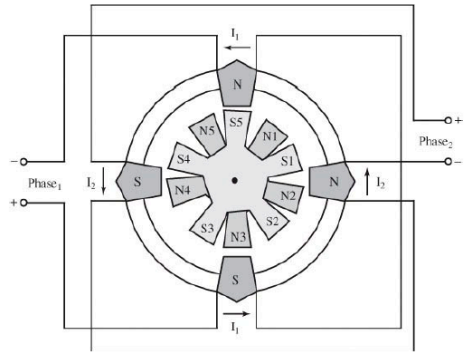


reverse polarity of phase 2 and movement continues

Continue by Reversing Phase 1

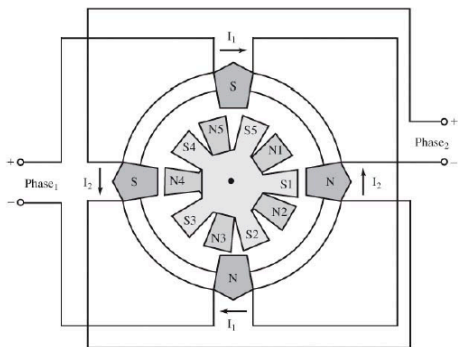

Simple Interface

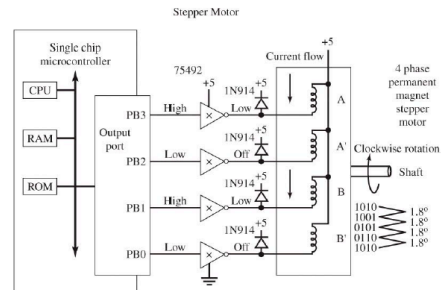


note this motor has 200 steps – hence 1.8 degrees
Port B output is (10, 9, 5, 6)*
reverse direction? (6, 5, 9, 10)*

Slip & Torque Issues

- **Slip**
 - **command issued but motor doesn't move**
 - **causes**
 - » **motor torque insufficient to drive mechanical load**
 - » **or if computer change is too fast**
 - → magnetic field is too weak
- **IF no slip can be guaranteed**
 - **then computer knows the shaft position**
 - » **and doesn't need a sensor**

Stepper Motor Sequence

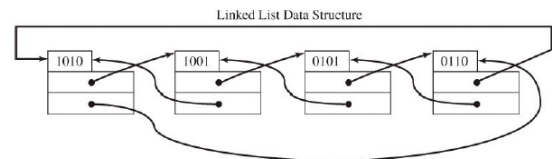

Control Data Structures (FSM)

```

const struct State{
    unsigned char Out;          // Output
    const struct State *Next[2]; // CW/CCW
};
typedef struct State StateType;
typedef StateType *StatePtr;
#define clockwise 0 // Next index
#define counterclockwise 1 // Next index
StateType fsm[4]={
    {10,{&fsm[1],&fsm[3]}},
    { 9,{&fsm[2],&fsm[0]}},
    { 5,{&fsm[3],&fsm[1]}},
    { 6,{&fsm[0],&fsm[2]}}};
unsigned char Pos; // between 0 and 199
StatePtr Pt;      // Current State
  
```

Init Ritual

```

void Init(void){
    Pos = 0;
    Pt = &fsm[0];
    DDRB = 0xFF;
}
  
```

Helper Functions

```
void CW(void){
    Pt = Pt->Next[clockwise]; // circular
    PORTB = Pt->Out;          // step motor
    if(Pos==199){              // shaft angle
        Pos = 0;              // reset
    }else{
        Pos++;}               // CW
}
void CCW(void){
    Pt = Pt->Next[counterclockwise];
    PORTB = Pt->Out;          // step motor
    if(Pos==0){                // shaft angle
        Pos = 199;            // reset
    }else{
        Pos--;}               // CCW
}
```

High Level Control

```
void Seek(unsigned char desired){
    short CWsteps;
    if((CWsteps=desired-Pos)<0){
        CWsteps+=200;
    } // CW steps is 0 to 199
    if(CWsteps>100){
        while(desired!=Pos){
            CCW();
        }
    }
    else{
        while(desired!=Pos){
            CW();
        }
    }
}
```

Concluding Remarks

- **Lots of types of electrical motors**
 - **stepper & DC are most common in inexpensive ES's**
- **Beware when driving inductive loads**
 - **back EMF has to be controlled**
 - » **snub diode is cheap**
 - » **optical isolation is even more secure**
- **5780 students**
 - **lab 9 will get you provide an introduction**
 - **stepper motor kits available for checkout**