



Problem 1 – (20 points)

Solution

Assume all diodes are identical and have $V_{D0}=0.7V$, $n=5$, and $V_T=25mV$. Use the **constant voltage drop** method. Verify that your assumption for the diode operation(i.e. on or off) are correct. Find the following making sure you find the correct operation of the diodes.

- State your assumptions (diode is on/off).
- The current I_{D1}
- The current I_{D2}
- The current I_{D3}
- The voltage V_o
- Verification to prove your assumptions for the diodes are correct.
- If there is noise on the $+10V$ supply of $\pm 1V$, what is the total value for I_{D1} (the AC current through diode, D1).
{Hint: remember to use the AC model for the diode}

Assume D1, D2 on, D3 off:

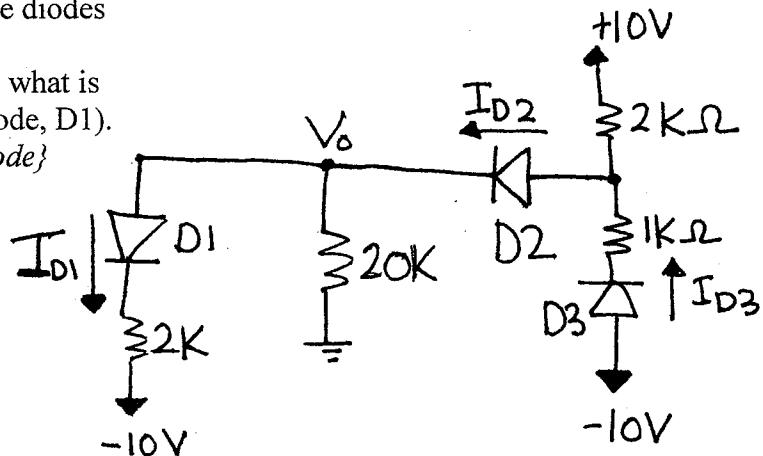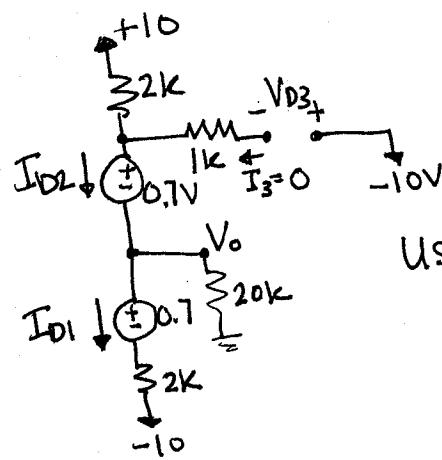

Using node voltage:

$$\frac{V_o}{20k} + \frac{V_o - 0.7 + 10}{2k} + \frac{V_o + (0.7) - 10}{2k} = 0$$

$$V_o \left(\frac{1}{20k} + \frac{1}{2k} + \frac{1}{2k} \right) = 0 \quad \therefore V_o = 0$$


$$I_{D2} = I_{D3} = \frac{10 - 0.7}{2k} = \frac{9.3}{2k} = 4.65mA \quad , \quad I_{D3} = 0A$$

check: $I_{D2}, I_{D3} > 0$ ✓

$$V\text{-loop with } V_{D3}: +V_o + 0.7 + V_{D3} + 10 = 0$$

$$V_{D3} = -10.7V < 0.7 \quad \therefore \underline{\text{off}} \quad \checkmark$$

g) AC:

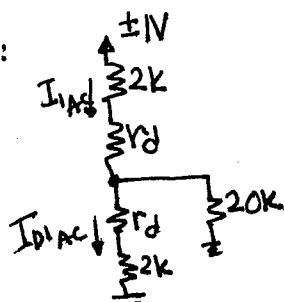

$$I_{D1AC} = \frac{\pm 1V}{2k + r_d + 20k \parallel (2k + r_d)} \quad \text{where} \quad r_d = \frac{nV_T}{I_D} = \frac{5(25m)}{4.65m} \approx 27\Omega$$

$$I_{D1AC} \approx \pm 259\mu A$$

$$I_{D1AC} = \pm \frac{259\mu A (20k)}{22.027k} \approx \pm 235\mu A$$

$$I_{D1} = 4.65mA \pm 235\mu A$$

Problem 2 – (30 points)

- a) Sketch the Bode (both magnitude & phase) plot for: {label as many y values as possible for both magnitude and phase and/or each slope along with showing all your work}

$$H(s) = \frac{-100k \cdot (s+10)}{(s+100) \cdot (s+1k)}$$

- b) What is the estimated or actual magnitude value at $\omega=200$ rad/sec (in dB):

$$+40\text{dB} \text{ (from graph)} \quad \text{or} \quad 10 \cdot \sqrt{\left(\frac{200}{10}\right)^2 + 1^2} \\ \sqrt{\left(\frac{200}{100}\right)^2 + 1^2} \cdot \sqrt{\left(\frac{200}{1k}\right)^2 + 1^2} \approx 40\text{dB}$$

- c) What range of frequency will this circuit operate correctly:

up to $10 \frac{\text{rad}}{\text{sec}}$ and 100 to $1k \frac{\text{rad}}{\text{sec}}$

standard form:

$$\frac{-100k(10)\left(\frac{s}{10} + 1\right)}{100 \cdot 1k \cdot \left(\frac{s}{100} + 1\right)\left(\frac{s}{1k} + 1\right)} = \frac{-10\left(\frac{s}{10} + 1\right)}{\left(\frac{s}{100} + 1\right)\left(\frac{s}{1k} + 1\right)}$$

only effects phase (180°) not magnitude

zero at $\omega=10$: $+20\text{dB/dec}$ starting at $\omega=10$

magnitude phase
 $1 < \omega < 100$ $+45^\circ \text{slope/dec}$

pole at $\omega=100$: -20dB/dec " " $\omega=100$

$10 < \omega < 1k$ $-45^\circ \text{slope/dec}$

pole at $\omega=1k$: -20dB/dec " " $\omega=1k$

$100 < \omega$ $-45^\circ \text{slope/dec}$



magnitude: at $\omega=1$:

$$\frac{10 \cdot \sqrt{\left(\frac{1}{10}\right)^2 + 1^2}}{\left(\sqrt{\left(\frac{1}{100}\right)^2 + 1^2}\right)\left(\sqrt{\left(\frac{1}{1k}\right)^2 + 1^2}\right)} = 10 \frac{\text{V}}{\text{V}} \text{ or } 20 \log(10) \\ 20\text{dB}$$

There is a flat line in magnitude until the first critical $f(\omega=10)$

phase: a flat line at 180° until first frequency range


$$H(s) = \frac{-100k \cdot (s + 10)}{(s + 100) \cdot (s + 1k)}$$

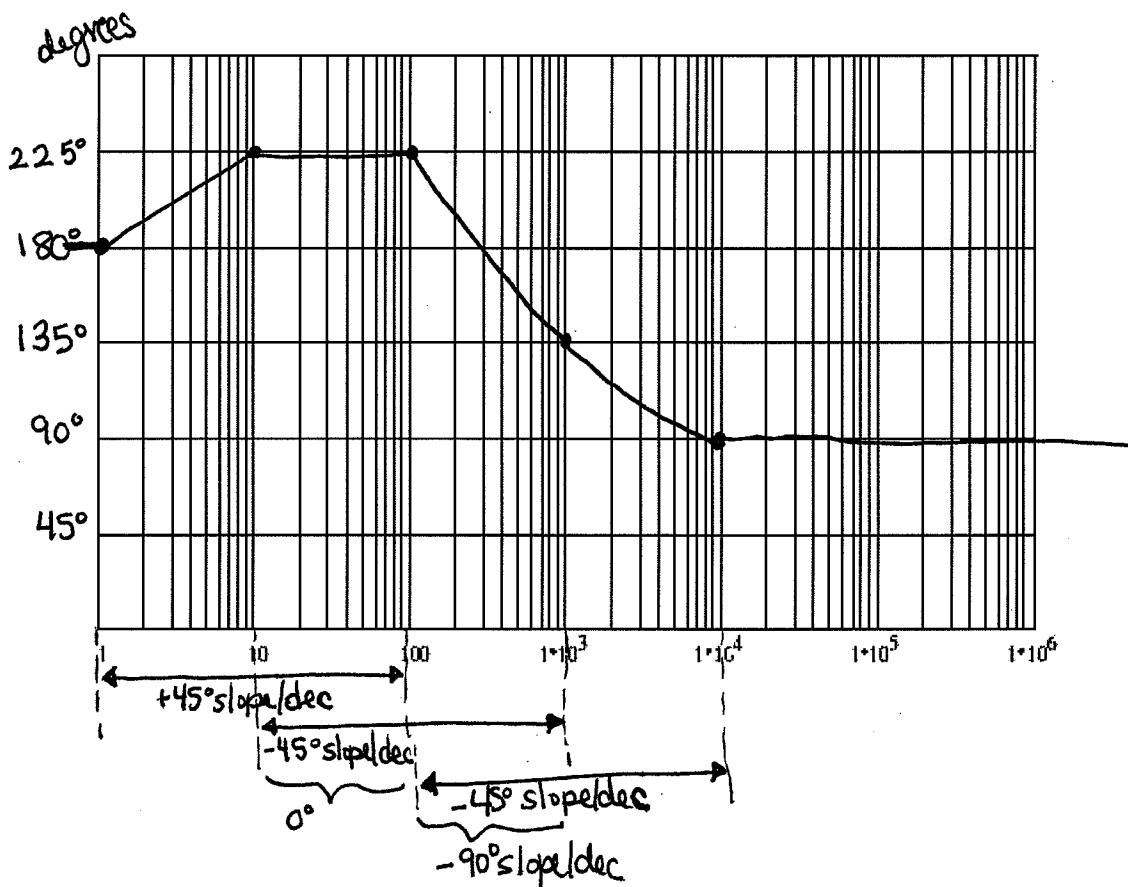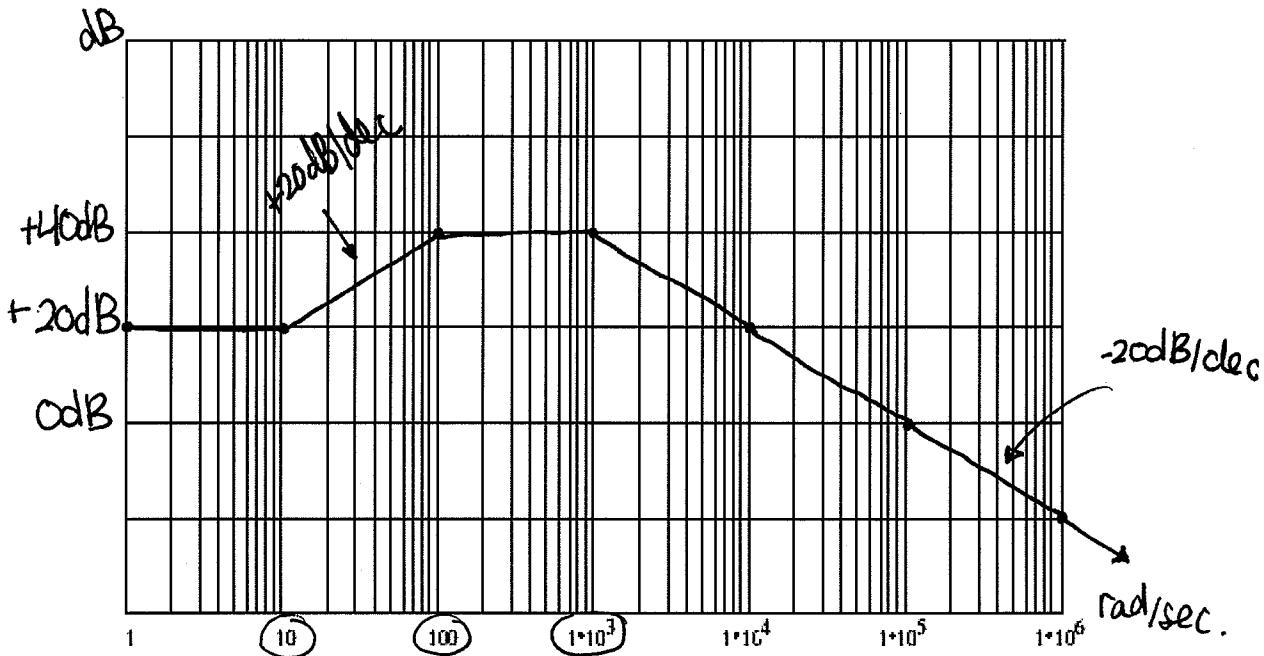

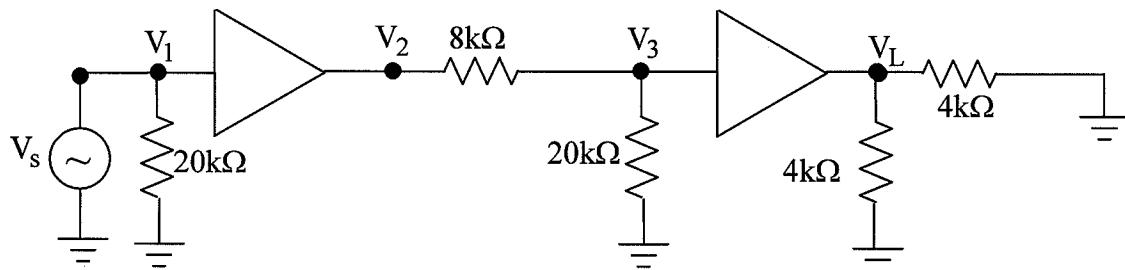
Problem 3 – (30 points)

V_s is an AC signal. Assume linear operation for both amplifiers with only the following nonideal effects:

$$A_{vo} = 10, \quad R_{in} = 20\text{k}\Omega, \quad R_o = 2\text{k}\Omega \quad \text{power supplies} = \pm 12 \text{ V}$$



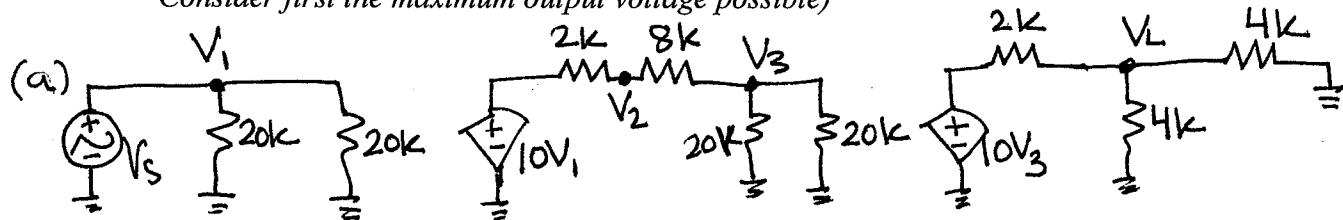- (a) Draw this 2 stage amplifier using the voltage amplifier model. Make sure to label V_s , V_1 , V_2 , V_3 , and V_L on the schematic.
- (b) Find the voltage gain V_L/V_s without frequency dependence or amplifier imperfections.
- (c) What are the pole locations if both amplifiers are internally compensated with $f_T = 5\text{MHz}$. (Hint: Find V_2/V_s and V_L/V_2)
- (d) What is the maximum amplitude for V_s considering the limits of a nonideal amplifier? (Hint: Consider first the maximum output voltage possible)



$$(b) V_L = \frac{10 \cdot V_3 (2\text{k})}{4\text{k}} = 5 \cdot V_3$$

$$V_3 = \frac{V_2 \cdot 10\text{k}}{18\text{k}} = \frac{5}{9} \cdot V_2$$

$$V_2 = \frac{10V_1 \cdot 18\text{k}}{20\text{k}} = 9 \cdot V_1$$

$$V_1 = V_s$$

$$V_L = 5 \cdot \frac{5}{9} \cdot 9 \cdot V_s$$

$$\boxed{\frac{V_L}{V_s} = 25 \frac{V}{V}}$$

(c) For first amplifier:

$$\frac{V_2}{V_s} = 9$$

$$f_{3dB} = \frac{5M}{9}$$

For second amplifier:

$$\frac{V_L}{V_2} = 5 \cdot \frac{5}{9} = \frac{25}{9}$$

$$f_{3dB} = \frac{5M \cdot 9}{25} = \frac{9}{5}M$$

overall transfer function:

$$\therefore \frac{9 \cdot \frac{25}{9}}{\left(\frac{jf}{5/9M} + 1\right) \cdot \left(\frac{jf}{9/5M} + 1\right)} = \boxed{\frac{25}{\left(\frac{9jf}{5M} + 1\right) \cdot \left(\frac{5jf}{9M} + 1\right)}}$$

(d) $V_{outmax} = +12$

$$\therefore V_{smax} = \frac{+12}{25} = \boxed{0.48V}$$

Problem 4 – (20 points)

You are given the following characteristics for a real amplifier:

Input offset voltage, $V_{ios} = 3\text{mV}$


Input Resistance, $R_i = 2\text{M}\Omega$

Unity-gain bandwidth, $f_T = 20\text{MHz}$

Output swing limits, within 2Volts of power supply

Slew Rate, $SR = 6 \frac{\text{V}}{\mu\text{sec}}$

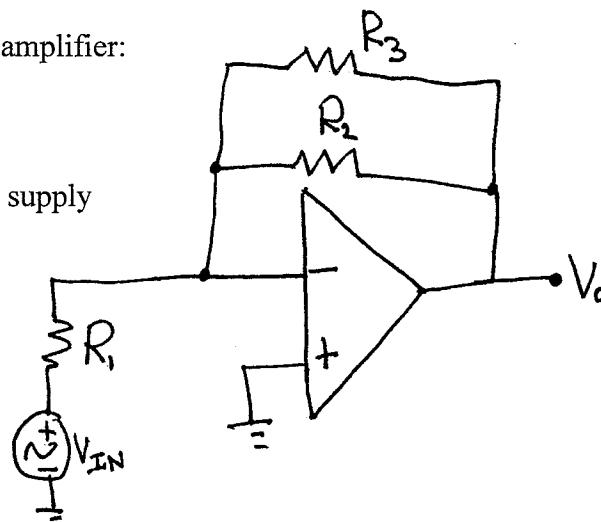The following circuit is powered at $\pm 15\text{V}$:



a) If $R_1 = 20\text{k}$ and $R_2 = R_3 = 100\text{k}$, what is the bandwidth of the circuit. Consider both the effect due to slew rate (use the maximum output value possible) compared to the effect due to the unity gain bandwidth.

b) For $V_{in} = 0.002\sin(2\pi 90kt)$, what is the PEAK(not peak to peak) value at the output considering the input offset voltage?

c) How should the circuit above be modified to minimize the effect of the input bias current? Draw the schematic of the modified circuit and state values of added component(s).

$$(a) R_2 \parallel R_3 = 50\text{k}$$

$$\text{inverting amp gain} = -\frac{50\text{k}}{20\text{k}} = -2.5\text{V/V}$$

$$f_{3dB} = \frac{20\text{M}}{2.5} = 8\text{MHz}$$

$$\text{SR effect: } f_{max} = \frac{SR}{2 \cdot V_p \cdot \pi} = \frac{6}{1 \times 10^6 \cdot 2 \cdot 13 \cdot \pi} = 73.5\text{kHz}$$

↑
bandwidth

$$(b) -5\text{m} \sin(2\pi 90kt) - 2.5(3\text{m})$$

$$\text{peak} \Rightarrow -7.5\text{m} + 5\text{m} = -2.5\text{mV}$$

(c)

