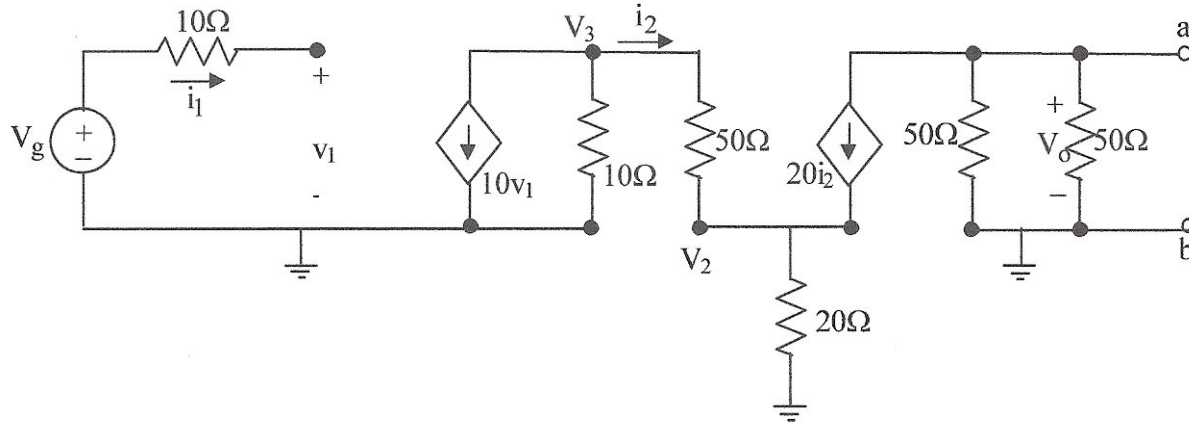


Homework #1:

1. Given $V_g=10mV$, find V_o . Find the Thevenin equivalent between terminals a-b.



2. Give expressions for the sine-wave voltage signals having:

- a. 5V peak amplitude and 1kHz frequency
- b. 120Vrms and 60Hz frequency
- c. 200mV peak-to-peak and 1000 rad/sec frequency
- d. 0.1V peak and 10ms period

3. Explain in your own words the procedural steps for plotting Bode Plots. (Note: I would prepare this question for use during an exam)

- 4. (a) Plug in values of ω from 0.1 to 10^5 rad/sec. Plot this graph of dB vs ω . (Convert Volts/Volts to dB)
- (b) Sketch the Bode plots using a straight-line approximation (procedures described in class)
- (c) Use Matlab to obtain the Bode Plot.
- (d) Compare the three. What differences do you see?

$$H(s) = \frac{10,000(s + 10)}{(s + 1,000)(s + 100)}$$

5. Sketch the Bode plot using a straight-line approximation (procedures described in class) and then use Matlab to obtain the Bode Plot. Compare the two.

$$H(s) = \frac{100s^2}{(s + 1)(s + 10)}$$

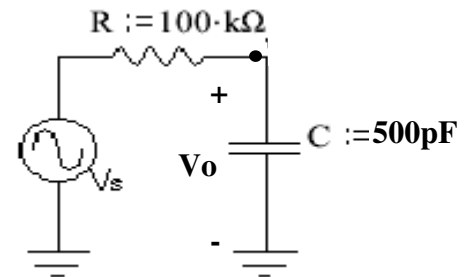


Fig. 1

6. Use PSPICE to simulate the circuit of Fig. 1 and determine the Bode Plots. Print out the schematic, along with the plots. (**Double points – counts as three homework problems**)

7. Analyze the following circuit to find the transfer function V_{out}/V_s . Solve the circuit symbolically first (with R_1, R_2, R_3, R_4, C) and then plug in their values. Create a rough sketch of the transfer function using a straight-line approximation procedure.

