
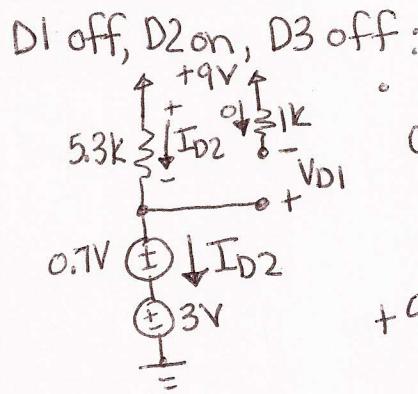


The material we have covered so far this semester is summarized (but NOT limited to) below:

1. Understand the difference between AC & DC signals.
2. Understand how to analyze circuit (with or without cap in it) to obtain transfer function.
3. Understand how to plot the Bode plots from an equation or circuit.
4. Amplifiers:
 - a) Understand how to apply Amplifier models (voltage, current, etc.) to multistage amplifiers
 - b) Analyze single input Amplifier (with model) for transfer function.
 - c) Analyze amplifier's gain in different configurations (inverting, noninverting, voltage follower)
 - d) Understand frequency response of amplifiers for single amplifiers
 - e) Compensation of real op-amp imperfections (Slew Rate, Clipping, Input bias currents, Voltage offset, frequency limitations, finite gain)
5. Diodes:
 - a) Analyze diode circuit using ideal model
 - b) Analyze diode circuit using constant voltage drop model
 - c) Analyze diode circuit with both DC and AC signals

1. (a) Find I_{D1} , I_{D2} , I_{D3} , and V_o using constant voltage drop method with $n=1$, $V_T=25mV$, and $V_{D0}=0.7V$.

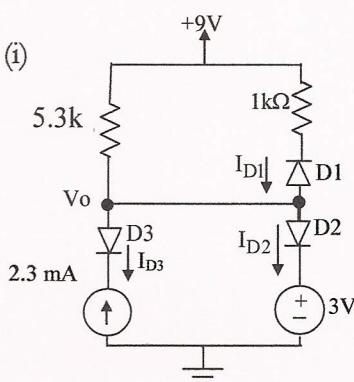(b) Find $V_{o\text{total}}$ if the 3V source has $0.5\sin(\omega t)$ noise.



D3 has to be off because current is not allowed to flow in that direction through the diode.

$$+9 - I_{D2}(5.3k) - 3.7 = 0$$

$$I_{D2} = \frac{(9-3.7)}{5.3k} = \frac{5.3}{5.3k} = 1\text{mA} \checkmark > 0$$

$\therefore D2 \text{ on}$


Check V_{D1} :

$$+3V + 0.7 - V_{D1} - 9 = 0$$


$$V_{D1} = -9 + 3 + 0.7 = -5.3 < 0.7$$

$\therefore D1 \text{ is off}$

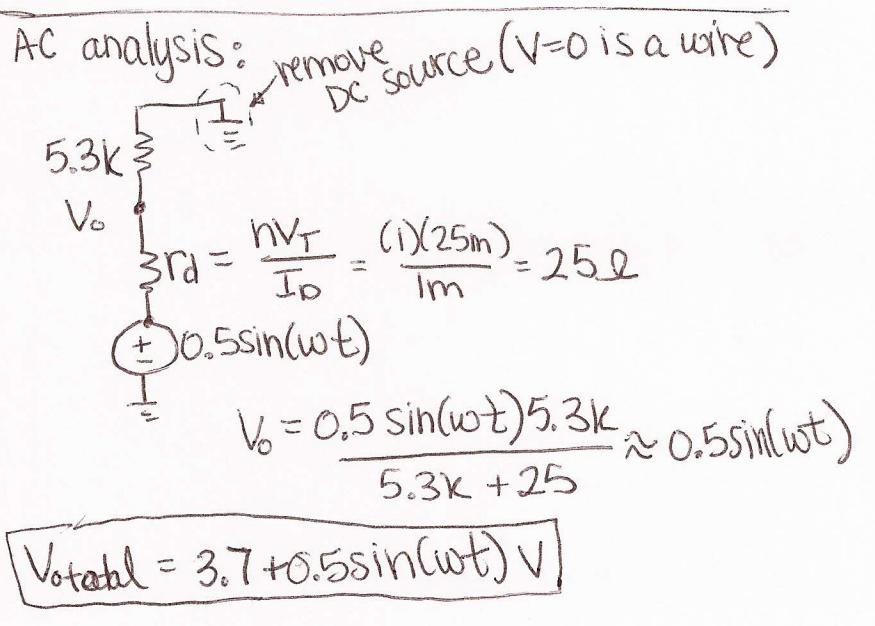$I_{D1} = 0$
$I_{D2} = 1\text{mA}$
$I_{D3} = 0$
$V_o = 3.7V$



(ii)

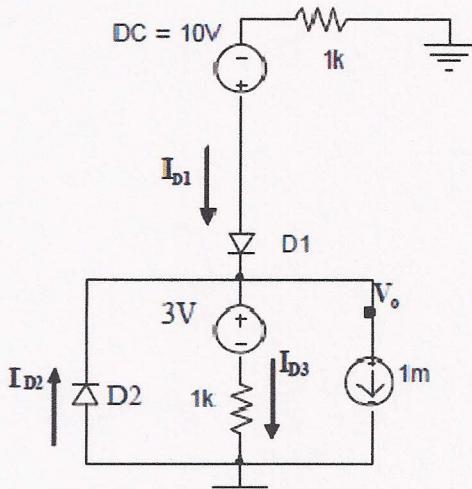

$$V_o = +3 + I_{D3}(1k)$$

V-loop:

$$-I_{D1}(1k) + 10 - 0.7 - 3 - I_{D3}(1k) = 0$$

 $\sum I:$

$$-I_{D1} + 1m + I_{D3} = 0$$

$$I_{D1} = (1m + I_{D3})$$

$$\therefore -(1m + I_{D3})(1k) + 6.3 - I_{D3}(1k) = 0$$

$$-1(-2k)I_{D3} + 6.3 = 0$$

$$I_{D3} = \frac{6.3}{2k} = 2.65m > 0$$

$$\therefore \underline{\text{D3 is on}} \Rightarrow V_o = 3 + 1k(2.65m)$$

$$V_o = 5.65V$$


Check V_{D2} :

$$-V_{D2} - 3 - I_{D3}(1k) = 0$$

$$V_{D2} = -3 - 1k(2.65m) = -5.65 < 0.7$$


D2 is off
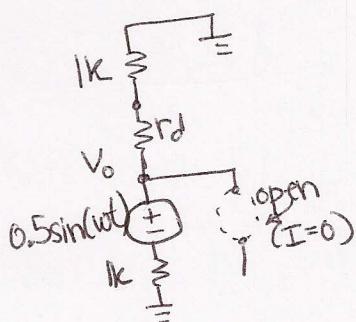
$$\text{AC analysis: } r_d = \frac{hVI}{ID_3} = \frac{(1)(25m)}{2.65m} = 9.4\Omega$$



$$V_{oAC} = \frac{0.5\sin(\omega t)(1k + r_d)}{(1k + r_d) + 1k} \approx 0.25\sin(\omega t)$$
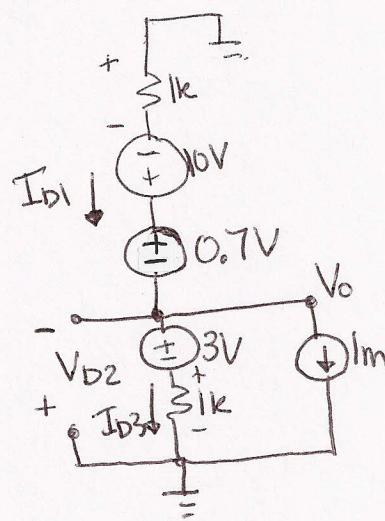
$$V_{ototal} = 5.65 + 0.25\sin(\omega t)$$



OR use node-voltage

$$\frac{V_o - 3}{1k} + 1m + \frac{-(10 - 0.7) + V_o}{1k} = 0$$

$$V_o \left(\frac{1}{1k} + \frac{1}{1k} \right) = 3m - 1m + 9.3m$$

$$\therefore V_o = \frac{11.3m}{\frac{1}{1k} + \frac{1}{1k}} = 5.65V$$

$$I_{D3}(1k) + 3 - V_o = 0$$

$$I_{D3} = \frac{V_o - 3}{1k} = \frac{2.65}{1k} = 2.65m$$

$$I_{D1} = 1m + 2.65m = 3.65m$$

$$I_{D2} = 0$$

$$I_{D3} = 2.65m$$

$$V_o = 5.65V$$

2. Sketch Bode Plots for (a) $H(s) = \frac{-1 \times 10^{14}(s^2)}{(s+10k)^2(s+100k)}$ \Rightarrow Standard Form: $\frac{-1 \times 10^{14}(s^2)}{(10k)^2\left(\frac{s}{10k}+1\right)^2(100k)\left(\frac{s}{100k}+1\right)}$

critical frequencies: origin($\times 2$), $10k(\times 2)$, $100k$


at $w=1$: $\frac{-1 \times 10^{14}(1)}{(10k)^2(100k)\left(\sqrt{\frac{1}{10k}+1}\right)^2\left(\frac{1}{100k}+1\right)} = 10^{\sqrt{2}} \Rightarrow 20 \log(10) = \underline{20 \text{dB}}$

magnitude:


2 at origin	zeroes	+2 (+20dB/decade)
$10k(\times 2)$	pole	$2(-20 \text{dB/decade})$
$100k$	pole	-20dB/decade

phase:

(-) sign starts phase at $\pm 180^\circ$		
2 at origin	zeroes	$2(+90) = +180^\circ$
$10k < w < 100k$	pole	$< -45^\circ / \text{decade} \times 2$
$100k < w < 1 \text{ Meg}$	pole	-45°/decade


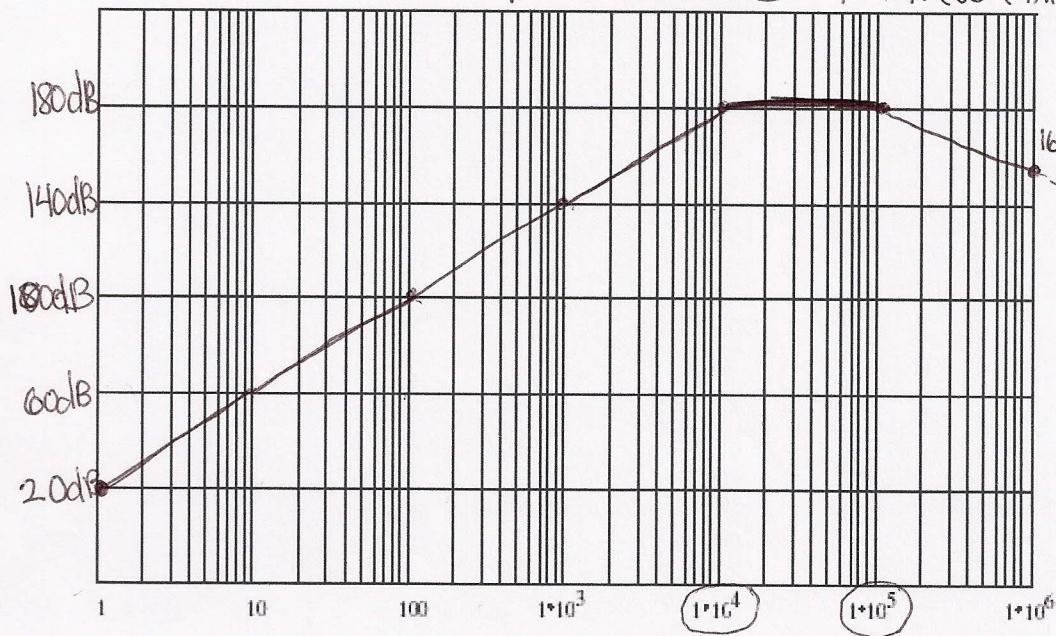


Bandwidth is from
10k to 100k

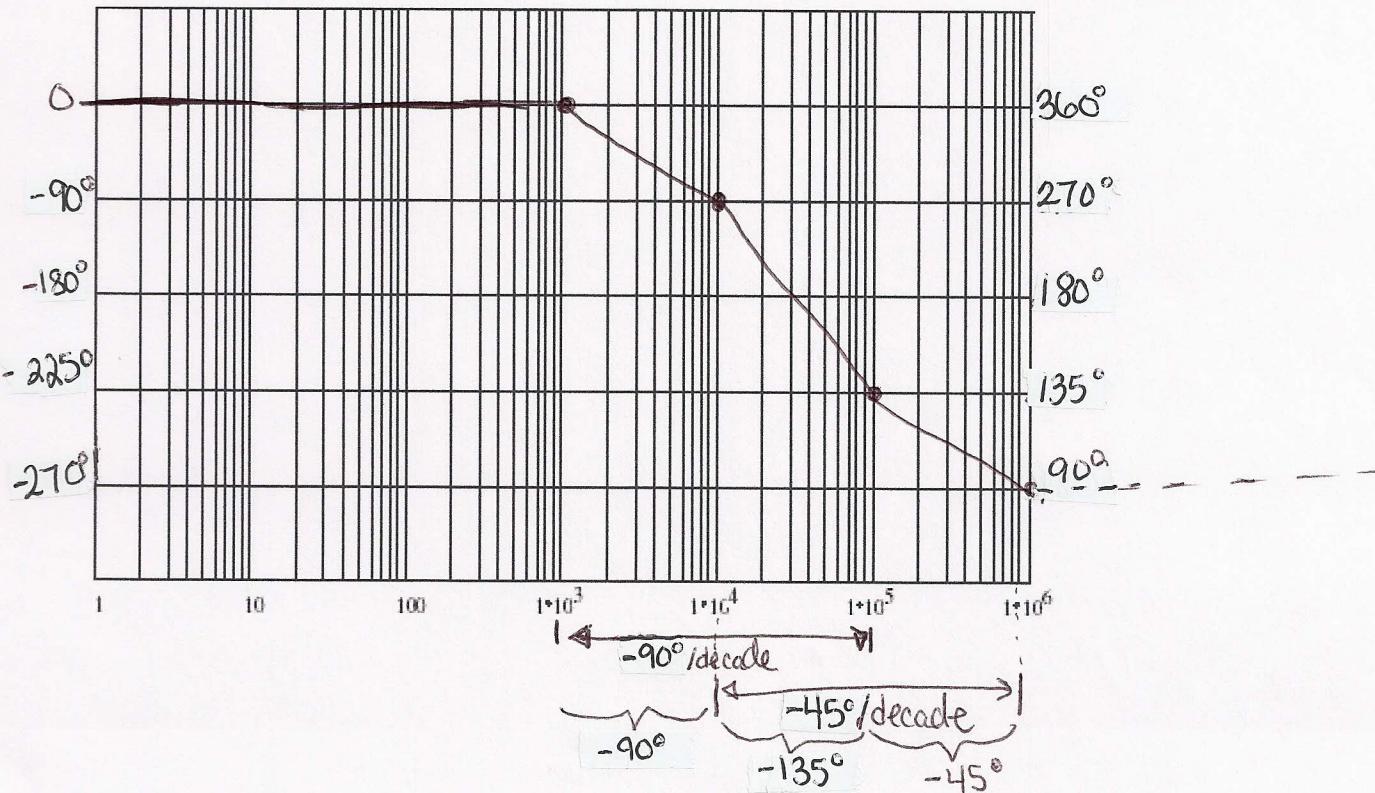

$$4. b \quad H(s) = \frac{10k(10)(\frac{s}{10} + 1)}{1k(\frac{s}{1k} + 1)(100)(\frac{s}{100} + 1)} = \frac{(\frac{s}{10} + 1)}{(\frac{s}{1k} + 1)(\frac{s}{100} + 1)}$$



Break freq: $\omega = 10, 100, 1k$

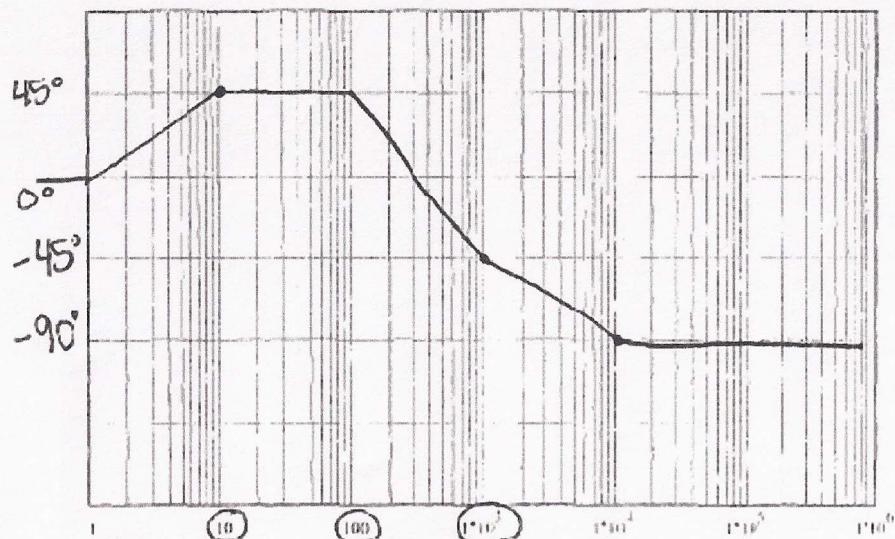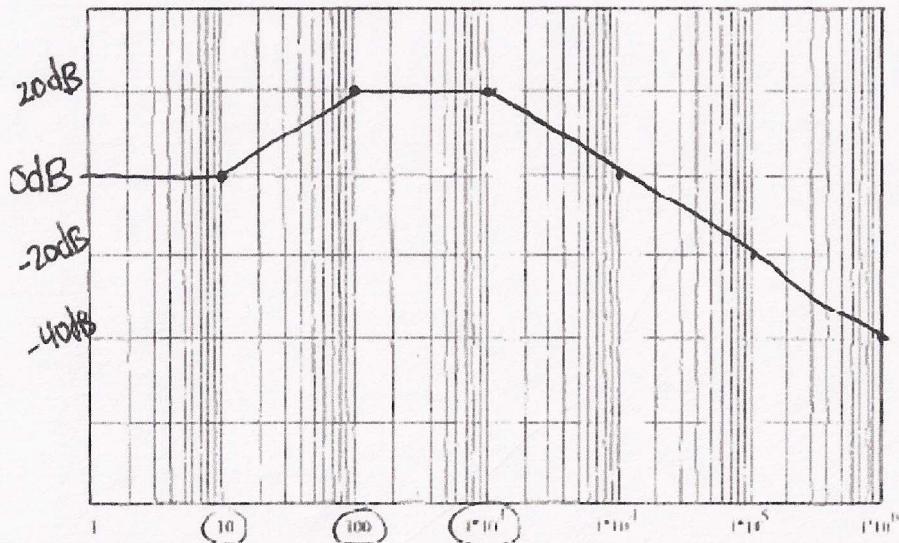


$$5. H(s) = \frac{100s^2}{(s+1)(10)(\frac{s}{10} + 1)} = \frac{10s^2}{(s+1)(\frac{s}{10} + 1)}$$

Break freq: $\omega = 1, 10$

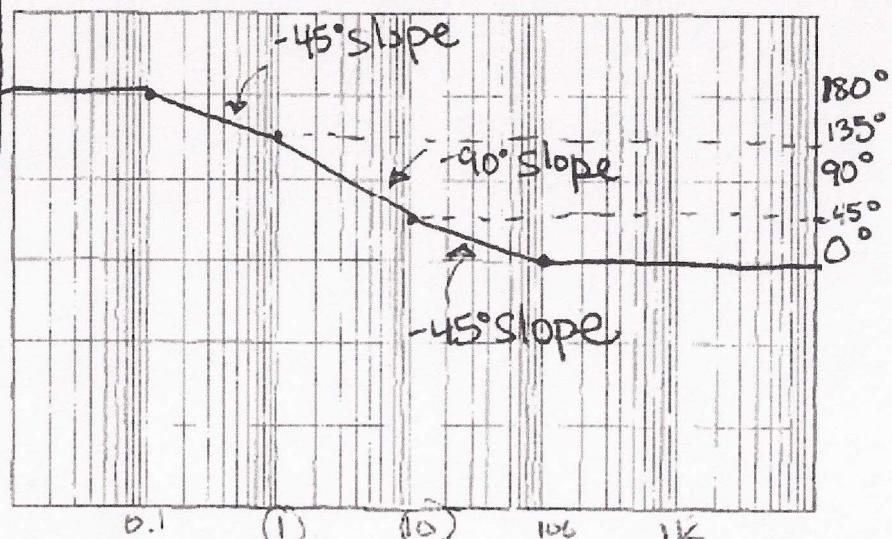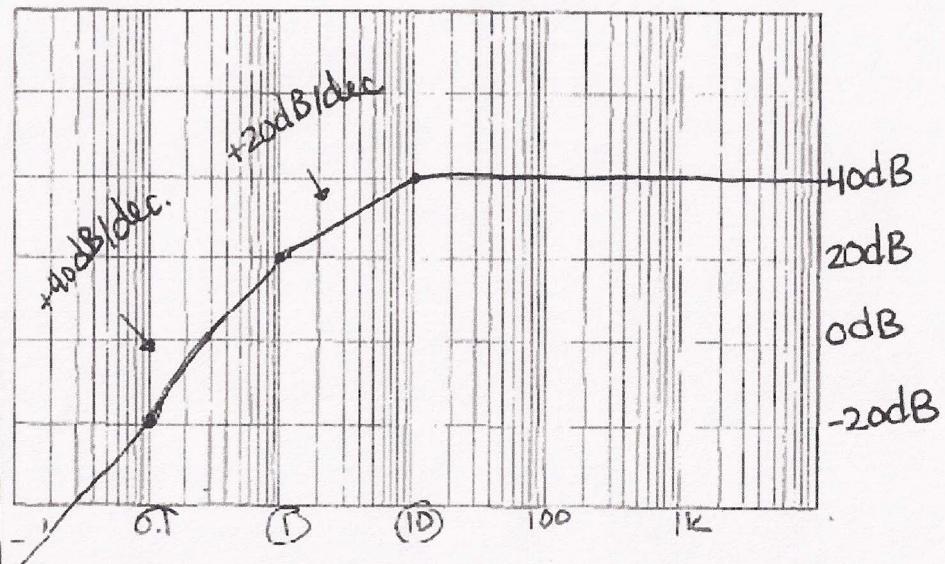phase starts at 180°
slope starts at +40dB/dec.
 $\Rightarrow \omega=1 \Rightarrow 20 \log(10) = 20 \text{dB}$



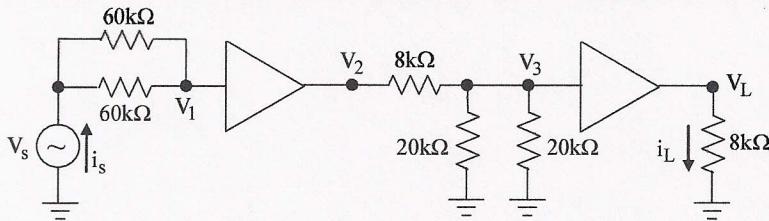3. (a) Use voltage amplifier model to find voltage gain. $A_{vo}=20$, $R_i=10k\Omega$, $R_o=2k\Omega$.



whole number

a) $30k = (60k \parallel 60k)$

V_s $\xrightarrow{i_s}$ $V_1 \xrightarrow{10k} 20V_1$ $V_2 \xrightarrow{2k} 8k$ $V_3 \xrightarrow{10k} 10k$ $V_L \xrightarrow{2k} 8k$


b) $V_L = \frac{8k \cdot 20V_3}{10k} = \frac{4}{5} \cdot 20V_3$ $\frac{V_L}{V_s} = \left(\frac{4}{5}\right)(20)\left(\frac{1}{3}\right)(20)\left(\frac{1}{4}\right)$

$V_3 = \frac{5k \cdot 20V_1}{5k+10k} = \frac{1}{3} \cdot 20V_1$ $\frac{V_L}{V_s} = \frac{4}{3}(20) = \boxed{\frac{80V}{3}/V \approx 29dB}$

$V_1 = \frac{V_s \cdot 10k}{40k} = \frac{1}{4} \cdot V_s$

(b)

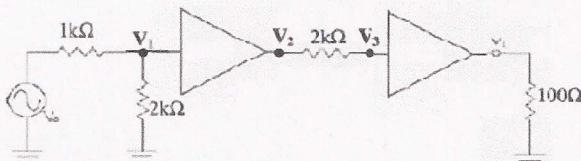
- Both amplifiers have the following characteristics:
 $A_{vo}=40$ $R_i=2k\Omega$ $R_o=4k\Omega$ Clipping levels: $L=\pm 12V$ (unloaded)



- (a) Redraw this 2 stage amplifier using the amplifier model. Make sure to label V_1 , V_2 , V_3 , and V_L on the schematic.

(b) Find $A_v = \frac{V_L}{V_s}$. Express your answer as a ratio(V/V) and in dB. [Round the answer to a whole number]

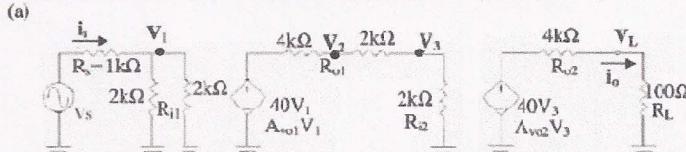- (c) For the input $V_s = \sin(\omega t)$. State the maximum output value at V_L .



(b) Find $A_v = \frac{V_L}{V_s}$. Express your answer as a ratio(V/V) and in dB. [Round to a whole number]

$$\frac{V_L}{V_s} = A_v = \left(\frac{R_{i1}}{R_s + R_{i1}} \right) \cdot A_{v1} \cdot \left(\frac{R_{o1}}{R_{o1} + R_{i2}} \right) \cdot A_{v2} \cdot \left(\frac{R_L}{R_{o2} + R_L} \right)$$

$$R_{i1} = \frac{1}{\frac{1}{2k} + \frac{1}{2k}} = 1k \quad R_{o1} = 4k + 2k - 6k$$

$$A_{v1} = \frac{1k \cdot 40 - 2k \cdot 40}{1k - 1k} = 4878 \quad (\text{rounded } = 5V/V \text{ or } 20 \log(4878) = 13.970)$$

$$(c) \text{Amplitude} \Rightarrow \text{maximum output will be the peak value: } \text{gain} = V_L/V_s = 5V/V \quad V_L = 5 \cdot V_{s_peak} = \pm 5V$$

Checking for clipping $\Rightarrow \frac{V_2}{V_s} = \frac{40 \cdot (1k)}{2k} = \frac{4k}{8k} = 0.5V < \pm 2V$
 \rightarrow No clipping at 1st amp
if $V_s = 1V_{max}$.

4 (a) You are given the following characteristics for a real amplifier:

Input offset voltage, $V_{ios} = 4 \text{ mV}$

Input offset current, $I_{ios} = 100 \text{nA}$

Input bias current, $I_{ib} = 1 \mu\text{A}$

Input Resistance, $R_i = 1 \text{ M}\Omega$

Output Resistance, $R_o = 50 \Omega$


Open-loop gain, $A_{vo} = 180 \text{ dB}$

Unity-gain bandwidth, $f_T = 11 \text{ MHz}$

Output swing limits, within 2 Volts of supply

Settling Rate, $SR = 2^{\frac{V}{V}}/\mu\text{sec.}$

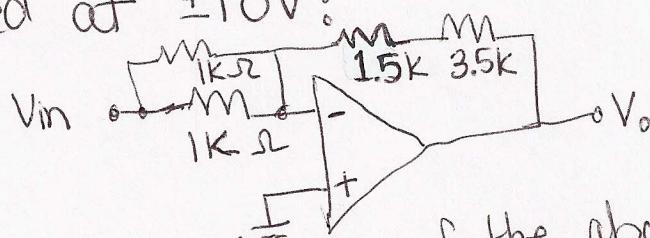Given the following circuit with the operational amplifier powered at $\pm 10 \text{ V}$:



i) Find the ideal gain of the above circuit:

$$\frac{V_o}{V_{in}} = \frac{-5k}{500} = -10^{\frac{V}{V}} \Rightarrow 20 \text{ dB}$$


ii) For small input signals, what is the bandwidth of the circuit?

$$f_{3dBnew} = \frac{11 \text{ MHz}}{1 + (10)} = \underline{1 \text{ MHz}}$$

iii) If a circuit needs to operate up to 5 MHz, what is the maximum gain I can achieve using an inverting amplifier configuration?

$$f_{3dBnew} = 5 \text{ MHz} = \frac{11 \text{ MHz}}{(1 + \frac{R_2}{R_1})} \Rightarrow \left| \frac{R_2}{R_1} \right| = \frac{11}{5} - 1 = \underline{1.2 \frac{V}{V}}$$

4. (cont)

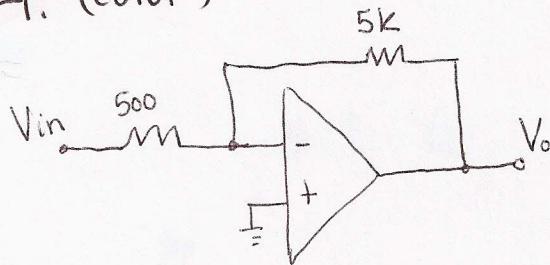

- iv) If the above circuit is operated to produce the maximum possible peak voltage
a) what is the bandwidth?
b) what is the maximum peak voltage value for the input?

$$a) f_{max} = \frac{SR}{V_p \cdot 2 \cdot \pi} = \frac{2}{1 \times 10^6 \times (8)(2)\pi} = 39.8 \text{ KHz}$$

b) maximum peak voltage = +8V output max.


Using ideal gain = -10 V/V

$$\left| \frac{V_o}{V_{in}} \right| = +10 \Rightarrow V_{in} = \frac{V_o}{10} = \frac{8}{10} = 0.8 \text{ V max}$$

- v) Find the effect of the input offset voltage when $V_{in}=0V$.

$$V_{out} = 4m(-10) = -40 \text{ mV}$$

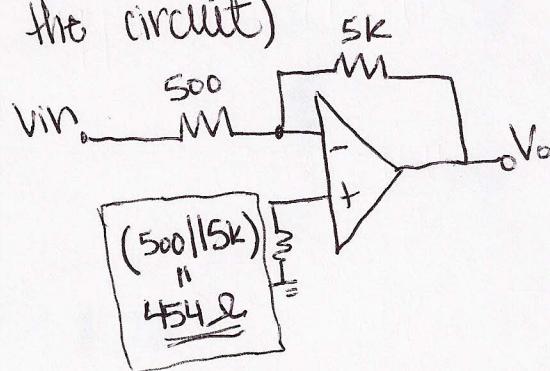- vi) How should the circuit above be modified to minimize the effect of the input bias current?
(Draw the circuit)



4. (b) You are given the following characteristics for a real amplifier:

Input offset voltage,	$V_{ios}=3\text{mV}$
Input offset current,	$I_{ios}=100\text{nA}$
Input bias current,	$I_{ib}=1\mu\text{A}$
Input Resistance,	$R_i=1\text{M}\Omega$
Output Resistance,	$R_o=50\Omega$
Open-loop gain,	$A_{vo}=180\text{dB}$
Unity-gain bandwidth,	$f_t=15\text{MHz}$
Output swing limits,	within 2Volts of power supply
Slew Rate,	$\text{SR}=4 \frac{\text{V}}{\mu\text{sec}}$

If a circuit needs to operate at 5MHz using the above specifications for an operational amplifier and having a power supply of $\pm 15\text{V}$, what is the maximum gain that can be achieved using an:


- i) Inverting amplifier

$$f_{3\text{dB}_{\text{new}}} = \frac{15 \times 10^6}{\left(1 + \frac{R_2}{R_1}\right)} = 5\text{MHz} \Rightarrow -\frac{R_2}{R_1} = -\left(\frac{15 \times 10^6}{5 \times 10^6} - 1\right) = -2 \frac{\text{V}}{\text{V}}$$

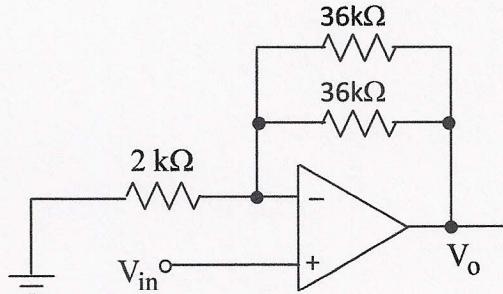- ii) Non-inverting amplifier

$$f_{3\text{dB}_{\text{new}}} = \frac{15 \times 10^6}{\left(1 + \frac{R_2}{R_1}\right)} = 5\text{MHz} \Rightarrow \left(1 + \frac{R_2}{R_1}\right) = \frac{15 \times 10^6}{5 \times 10^6} = 3 \frac{\text{V}}{\text{V}}$$

Given the following circuit with the operational amplifier powered at $\pm 15\text{V}$.



- i) Find the ideal gain of the above circuit:

$$\frac{V_o}{V_{in}} = \left(1 + \frac{18k}{2k}\right) = 10 \frac{\text{V}}{\text{V}}$$

- ii) For small input signals, what is the bandwidth of the circuit

$$f_{3\text{dB}_{\text{new}}} = \frac{15 \times 10^6}{10} = 1.5\text{MHz}$$

- iii) What is the bandwidth when the circuit is operated to produce the maximum possible peak voltage value?

$$f = \frac{4}{10^{-6}(13 \cdot \pi)} = 98\text{kHz}$$

- iv) What is the maximum amplitude of the input ?


$$\frac{V_o}{V_{in}} = 10 \frac{\text{V}}{\text{V}} \Rightarrow V_{in} = \frac{V_o}{10} = \frac{13}{10} = 1.3\text{V}$$

- v) For $V_{in}=0.001\sin(2\pi 90kt)$, what is the ideal value for the peak to peak voltage value at the output?

$$V_{o_{pp}} = 2(0.001)(10) = 0.02\text{V}_{pp}$$

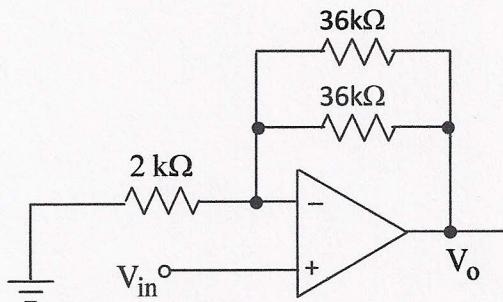- vi) For $V_{in}=0.001\sin(2\pi 90kt)$, what is the peak to peak voltage value at the output considering the input offset voltage?

$$V_{o_{pp}} = 2(0.001)(10) + 3m(10) = .02 + .030 = .05\text{V}_{pp}$$



- vii) How should the circuit above be modified to minimize the effect of the input bias current? Draw the schematic of the modified circuit and state values of added component(s).

