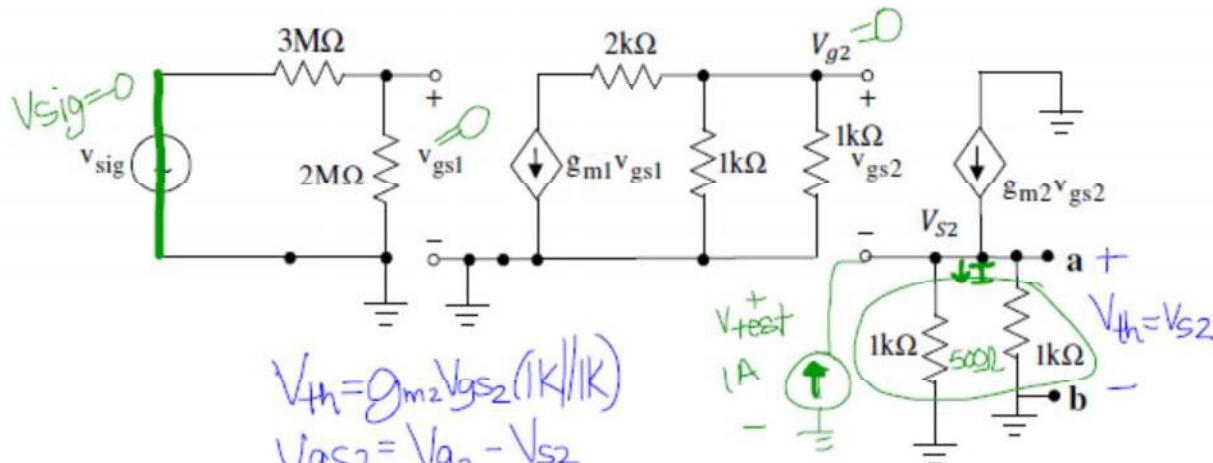


2. Find the Thevenin equivalent(V_{th} and R_{th}) between a-b. (Note: $v_{gs2} = V_{g2} - V_{S2}$) Assume that gm_1 and gm_2 are known values.




$$V_{th} = g_{m2} V_{gs2} \left(\frac{1}{k} \parallel \frac{1}{k} \right)$$

$$V_{gs2} = V_{g2} - V_{S2}$$

$$V_{g2} = -\frac{g_{m1} V_{gs1} \left(\frac{1}{k} \right) \left(\frac{1}{k} \right)}{2k} \rightarrow V_{gs2} = -g_{m1} V_{gs1} (500) - g_{m2} V_{gs2} 500$$

$$V_{gs1} = \frac{2M}{5M} V_{sig}$$
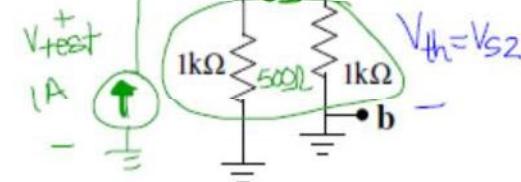
$$V_{th} = \frac{g_{m2} 500 (g_{m1} 500)}{(1 + g_{m2} 500)} \cdot \frac{2}{5}$$



$$V_{gs2} (1 + g_{m2} 500) = -g_{m1} V_{gs1} 500$$

$$V_{gs2} = -\frac{g_{m1} V_{gs1} 500}{(1 + g_{m2} 500)}$$

$$R_{th} = \frac{V_{test}}{I}$$

$$V_{test} = I (500)$$

$$-I + 1A + g_{m2} V_{gs2} = 0$$

$$V_{gs2} = V_{g2} - V_{S2}$$

$$V_{gs2} = 0 - V_{test}$$

$$I = 1 - g_{m2} V_{test}$$

$$V_{test} = 500 - g_{m2} V_{test} 500$$

$$V_{test} (1 + g_{m2} 500) = 500$$

$$V_{test} = \frac{500}{1 + g_{m2} 500}$$

$$R_{th} = \frac{500}{1 + g_{m2} 500}$$

$$R_{th} = \frac{1}{g_{m2} \parallel 500}$$