



Find V_0 :

$$V_0 = -3i_2 (20\Omega)$$

$$i_2 = -5v_1$$

$$v_1 = V_g - (5v_1 \cdot 3\Omega)$$

$$v_1 = \frac{1}{16} V_g$$

$$i_2 = -\frac{5}{16} V_g$$

$$V_0 = \frac{75}{4} V_g = 18.75 V_g$$

Thevenin's Equivalent:

$$V_{th} = \text{open circuit voltage} = V_0 = 18.75 V_g$$

$$R_{th} = 20\Omega \text{ because with } V_g \text{ off } i_2 = i_3 = 0 \text{ A}$$

leaving the only path between terminals a and b as the 20Ω resistor shown.