

# Partial Logic Synthesis

## *Synthesis of ECO & Rectification Functions*

**Priyank Kalla**



Professor

Electrical and Computer Engineering, University of Utah

kalla@ece.utah.edu

<http://www.ece.utah.edu/~kalla>


# Problem Description

- Given: *Spec* function  $f$  or a gate-level circuit  $C_1$
- Given: Implementation *Impl* function  $g$  or a gate-level circuit  $C_2$
- Suppose  $Spec \neq Impl$ , i.e. Equivalence checking between  $C_1, C_2$  generates a counter-example
- We have to rectify  $C_2$  to match the *Spec*, but do not resynthesize the whole circuit  $C_2$ 
  - Perform *single-fix* or *multi-fix* rectification
  - Identify a set of nets  $\{x_i\}$  in  $C_2$  where rectification can be applied
  - Compute a rectification function  $U$ , replace  $x_i = U$ , such that  $C_1 \equiv C_2$

# The Scenario

- Compute rectification patches for buggy implementations  $C_2$
- Compute rectification patches for Engineering Change Orders (ECO)
  - Suppose, given  $C_1$  *Spec* and correct *Impl*  $C_2$
  - Make slight modifications on  $C_1$ : small change in functionality
  - New  $C_1 \neq C_2$  (bug!)
  - Minimally modify  $C_2$  to match the *Spec*
- Topologically constrained logic synthesis, synthesize subcircuits partially

# The Scenario: Miter Model

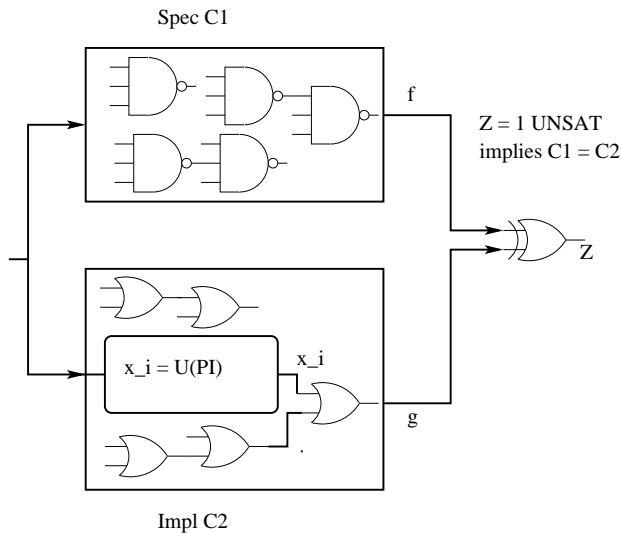

# Single-Fix Rectification

- Irrespective of the type of bugs, or the number of error inputs (counter-examples) ...
- Does there exist a net  $x_i$  and a Boolean function  $U(X_{PI})$ , s.t.  $x_i = U(X_{PI})$  makes  $C_1 \equiv C_2$ ?
- Mathematically, a Quantified Boolean Formula:
  - $\exists U, \forall X_{PI} \ C_1 \equiv C_2$  is SAT
- Single-fix rectification may or may not exist
- Multi-fix: Find  $x_1 = U_1, x_2 = U_2, \dots, x_t = U_t$ , s.t.  $C_1 \equiv C_2$

# Single-Fix Rectification

The Problem is three-fold:

- Once  $C_1$  does not match  $C_2$
- Identify a net  $x_i$  where single-fix rectification is admissible. So how to pick the net  $x_i$ ? (Discuss later...)
- How to ascertain that there exists a single-fix rectification function  $x_i = U(X_{PI})$ ? (Decision procedure)
- If single-fix exists at  $x_i$ , find the Boolean function  $U$ . (Quantification procedure).

## Theorem (Existence of Single-fix rectification at net $x_i$ (Thm. 1))

Given the Spec circuit  $C_1$  with function  $f$  and Impl circuit  $C_2$  with function  $g$ , where  $X$  is the set of primary inputs,  $f \neq g$ , and a net  $x_i \in C_2$ , the circuit  $C_2$  can be single-fix rectified at  $x_i$  with function  $x_i = U(X_{PI})$ , **if and only if**

$$[f(X) \oplus g(X, x_i = 0)] \wedge [f(X) \oplus g(X, x_i = 1)] = \perp \text{ (UNSAT)}$$
$$M(X, x_i = 0) \wedge M(X, x_i = 1) = \perp$$

## Existence of Single-fix at net $x_i$

### Theorem (Existence of Single-fix rectification at net $x_i$ (Thm. 1))

Given the Spec circuit  $C_1$  with function  $f$  and Impl circuit  $C_2$  with function  $g$ , where  $X$  is the set of primary inputs,  $f \neq g$ , and a net  $x_i \in C_2$ , the circuit  $C_2$  can be single-fix rectified at  $x_i$  with function  $x_i = U(X_{PI})$ , **if and only if**

$$[f(X) \oplus g(X, x_i = 0)] \wedge [f(X) \oplus g(X, x_i = 1)] = \perp \text{ (UNSAT)}$$
$$M(X, x_i = 0) \wedge M(X, x_i = 1) = \perp$$

What are  $[f(X) \oplus g(X, x_i = 0)]$  and  $[f(X) \oplus g(X, x_i = 1)]$ ?



## Theorem (Existence of Single-fix rectification at net $x_i$ (Thm. 1))

Given the Spec circuit  $C_1$  with function  $f$  and Impl circuit  $C_2$  with function  $g$ , where  $X$  is the set of primary inputs,  $f \neq g$ , and a net  $x_i \in C_2$ , the circuit  $C_2$  can be single-fix rectified at  $x_i$  with function  $x_i = U(X_{PI})$ , **if and only if**

$$[f(X) \oplus g(X, x_i = 0)] \wedge [f(X) \oplus g(X, x_i = 1)] = \perp \text{ (UNSAT)}$$
$$M(X, x_i = 0) \wedge M(X, x_i = 1) = \perp$$

What are  $[f(X) \oplus g(X, x_i = 0)]$  and  $[f(X) \oplus g(X, x_i = 1)]$ ?


The set of all test vectors for  $x_i$  stuck-at-0, and  $x_i$  stuck-at-1, resp. In other words,  $[f(X) \oplus g(X, x_i = 0)] =$  primary input assignments to  $X$  (minterms) that differentiate  $f(X)$  from  $g(X, x_i = 0)$ .

# Single-Fix Rectification Test

- $M(X, x_i = 0) \wedge M(X, x_i = 1) = \perp$  means that **product of positive and negative co-factors** of the miter w.r.t.  $x_i$  is empty.
- If  $M(X, x_i = 0) \wedge M(X, x_i = 1) \neq 0$ , then: there exists a minterm  $X$  s.t. the difference between *Spec* and *Impl* is observed for both values of target net  $x_i$
- Equivalently, if  $M(X, x_i = 0) \wedge M(X, x_i = 1) \neq 0$ , no matter what value  $x_i$  takes for this minterm  $X$ , functional difference between *Spec* and *Impl* remains.
- In other words, rectification is only feasible when  $M(X, x_i = 0) \wedge M(X, x_i = 1) = 0$ .
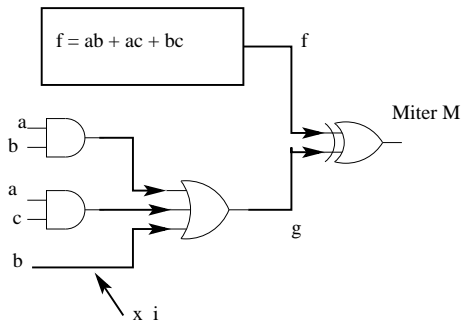
# Example

- Let  $f = ab + ac + bc$  and  $g = ab + ac + b$
- Clearly,  $f \neq g$ , can  $g$  be rectified at net  $x_i$  shown below?



# Rectification Check Passes: Example

In the example on the previous slide:

- Let  $f = ab + ac + bc$  and  $g = ab + ac + b$
- $M(X, x_i = 0) = (ab + ac + bc) \oplus (ab + ac + 0) = a'bc$
- $M(X, x_i = 1) = (ab + ac + bc) \oplus (ab + ac + 1) = a'b' + a'c' + b'c'$
- $M(X, x_i = 0) \wedge M(X, x_i = 1) = 0$ , so rectification is feasible

# Rectification Check Fails: Example

- Let  $f = ab + ac + bc$  (spec) and  $g = a + b$  (buggy implementation)
- Check for single-fix rectifiability at  $x_i = b$  (input of OR gate) in  $g$
- $M(X, x_i = 0) = (ab + ac + bc) \oplus (a + 0) = a'bc + ab'c'$
- $M(X, x_i = 1) = (ab + ac + bc) \oplus (a + 1) = a'b' + a'c' + b'c'$
- $M(X, x_i = 0) \wedge M(X, x_i = 1) = ab'c' \neq 0$ , so rectification at the  $b$  input of the OR gate in  $g$  is not possible.

# Compute Single-Fix Rectification Function $U(X_{PI})$

Theorem (Compute Rectification function  $x_i = U(X_{PI})$ )

*When the above condition (Theorem 1) is satisfied, then the single-fix rectification function can be computed as:*

$$\begin{aligned} [f(X) \oplus g(X, x_i = 0)] \subseteq U(X) \subseteq \overline{[f(X) \oplus g(X, x_i = 1)]} \\ M(X, x_i = 0) \subseteq U(X) \subseteq \overline{M(X, x_i = 1)} \end{aligned}$$

# Compute Single-Fix Rectification Function $U(X_{PI})$


## Theorem (Compute Rectification function $x_i = U(X_{PI})$ )

When the above condition (Theorem 1) is satisfied, then the single-fix rectification function can be computed as:

$$\begin{aligned} [f(X) \oplus g(X, x_i = 0)] \subseteq U(X) \subseteq \overline{[f(X) \oplus g(X, x_i = 1)]} \\ M(X, x_i = 0) \subseteq U(X) \subseteq \overline{M(X, x_i = 1)} \end{aligned}$$

- $[f(X) \oplus g(X, x_i = 0)] = M(X, x_i = 0) =$  ON-set of the rectification function. Call this  $M_0$ .
- $[f(X) \oplus g(X, x_i = 1)] = M(X, x_i = 1) =$  OFF-set of the rectification function. Call this  $M_1$ .
- $\overline{[f(X) \oplus g(X, x_i = 1)]} =$  ON-set  $\cup$  DC-set.
- DC-set =  $\overline{M_0 + M_1}$ .
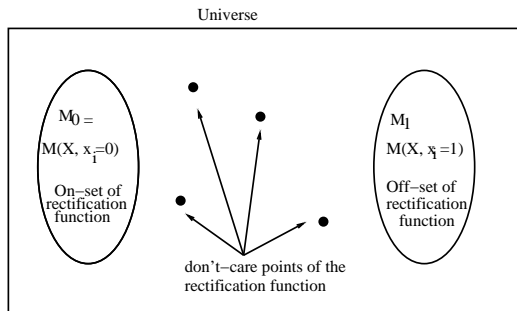
# Characterizing the Rectification Function $U(X_{PI})$



- $[f(X) \oplus g(X, x_i = 0)] = M(X, x_i = 0) = \text{ON-set of the rectification function. Call this } M_0.$
- $[f(X) \oplus g(X, x_i = 1)] = M(X, x_i = 1) = \text{OFF-set of the rectification function. Call this } M_1.$
- $\text{DC-set} = \overline{M_0 + M_1}.$



# Compute Single-Fix Rectification Function $U(X_{PI})$

Theorem (Compute Rectification function  $x_i = U(X_{PI})$ )

*When the above condition (Theorem 1) is satisfied, then the single-fix rectification function can be computed as:*

$$[f(X) \oplus g(X, x_i = 0)] \subseteq U(X) \subseteq \overline{[f(X) \oplus g(X, x_i = 1)]}$$

# Compute Single-Fix Rectification Function $U(X_{PI})$

Theorem (Compute Rectification function  $x_i = U(X_{PI})$ )

*When the above condition (Theorem 1) is satisfied, then the single-fix rectification function can be computed as:*

$$[f(X) \oplus g(X, x_i = 0)] \subseteq U(X) \subseteq \overline{[f(X) \oplus g(X, x_i = 1)]}$$

Does this remind you of Craig Interpolants?

# Compute Single-Fix Rectification Function $U(X_{PI})$

Theorem (Compute Rectification function  $x_i = U(X_{PI})$ )

When the above condition (Theorem 1) is satisfied, then the single-fix rectification function can be computed as:

$$[f(X) \oplus g(X, x_i = 0)] \subseteq U(X) \subseteq \overline{[f(X) \oplus g(X, x_i = 1)]}$$

Does this remind you of Craig Interpolants?

$$M(X, x_i = 0) \wedge M(X, x_i = 1) = \perp$$

There exists C.I.  $I(X)$  s.t.:

- $M(X, x_i = 0) \implies I(X)$ ;
- $I(X) \wedge M(X, x_i = 1) = \perp$ ;
- $I(X)$ , where  $X$  = common variables of  $M(X, x_i = 0)$  and  $M(X, x_i = 1)$ .

Rectification function  $U(X) = I(X)$ !!


Craig Interpolants: A concept of “abstraction”, for UNSAT problems

## Definition

Let  $f(X_A, X_B, X_C)$  be a Boolean function in variables  $X = \{x_1, \dots, x_n\}$  such that  $X$  is partitioned into disjoint subsets  $X_A, X_B, X_C$ . Let  $f = f_A(X_A, X_C) \wedge f_B(X_B, X_C) = \emptyset$ . Then there exists another Boolean function  $f_I$  such that:

- $f_A \implies f_I$ ; or  $f_A \subseteq f_I$
- $f_I \wedge f_B = \emptyset$
- $f_I(X_C)$  only contains  $X_C$  variables, i.e. the common variables of  $f_A, f_B$ :  $\text{Vars}(f_I) \subseteq \text{Vars}(f_A) \cap \text{Vars}(f_B)$

# Craig Interpolants

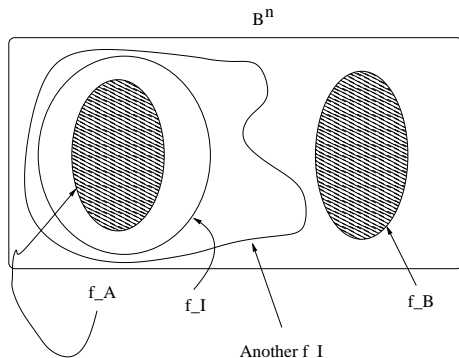

- The ABC tool with MiniSAT solver can return an  $f_I$ , provided  $f_A, f_B, X_A, X_B, X_C$  is given.
- Interpolant computed through a **resolution proof**

# Craig Interpolants: Examples

There may be more than one interpolants:

- $f = f_A \cdot f_B$
- $f_A = (a_1 + a'_2)(a'_1 + a'_3)(a_2) = a_1 a_2 a'_3$
- $f_B = (a'_2 + a_3)(a_2 + a_4)(a'_4) = a_2 a_3 a'_4$
- $X_A = \{a_1\}, X_B = \{a_4\}, X_C = \{a_2, a_3\}$
- One interpolant  $f_{I_1} = a'_3 a_2$
- Another interpolant  $f_{I_2} = a'_3$
- The set of all interpolants forms a **lattice**, the smallest interpolant at the bottom, and the largest at the top
- Smallest interpolant:  $f_I^{smallest} = \exists_{X_A} f_A(X_A, X_C)$
- Largest interpolant:  $f_I^{largest} = \overline{\exists_{X_B} f_B(X_B, X_C)}$

# To compute Interpolants

Use Boolean logic manipulation, or use a SAT solver

- Using Boolean manipulation, we can compute two interpolants
- Smallest interpolant:  $f_I^{smallest} = \exists_{X_A} f_A(X_A, X_C)$ , where  $\exists_x f(x, y, z, \dots)$  is a Boolean function defined as
  - $\exists_x f(x, y, z, \dots) = f_x + \overline{f_x}$ ,  $f_x = f(x = 1)$  and  $\overline{f_x} = f(x = 0)$ .
  - $f_x$  = the positive cofactor of  $f$  w.r.t.  $x$ ,  $\overline{f_x}$  is negative cofactor.
  - $\exists_x f(x, y, z, \dots)$  is called existential abstraction of  $f$  w.r.t.  $x$ , also called smoothing.
  - $\exists_x f(x, y, z, \dots)$  is the smallest function larger than  $f$ , i.e. it contains  $f$  and does not have  $x$  in its support.
- Largest interpolant =  $\overline{\exists_{X_B} f_B(X_B, X_C)}$

# Craig Interpolant: Examples

From the previous slides:

- $f_A = a_1 a_2 a'_3$  and  $f_B = a_2 a_3 a'_4$
- $X_A = \{a_1\}$ ,  $X_B = \{a_4\}$ ,  $X_C = \{a_2, a_3\}$
- Smallest interpolant:  $f_I^{smallest} = \exists_{X_A} f_A(X_A, X_C) = a_2 a'_3$
- Largest interpolant:  $f_I^{largest} = \overline{\exists_{X_B} f_B(X_B, X_C)}$ 
  - Largest interpolant =  $\overline{\exists_{X_B} a_2 a_3 a'_4} = \overline{a_2 a_3} = a'_2 + a'_3$
- Let  $f_I$  be any interpolant, then  $f_I^{smallest} \subseteq f_I \subseteq f_I^{largest}$



# To compute Rectification Function

$$M(X, x_i = 0) \wedge M(X, x_i = 1) = \perp$$

There exists C.I.  $I(X)$  s.t.:

- $M(X, x_i = 0) \implies I(X)$ ;
  - $I(X) \wedge M(X, x_i = 1) = \perp$ ;
  - $I(X)$ , where  $X$  = common variables of  $M(X, x_i = 0)$  and  $M(X, x_i = 1)$ .
- 
- Rectification function  $x_i = U(X) = I(X)$ !
  - $X$  = primary inputs of the circuit, as all PIs common variables of the miter.
  - $I(X) = M(X, x_i = 0)$  is the smallest interpolant, and serves as the rectification function.

## Example: Compute $U(X_{PI})$

- Let  $f = ab + ac + bc$  and  $g = ab + ac + b$
- $U(X) = I(X) = M(X, x_i = 0) = a'bc$ , the smallest interpolant works as a rectification function  $g = ab + ac + a'bc$
- Largest interpolant:  $\overline{M(X, x_i = 1)} = ab + ac + bc$  also works:  
 $g = ab + ac + ab + ac + bc$
- Any interpolant works as a rectification function:  
 $M(X, x_i = 0) \subseteq I(X) \subseteq \overline{M(X, x_i = 1)}$ 
  - $I(X) = bc$  also rectifies  $g$

For Logic Synthesis of  $U(X_{PI})$ , synthesize:  $M_0$  as the **care-set** of  $U$ ,  $M_1$  as the **offset** of  $U$ , and  $\overline{M_1} - M_0$  as the **don't care set** of  $U$ .

## Why $U(X_{PI}) = I(X)$ rectifies the circuit?

- $M_0 = M(X, x_i = 0)$  gives the error cubes for the implementation when  $x_i = 0$
- Since  $I(X) \supseteq M_0$ , and  $I(X)$  evaluates to 1 for all minterms of  $M_0$ , it fixes all the mismatches that occurred when  $x_i = 0$
- $M_1 = M(X, x_i = 1)$  gives the error cubes for the implementation when  $x_i = 1$
- $I(X) \wedge M_1 = 0$ , i.e.  $I(X)$  evaluates to 0 for all minterms of  $M_1$ , so it fixes all the mismatches that occurred when  $x_i = 1$
- Thus  $I(X)$  computes the rectification patch


Important References [1] [2] [3] [4]

# Identify Single-Fix Rectification Target Net $x_i$

- Perform Combinational Equivalence Checking (CEC) between  $C_1, C_2$ 
  - Use the following command in ABC: `ABC> cec C1.blif C2.blif`
- Since  $C_1 \neq C_2$ , ABC identifies the outputs of the circuits which are affected by the bug
- Say, there exists an input (counter-example to CEC)  $X_1$  s.t.  
 $f_i(X_1) \neq f_j(X_1)$
- Identify the transitive fanin-cones of  $f_i, f_j$
- Identify the set of nets  $\mathcal{N}$  (gate-outputs) that lie in the **intersection of fanin-cones** of  $f_i, f_j$
- Then the nets  $x_i \in \mathcal{N}$  are candidates for single-fix rectification

# Identify Single-Fix Target Net $x_i$



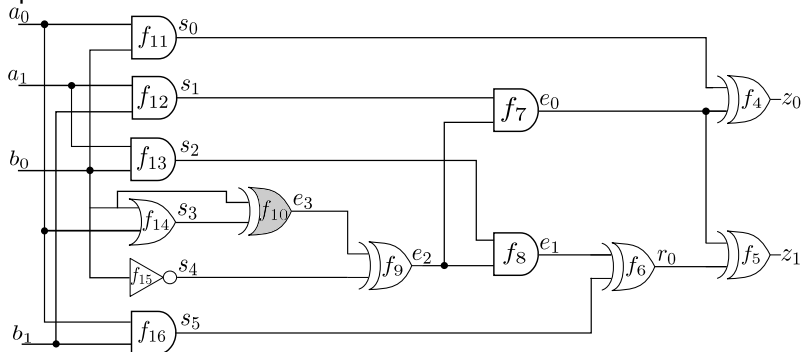

Example Circuit:



The circuit is buggy, bug = gate change at net  $e_3$ , which should have been an AND gate. Both outputs  $z_0, z_1$  affected by the bug.

## Identify Single-Fix Target Net $x_i$

- In the previous figure,  $e_3$  should have been an AND gate in the correct circuit  $C_1$
- Bug introduced,  $e_3 = XOR$  gate
- The bug affects both outputs  $z_0, z_1$
- Fanin cone  $z_0 = \{s_0, e_0, s_1, e_2, e_3, s_3, s_4, X_{PI}\}$
- Fanin cone  $z_1 = \{r_0, s_5, e_1, s_2, e_2, e_3, s_3, s_4, e_0, s_1, X_{PI}\}$
- Intersection of fanin cones:  $\mathcal{N} = \{s_3, e_3, e_2, s_4, e_0, s_1, s_2, X_{PI}\}$  are targets for rectification  $x_i$
- Select a net  $x_i \in \mathcal{N}$  to see if Theorem 1 ascertains rectifiability at  $x_i$

-  C. C. Lin, K. C. Chen, S. C. Chang, and M. Marek-Sadowska, “Logic Synthesis for Engineering Change,” in *Proc. Design Automation Conf. (DAC)*, 1995, pp. 647–652.
-  K.-F. Tang, C.-A. Wu, P.-K. Huang, and C.-Y. R. Huang, “Interpolation based incremental ECO Synthesis for Multi-Error Logic Rectification,” in *Proc. Design Automation Conf.*, 2011, pp. 146–151.
-  A. Dao, N.-Z. Lee, L.-C. Chen, M. Lin, J.-H. Jiang, A. Mishchenko, and R. Brayton, “Efficient Computations of ECO Patch Functions,” in *Proc. Design Auto. Conf.*, 2018.
-  M. Fujita, “Toward Unification of Synthesis and Verification in Topologically Constrained Logic Design,” *Proceedings of the IEEE*, 2015.