


Date Sept. 5

(i)

Testability of prime & irredundant
Two-level circuits.

$$f = ab + ac + b\bar{c}$$

a	b	c	f
1	1	-	1
1	-	1	1
-	1	0	1

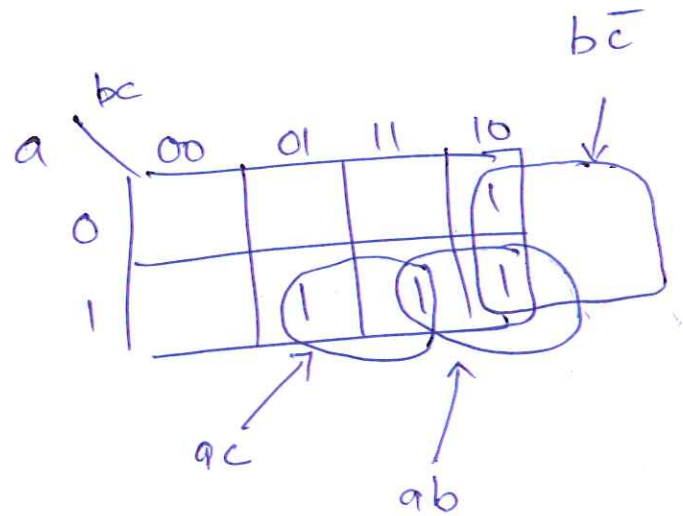


All cubes are prime.

'ab' = redundant \Rightarrow 'drop' ab from the cover of f

$$\Rightarrow f = ac + b\bar{c}$$

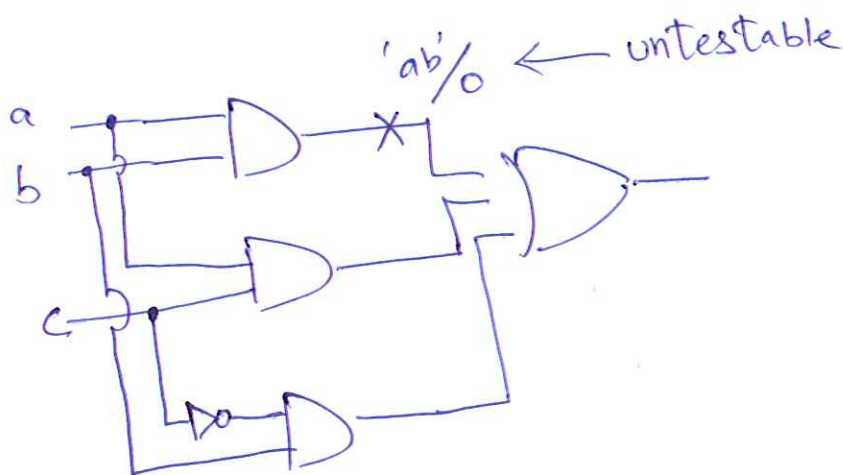
Redundancy \Leftrightarrow untestable fault



Now consider the same function

(2)

$$f = a\bar{b}c + ab + b\bar{c}$$

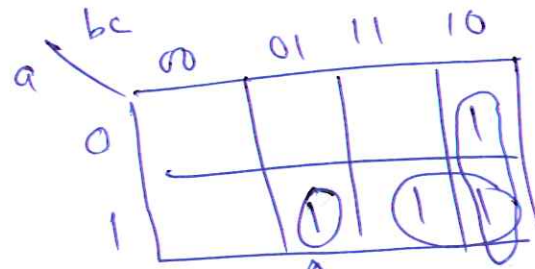


non-prime cube

$a\bar{b}c$

But, cover = irredundant

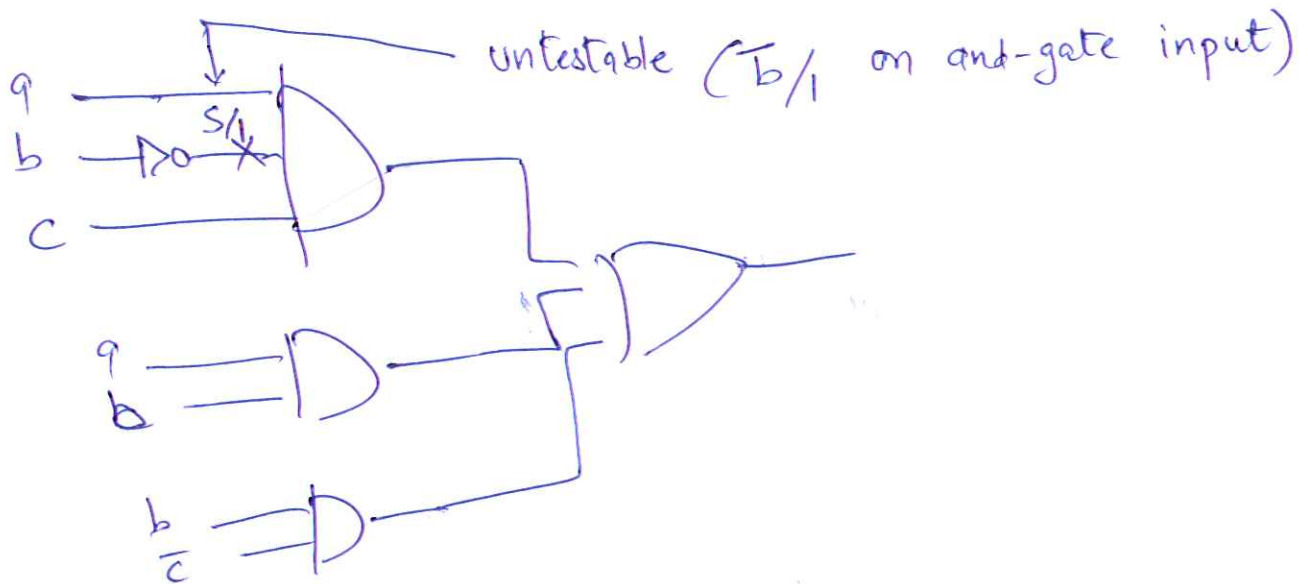\Rightarrow cannot 'drop' any cube from the cover.



Conclusion: -

Non-prime cubes \Rightarrow untestable $\frac{S}{1}$ on AND gate inputs.

Non-irredundant cover \Rightarrow untestable $\frac{S}{0}$ on OR-gate inputs.

3



Make a two-level cover

prime & irredundant

\Leftrightarrow every fault testable

$$f = ab + ac + b\bar{c}$$

$$= ac + b\bar{c}$$

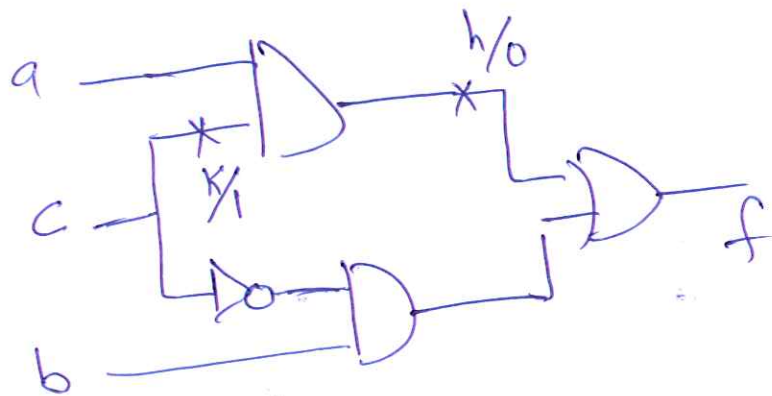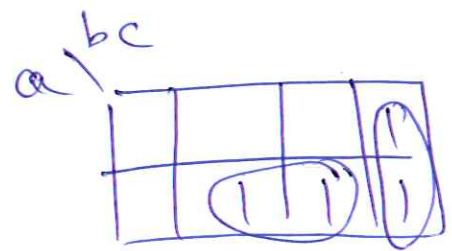

$T_{h/0}$ $a=1, c=1$ $f = 0$

$T_{k/1}$ $a=1, c=0, b=0, f = 1$

Concept of prime + irredundant too complicated for multi-level circuits.