 


Logic Synthesis

Timing Analysis

Timing Analysis - Delay Models


- Simple model 1:



$A_k = \text{arrival time} = \max(A_1, A_2, A_3) + D_k$

D_k is the delay at node k , parameterized according to function f_k and fanout node k

- Simple model 2:

 

- Can also have different times for **rise** time and **fall** time


Static delay analysis

```
// level of PI nodes initialized to 0,  
// the others are set to -1.  
// Invoke LEVEL from PO  
Algorithm LEVEL(k) { // levelize nodes  
    if( k.level != -1)  
        return(k.level)  
    else  
        k.level = 1+max{LEVEL(ki) | ki ∈ fanin(k)}  
    return(k.level)  
}  
  
// Compute arrival times:  
// Given arrival times on PI's  
Algorithm ARRIVAL() {  
    for L = 0 to MAXLEVEL  
        for {k|k.level = L}  
            Ak = MAX{Aki} + Dk  
}
```

Required Times

Required times:

given required times on primary outputs

 

- Traverse in reverse topological order (i.e. from primary outputs to primary inputs)
- if (k_i, k) is an edge between k_i and k , $R_{k_i, k} = R_k - D_k$
(this is the edge required time)
- Hence, the required time of output of node k is
$$R_k = \min (R_{k, k_j} \mid k_j \in \text{fanout}(k))$$

Propagating Slacks

Slacks: slack at the output node k is $S_k = R_k - A_k$

Since $R_{ki \rightarrow k} = R_k - D_k$


$$S_{ki \rightarrow k} = R_{ki \rightarrow k} - A_{ki}$$

$$S_{ki \rightarrow k} + A_{ki} = R_k - D_k = S_k + A_k - D_k$$

Since $A_k = \max \{A_{kj}\} + D_k$

$$S_{ki \rightarrow k} = S_k + \max \{A_{kj}\} - A_{ki} \quad k_j, k_i \in \text{fanin}(k)$$

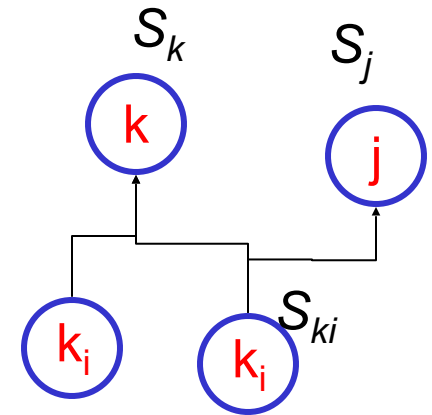
$$S_{ki} = \min \{S_{ki \rightarrow j}\} \quad j \in \text{fanout}(k_i)$$



Notes:

- Each edge in the graph has a slack and a required time
- Negative slack is bad.

Sequential networks

 

- Arrival times known at I_1 and I_2
- Required times known at I_3 , I_4 , and I_5
- Delay analysis gives arrival and required times (hence slacks) for C_1 , C_2 , C_3 , C_4

Static critical paths


Min-Max problem: minimize $\max\{-S_i, 0\}$

A **static critical path** of a Boolean network is a path $P = \{i_1, i_2, \dots, i_p\}$
where $S_{i_k, i_{k+1}} < 0$

Note: if a node k is on a static critical path, then at least one of the fanin edges of k is critical. Hence, all critical paths reach from an input to an output.

Note: There may be several critical paths

Example: Static critical paths

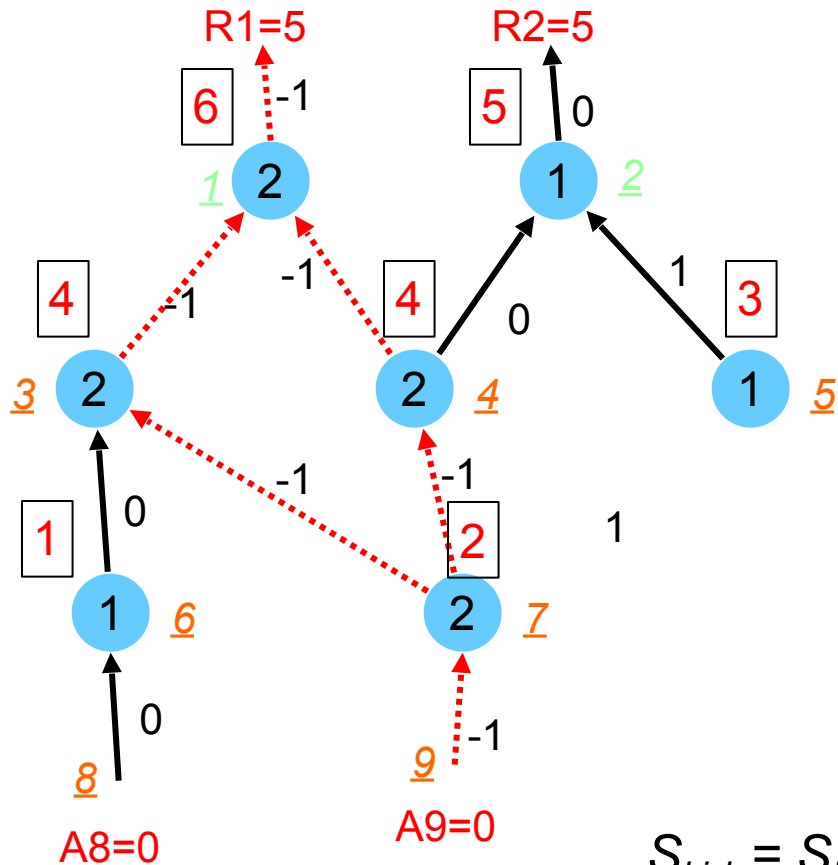

A1=6
A2=5

R1=5
R2=5

$S_1 = -1$
 $S_2 = 0$
 $S_{3,1} = -1$
 $S_{4,1} = -1$
 $S_{4,2} = 0$
 $S_{5,2} = 1$
 $S_{6,3} = 0$
 $S_{7,3} = -1$
 $S_{7,4} = -1$
 $S_{7,5} = 1$
 $S_{8,6} = 0$
 $S_{9,7} = -1$

R3=3
R7=1
R9=-1

..... critical path edges

$$S_{k_i, k} = S_k + \max\{A_{k_j}\} - A_{k_i}, k_j, k_i \in \text{fanin}(k)$$

$$S_k = \min\{S_{k, k_j}\}, k_j \in \text{fanout}(k)$$

Timing analysis problems

We want to determine the **true** critical paths of a circuit in order to:

- determine the minimum cycle time that the circuit will function
- identify critical paths from performance optimization - don't want to try to optimize the **wrong** (non-critical) paths


Implications:

- Don't want false paths (produced by static delay analysis)
- Delay model is **worst** case model. Need to ensure correctness for case where i^{th} gate delay $\leq D_i^M$

Functional Timing Analysis

What is Timing Analysis?

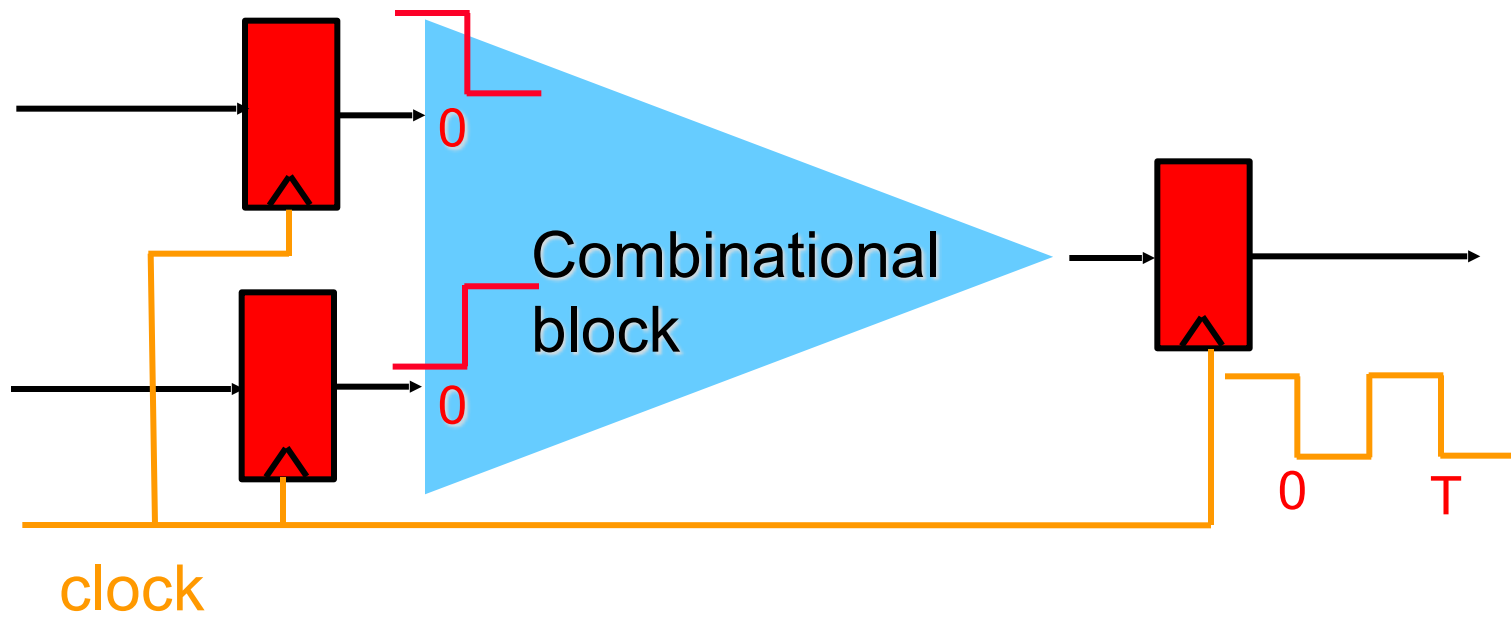Estimate when the output of a given circuit gets stable



Why Timing Analysis?

Timing verification

- Verifies whether a design **meets** a given timing constraint
 - **Example:** cycle-time constraint

Timing optimization

- Needs to identify **critical** portion of a design for further optimization
 - Critical path identification

In both applications, the more **accurate**, the better

Timing Analysis - Basics

Naïve approach - Simulate all input vectors with SPICE

- Accurate, but too expensive


Gate-level timing analysis

Focus of this lecture

- Less accurate than SPICE due to the level of abstraction, but **much** more efficient
- Scenario:
 - Gate/wire delays are pre-characterized (accuracy loss)
 - Perform timing analysis of a gate-level circuit assuming the gate/wire delays

Gate-level Timing Analysis

False
path
aware
 $\text{arr}(z)$?

 

$\text{arr}(x_1)=0$ $\text{arr}(x_2)=0$

A naive approach is topological analysis

- Easy longest-path problem
- Linear in the size of a network


Not all paths can propagate signal events

- **False paths**
- If all longest paths are false, topological analysis gives delay **overestimate**

Functional timing analysis = false-path-aware timing analysis

- Compute false-path-aware arrival time

Example: 2-bit Carry-skip Adder

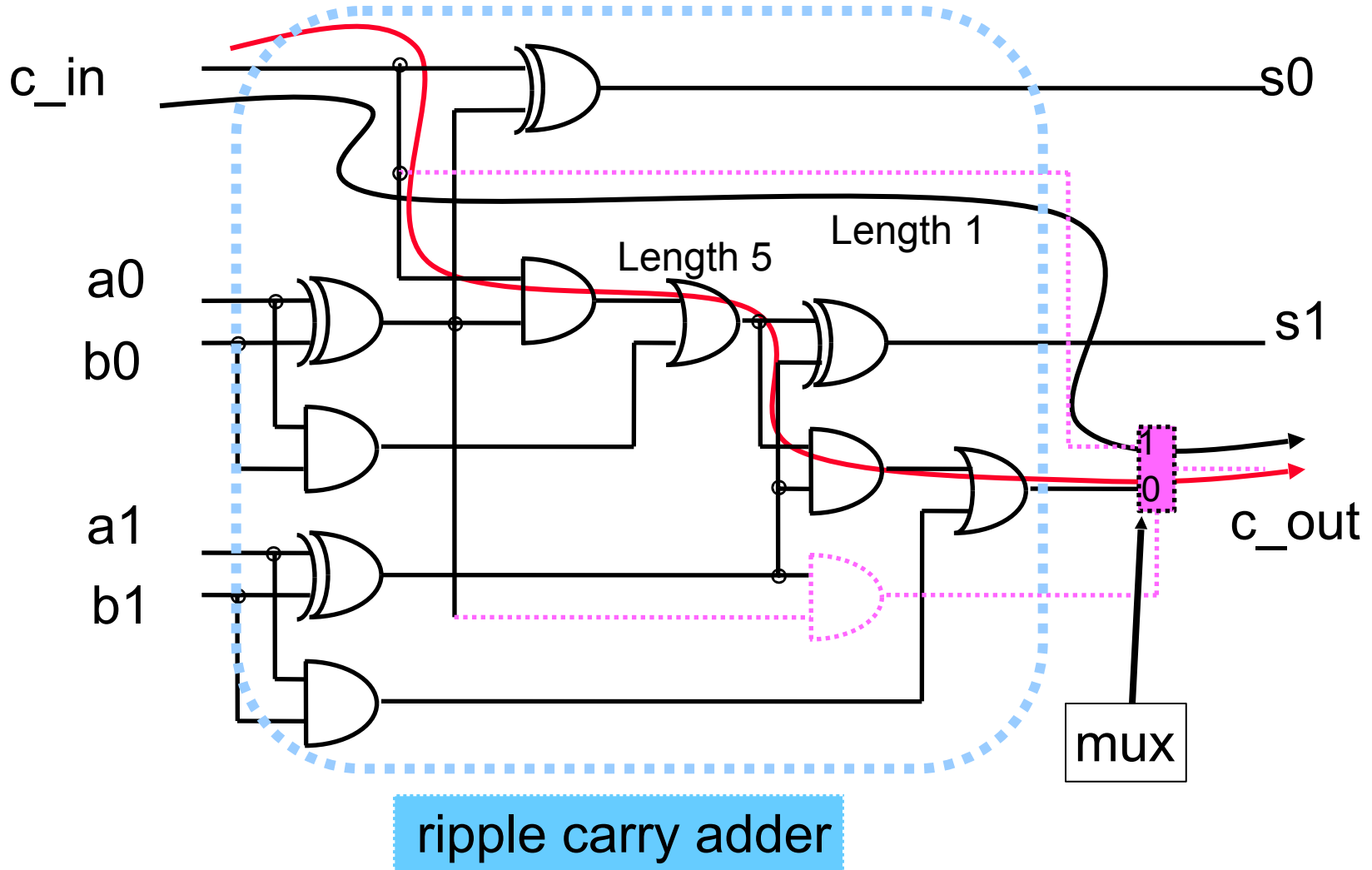

False Path Analysis - Basics

Is a path **responsible** for delay?

- If the answer is no, can **ignore** the path for delay computation

Check the falsity of long paths until we find the longest true path

- How can we determine whether a **path is false**?

Delay underestimation is **unacceptable**


- Can lead to overlooking a timing **violation**

Delay overestimation is not desirable, but **acceptable**


- **Topological** analysis can give overestimate, but never give underestimate

Controlling/Non-Controlling Values

Controlled value of AND

 


Controlling value of AND

 


Non-Controlling value of AND

Controlled value of OR

 

Controlling value of OR

 


Non-Controlling value of OR

Static Sensitization

A path is *statically-sensitizable* if there exists an input vector such that all the side inputs to the path are set to non-controlling values


- This is *independent* of gate delays

 

The longest *true* path is of length 2?

Static Sensitization

 - The (dashed) path is responsible for delay!
- Delay underestimation by static sensitization (delay = 2 when true delay = 3)
 - incorrect condition




What is Wrong with Static Sensitization?

The idea of forcing non-controlling values to side inputs is okay, **but** timing was ignored

- The same signal can have a **controlling** value at one time and a **non-controlling** value at another time.


How about **timing simulation** as a correct method?

Timing Simulation

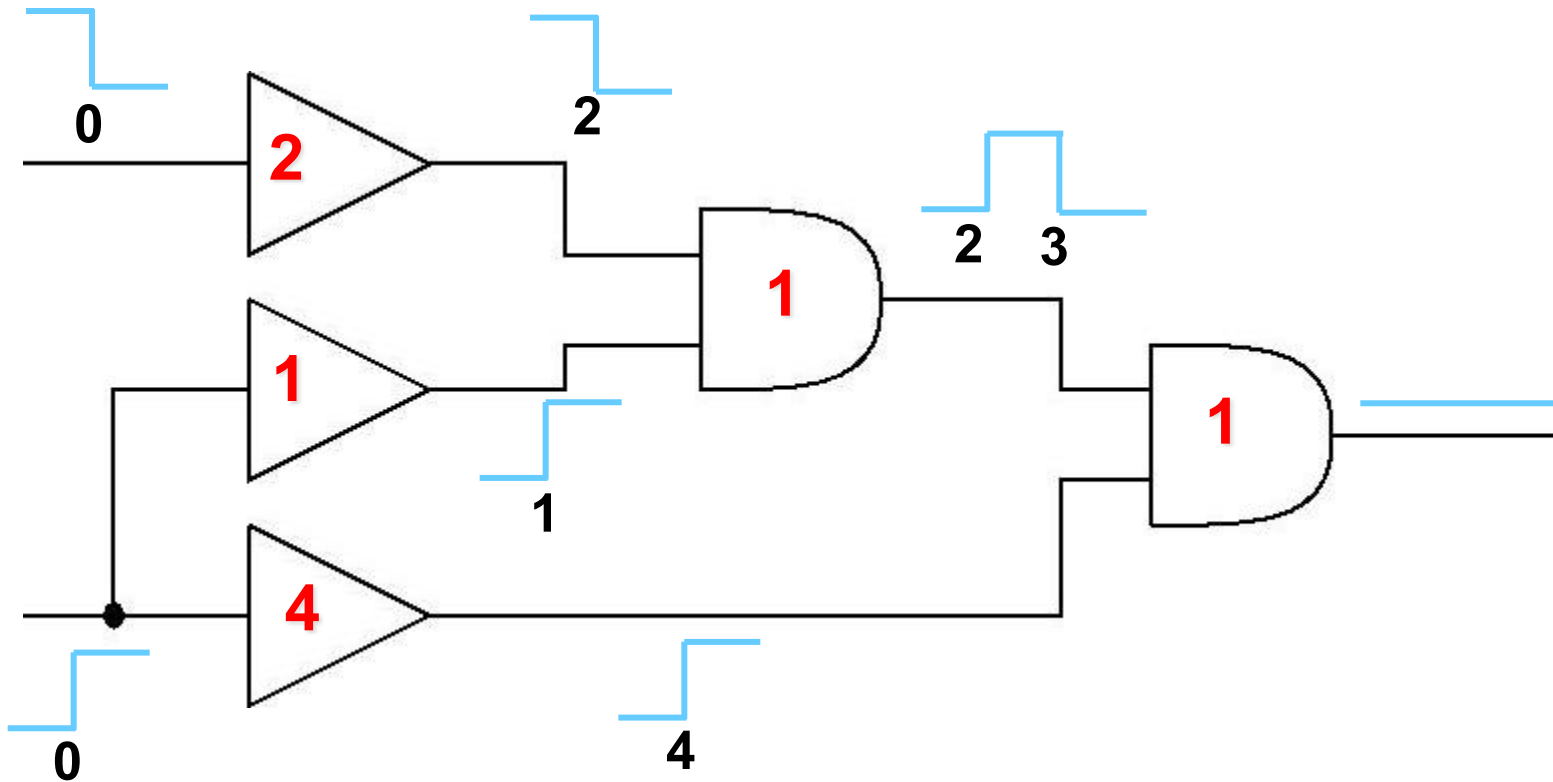

Implies that delay = 0 for these inputs
BUT!

Timing Simulation

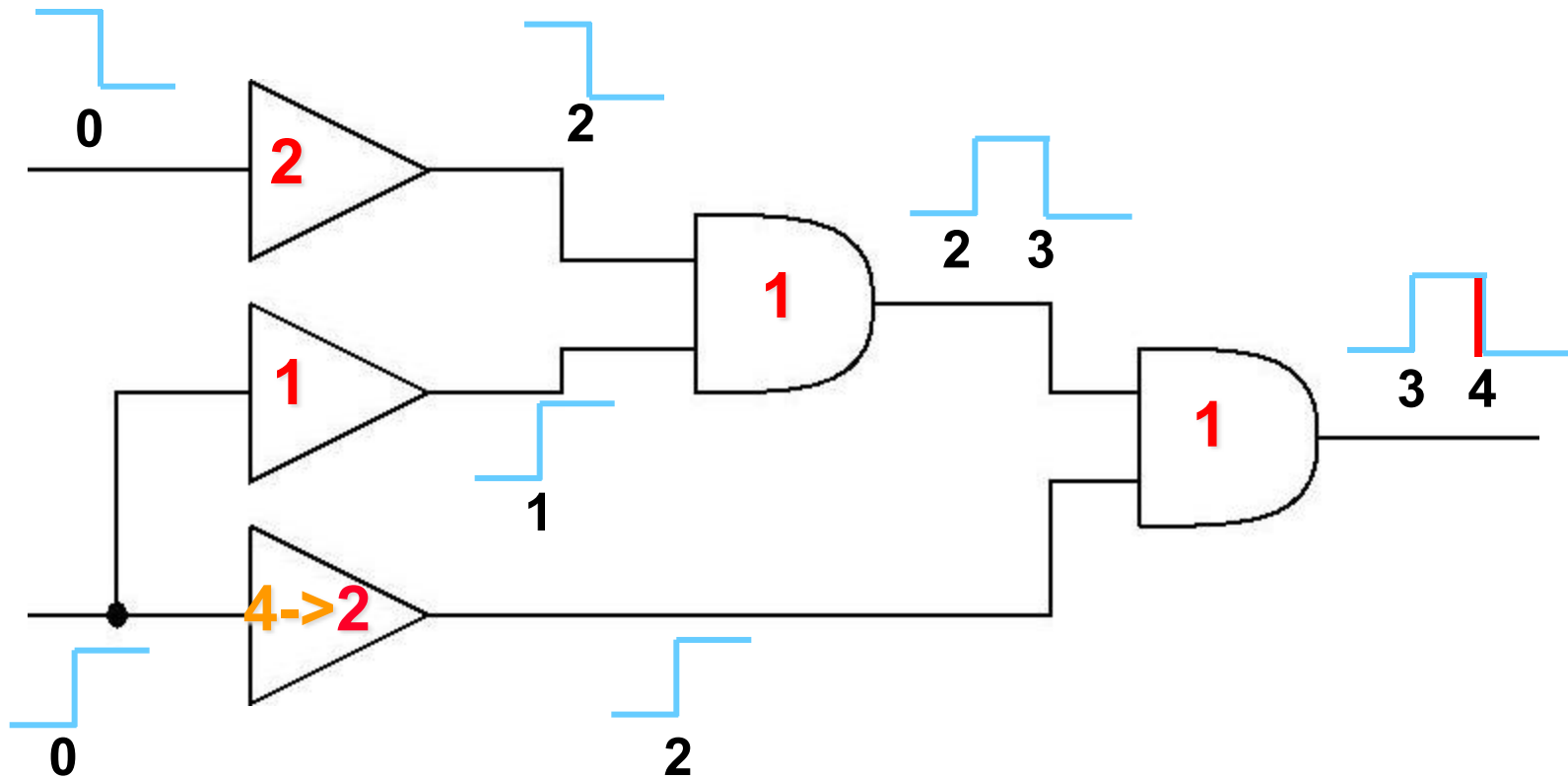

Implies that delay = 4 with the same set of inputs.

What is Wrong with Timing Simulation?

If gate delays are **reduced**, delay estimates can **increase**

Not acceptable since

- Gate delays are just **upper-bounds**, actual delay is in $[0,d]$
 - Delay **uncertainty** due to manufacturing
- We are implicitly analyzing a **family** of circuits where gate delays are **within** the upper-bounds

Monotone Speedup Property



Definition: For any circuit C , if

- C' is obtained from C by reducing some gate delays, and
- $\text{delay_estimate}(C') \leq \text{delay_estimate}(C)$,

then delay_estimate has *Monotone Speedup*

Timing simulation does **not** have this property

Timing Simulation Revisited

 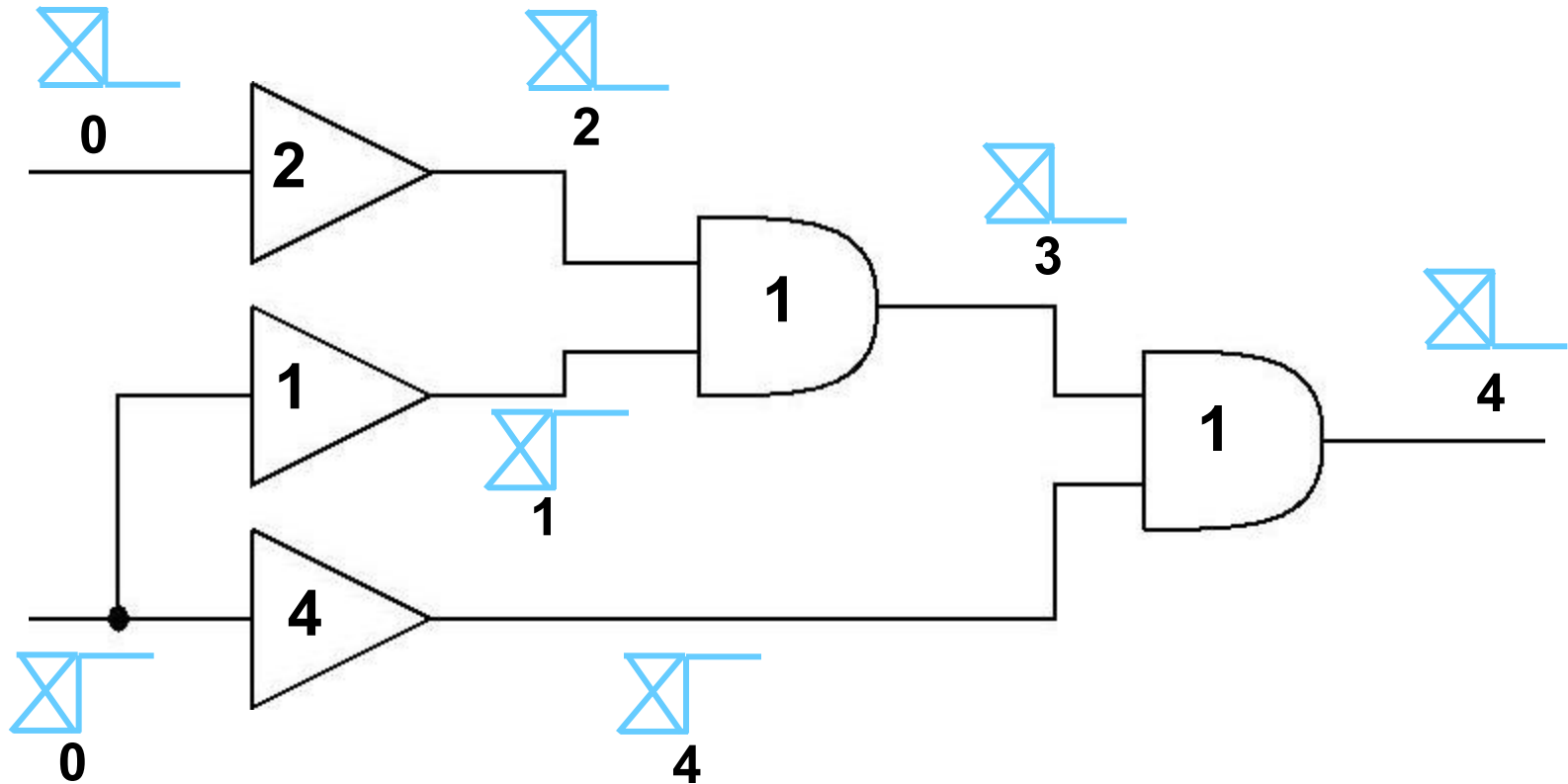

means that the rising signal occurs anywhere between $t = -\infty$ and $t = 4$.

X-valued simulation

Timing Simulation Revisited

Timed 3-valued (0,1,X) simulation

- called X-valued simulation

Monotone speedup property is *satisfied*.

Underlying model of

- *floating mode condition* [Chen, Du]
 - Applies to “simple gate” networks only
- *viability* [McGeer, Brayton]
 - Applies to general Boolean networks

False Path Analysis Algorithms

Checking the falsity of **every** path explicitly is too expensive - exponential # of paths

State-of-the-art approach:

1. Start: set $L = L_{\text{top}}$ - ! = topological longest path delay - !

$$L_{\text{old}} = 0$$

2. Binary search:

If (Delay(L)) (*)

$$! L = |L - L_{\text{old}}|/2, L_{\text{old}} = L, L = L + ! L$$

$$\text{Else, } ! L = |L - L_{\text{old}}|/2, L_{\text{old}} = L, L = L - ! L$$

If ($L > L_{\text{top}}$ or $! L < \text{threshold}$), $L = L_{\text{old}}$, done

(*) Delay(L) = 1 if there an input vector under which an output gets stable only at time t where $L \leq t$?

Can be reduced to

- a SAT problem [McGeer, Saldanha, Brayton, ASV] or
- a timed-ATPG [Devadas, Keutzer, Malik]

SAT-based False Path Analysis

Decision problem:

Is there an input vector under which the output gets stable only after $t = T$?

Idea:


1. characterize the set of all input vectors $S(T)$ that make the output stable no later than $t = T$
2. check if $S(T)$ contains $S =$ all possible input vectors

This check is solved as a SAT problem:

Is $S \setminus S(T)$ empty? - set difference + emptiness check

- Let F and $F(T)$ be the characteristic functions of S and $S(T)$
- Is $F \neg F(T)$ satisfiable?


Example

 

Assume all the PIs arrive at $t = 0$, all gate delays = 1
Is the output stable time $t > 2$?

 Example

$g(1, t=2)$: the set of input vectors under which
 g gets **stable to value** = 1 **no later** than $t = 2$




$$\begin{aligned}
 g(1, t=2) &= d(1, t=1) \cap f(1, t=1) \\
 &= (a(0, t=0) \cap b(0, t=0)) \cap (c(1, t=0) \cup e(1, t=0)) \\
 &= !a!b(c \cup \emptyset) = !a!bc = S_1(t=2)
 \end{aligned}$$

$$g(1, t=\infty) = \text{onset} = !a!bc = g(1, t=2) = S_1$$

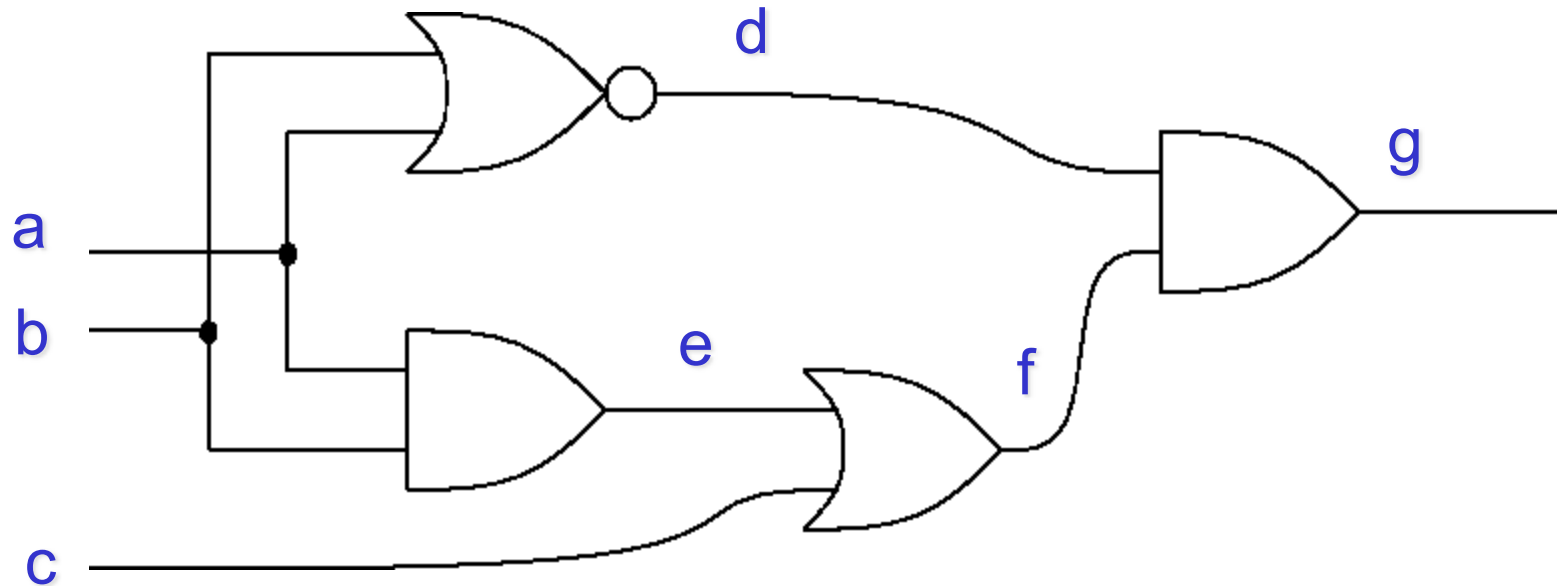Example

$g(0, t=2)$: the set of input vectors under which g gets stable to value = 0 no later than $t=2$




$$\begin{aligned} g(0, t=2) &= d(0, t=1) \cup f(0, t=1) \\ &= (a(1, t=0) \cup b(1, t=0)) \cup (c(0, t=0) \cap e(0, t=0)) \\ &= (a+b) + (!c \cap \emptyset) = a+b = S_0(t=2) \end{aligned}$$

$$g(0, t=\infty) = \text{offset} = a+b+!c = S_0$$

 Example

$g(0, t=2)$: the set of input vectors under which g gets stable to 0 no later than $t=2$



$$g(0, t=2) = a+b$$

$$g(0, t=\infty) = \text{offset} = a+b+!c$$

$$g(0, t=\infty) \setminus g(0, t=2) = (a+b+!c) !(a+b) = !a !b !c = \text{satisfiable}$$

Summary

False-path-aware arrival time analysis is **well-understood**

- **Practical** algorithms exist
 - Can handle industrial circuits easily

Remaining problems

- **Incremental** analysis (make it so that a small change in the circuit does not make the analysis start all over)
- Integration with logic **optimization**
- DSM issues such as **cross-talk-aware** false path analysis

Timed ATPG

Yet another way to solve the same decision problem

A **generalization** of regular ATPG:

- regular ATPG
 - find an input vector that **differentiates** a **fault-free** circuit and a **faulty** circuit in terms of functionality
- Timed ATPG
 - find an input vector that exhibits a **given timed behavior**
 - Timed extension of PODEM