

①

Automatic Test Pattern Generation for stuck-at Faults.

Given: ① A gate-level ckt model = golden model
= fault-free circuit. = G


DO:- ② Pick a net in G . Assume a net $x_i \in C$ is stuck-at-0. Derive a test for x_i stuck-at 0. Denoted $T_{x_i/0}$.

Test :- A set of vectors at Primary inputs that distinguishes the faulty and fault-free G under the presence of $x_i/0$.

- ③ Repeat ② for $x_i/1$: Find $T_{x_i/1}$
④ Repeat for all nets.

Test set = $\{ T_{x_i/0}, T_{x_i/1} \mid x_i \in C \}$

Test S-a-f on Primary Inputs.

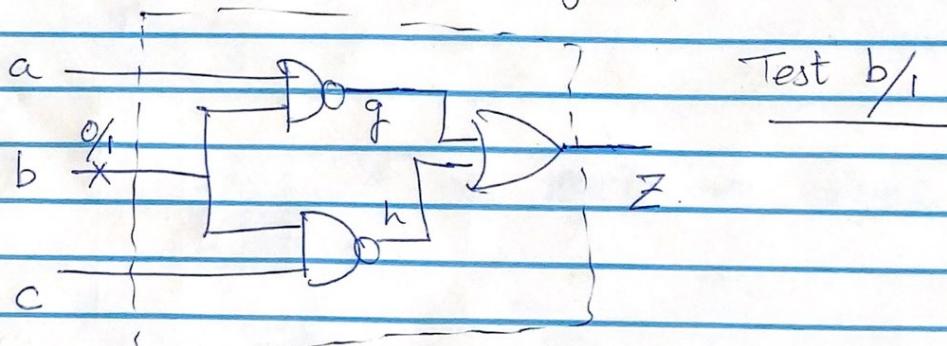

To test b/1

(2)


i) Fault Activation:- or excitation

Apply $\underline{\underline{b=0}}$, the value complement of stuck value


ii) Fault propagation: Apply values on the

Side-inputs (other inputs) such that
the fault-effect propagates to P.O.

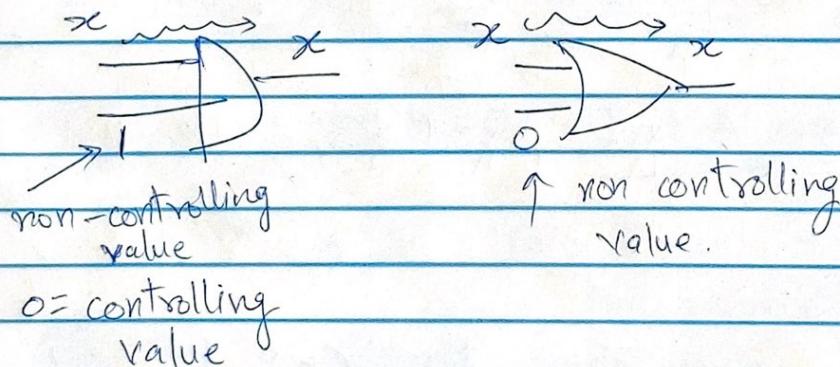iii) For this, you need non-controlling values
on the side-inputs of the gates on the
sensitized path.



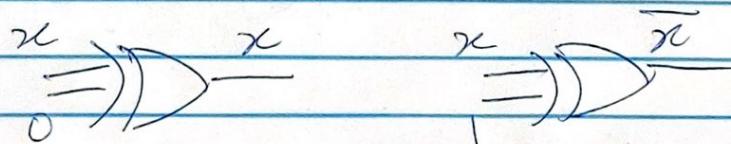
$\underline{\underline{XORs}} \rightarrow$ no controlling values.



(3)

iv) Path sensitization.

- single path sensitization ✓
- multi " "

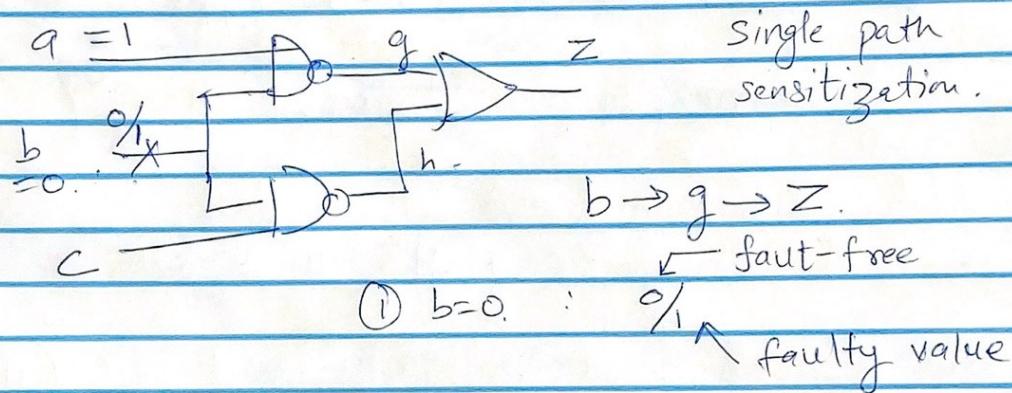(1) $b=0$: ✓(2) $a=1$ = non-controlling value
 $\Rightarrow g = \text{✓}$ $h=0 \Rightarrow z = \text{✓} = \text{fault-free} = 1$ (3) Can we get $h=0$? Justification needed.with $b=\text{✓}$, $c=?$ so that $h=0$?Not possible to get $h=0$.

(4) Try a different single path.


 $b \rightarrow h \rightarrow z$.
 $c=1 \quad h = \text{✓}, \quad (g=0) \quad z = \text{✓}$.

Justification not possible.

Single path sensitization fails.

(4)

⑤ Try Multipath sensitization.

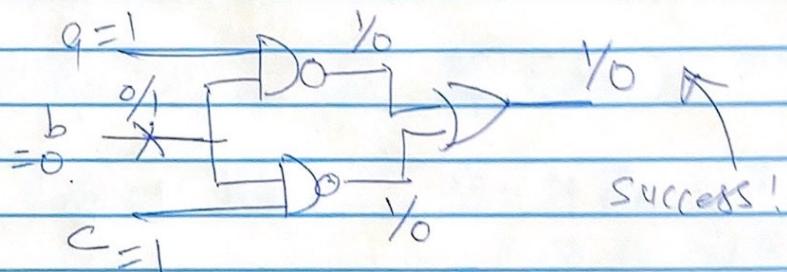

$$T_{b/1} = \{a=1, b=0, c=1\}.$$

IF no fault exists $Z=1$ } Detected.
If fault exists $Z=0$.

Sometimes: Single path sensitization works.

~~or~~ or

Sometimes multi path ✓

Sometimes both may work

other times None may work →

Untestable fault.

$$\text{Test on PIs: } T_{x/1} = \frac{\partial Z}{\partial x}$$

Activation ↑ Propagation

Pore it

remember Boolean difference.

(5)

$$\begin{array}{ll} \text{Fault free } & Z \\ \text{Faulty } & Z_f = Z(x=1) \end{array}$$

$$\text{Miter } Z \oplus Z_{\bar{x}}(x=1) = T_{x_1}$$

$$\begin{aligned} \text{Shannon's Expansion. } Z &= x Z_x + \bar{x} Z_{\bar{x}} \\ &= x Z_x \oplus \bar{x} Z_{\bar{x}} \end{aligned}$$

$$T_{x_1} = x Z_x \oplus \bar{x} Z_{\bar{x}} \oplus Z(x=1)$$

$$= \underline{x Z_x} \oplus \underline{\bar{x} Z_{\bar{x}}} \oplus Z_x$$

$$= x Z_x \oplus Z_x \oplus \bar{x} Z_{\bar{x}}$$

$$= Z_x(x \oplus 1) \oplus \bar{x} Z_{\bar{x}}$$


$$= \bar{x} Z_x \oplus \bar{x} Z_{\bar{x}}$$

$$= \bar{x} [Z_x \oplus Z_{\bar{x}}] = \bar{x} \frac{\partial Z}{\partial x}$$

$$T_{x_1} = x \cdot \frac{\partial Z}{\partial x}$$

Trick:- Shannon's OR = also XOR

(6)

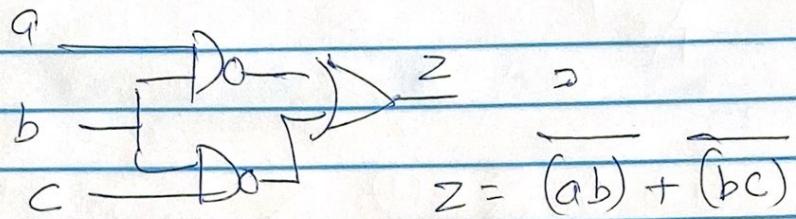


$$\begin{aligned}\frac{\partial Z}{\partial b} &= Z_b \oplus Z_b\bar{=} \\ &= [\overline{a \cdot 1} + \overline{1 \cdot c}] \oplus [\overline{0} + \overline{0}] \\ &= [\overline{a} + \overline{c}] \oplus 1 \\ &= \overline{\overline{a} + \overline{c}} = a \cdot c.\end{aligned}$$

Tb/ = b=0, a=1 c=1

↑ Propagation
condition.
 $a=1$ $c=1$

Tb/ = b=1 a=1, c=1

Fanout stems versus Fanout branches.

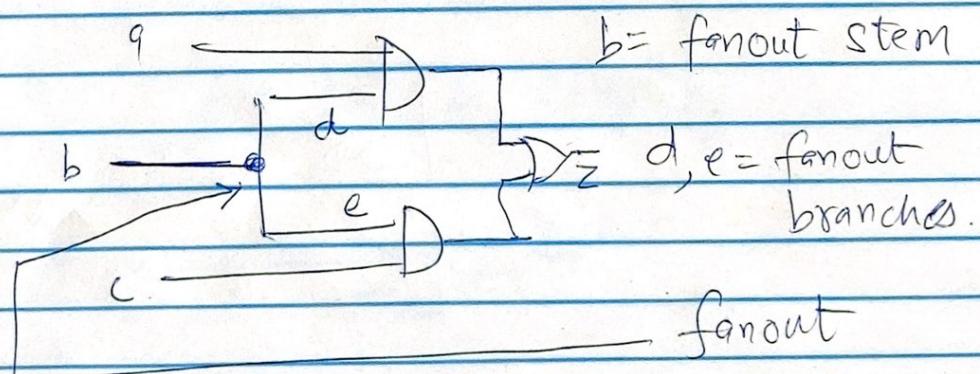


fanout reconverts to $Z = \text{reconvergent fanouts.}$

~~Stem faults~~ \neq branch faults.

(7)

See slide # 19 Te₁

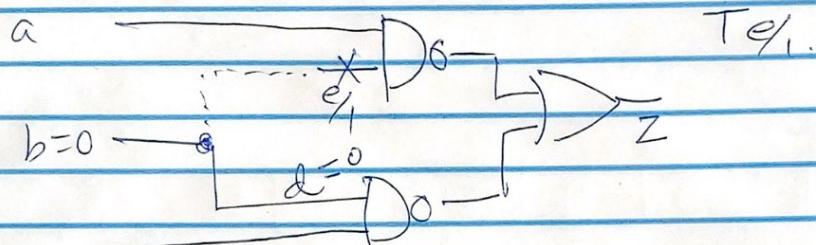

$$b=0, \boxed{e=1} \quad z=1$$
$$\Rightarrow d=0 \Rightarrow z_f=1$$

No Test \Leftrightarrow Redundancy.

Redundancy can be detected.

$e=1 \Rightarrow e=1$ has no effect on z .

Put $e=1$ & Simplify.

