

ECE/CS 3700

Digital System Design

Lecture Slides for Chapters 1 & 2





Priyank Kalla

Professor

Electrical & Computer Engineering

From Circuit to Logic and System Design

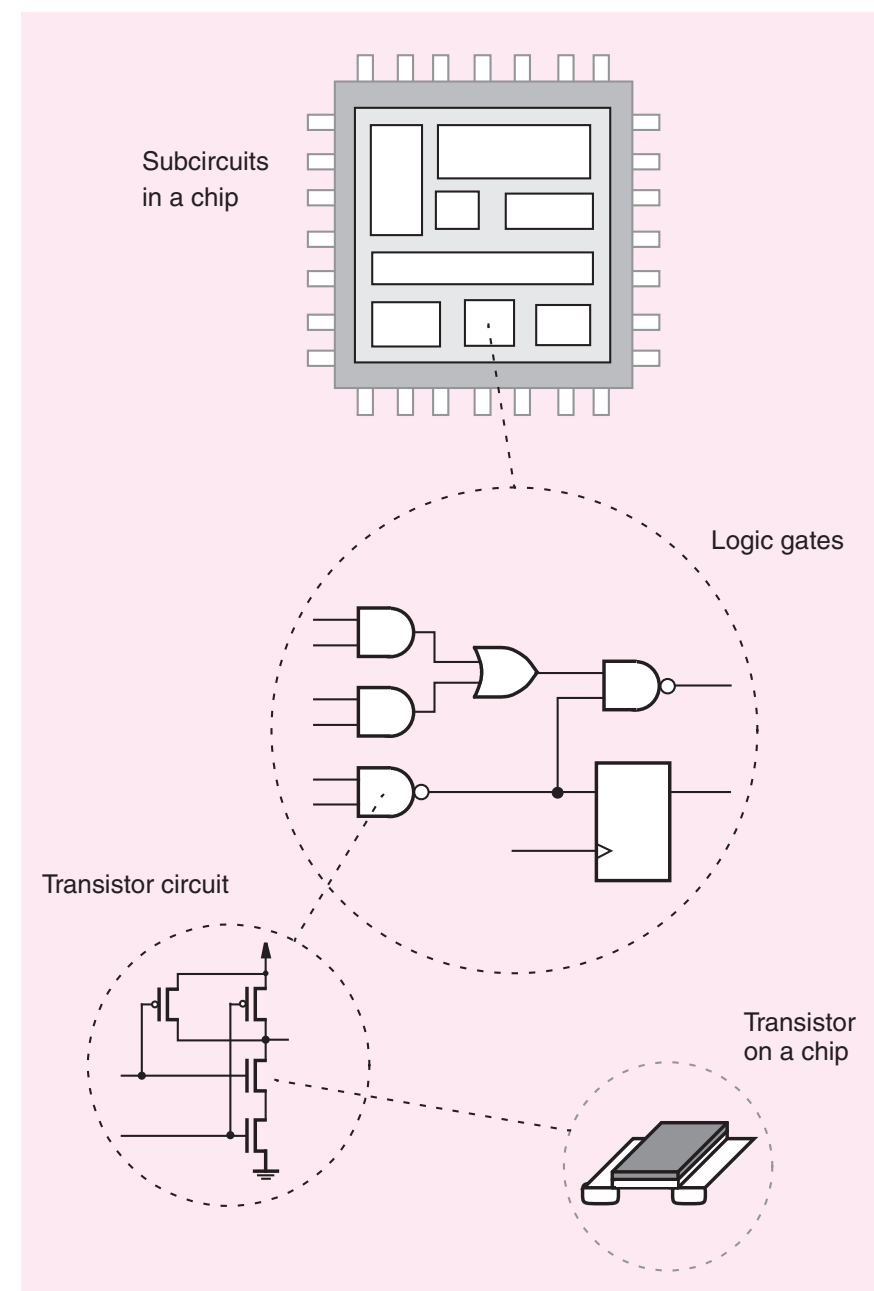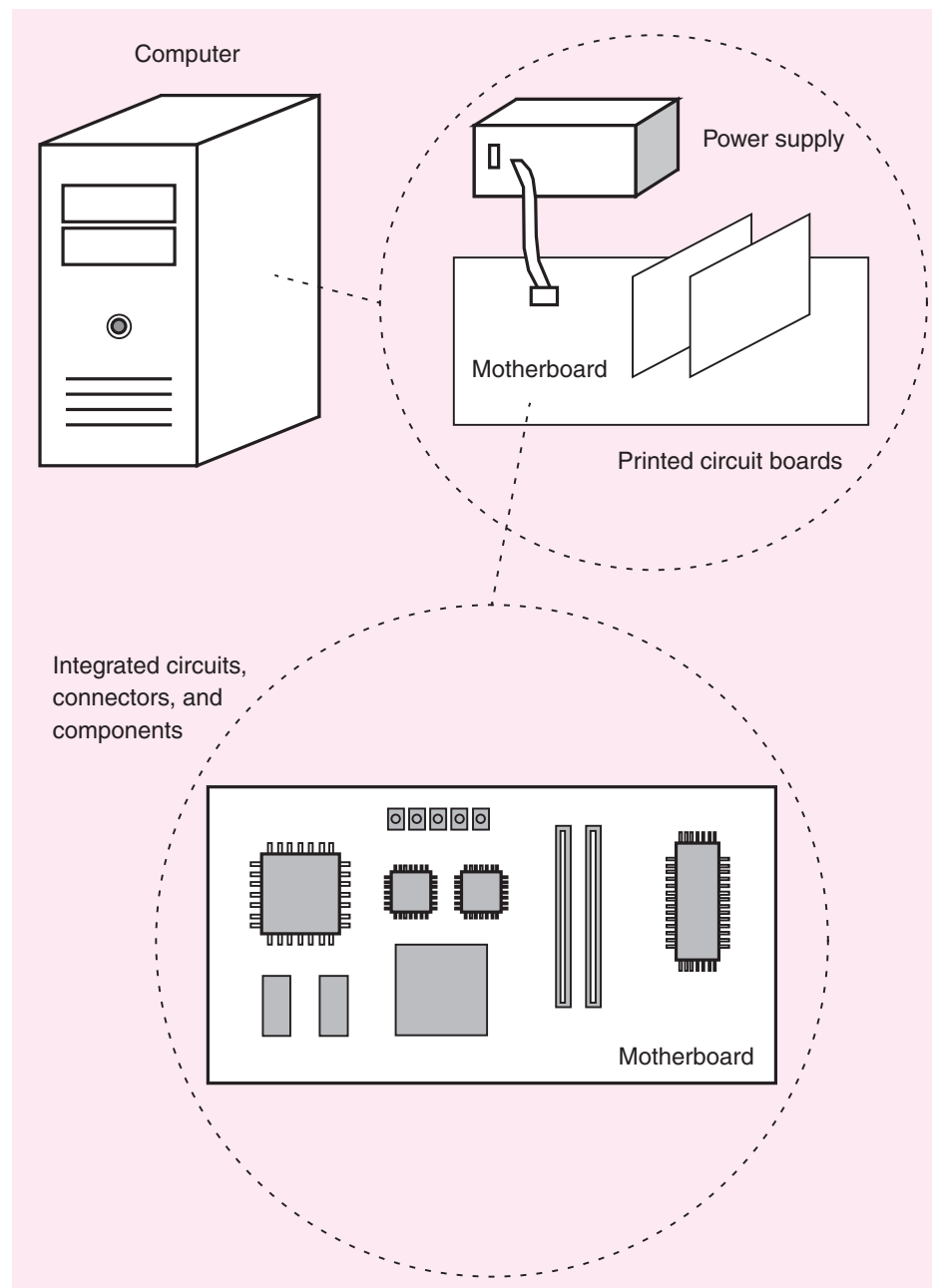

Learn Logic Design Fundamentals, as well as Modern Computer-Aided Design

- Logic Design with Boolean Algebra
- Hardware Description Languages (HDL)
 - We will study Verilog-HDL
 - Other HDLs exist: VHDL, others extensions
- Use of CAD tools


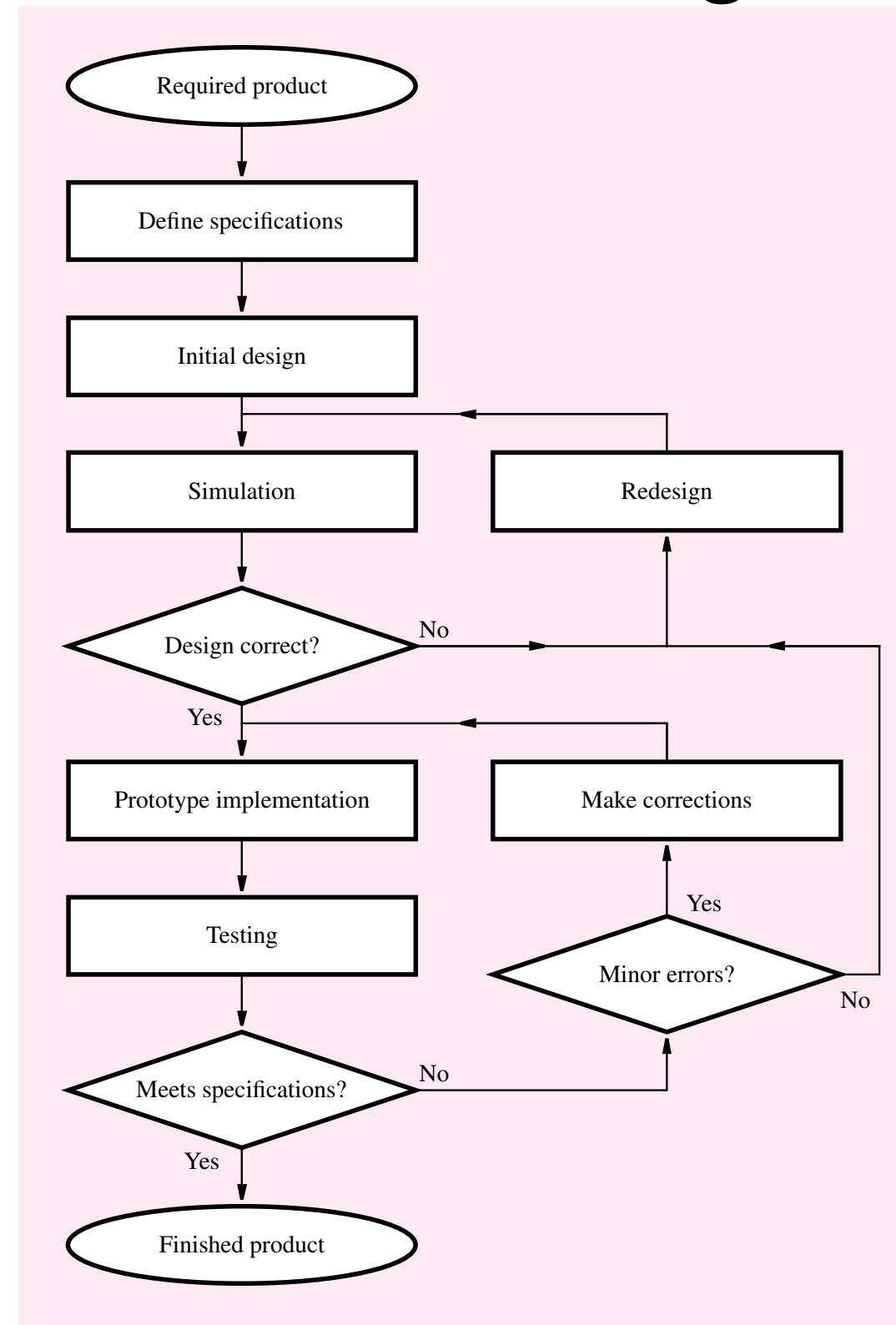


Figure 1.3 The development process.

Field Programmable Gate Array (FPGA)

- Learn how to design logic circuits
- Design in Verilog, Simulate, validate correctness
- Synthesize the circuit and implement on an FPGA
- FPGA = reconfigurable hardware, excellent for prototyping
- 6 or 7 Lab assignments

 


Chapter 2: Intro to Logic Circuits

- Boolean Algebra fundamentals
- Boolean functions and logical operations
- Boolean logic gates and circuits
- Logic Synthesis: Describe Boolean functions in the form of truth tables, and synthesize a logic circuit from it
- Perform logic optimization to reduce “cost of circuit implementation” — area, speed/delay, power, etc.

Boolean Algebra and Functions

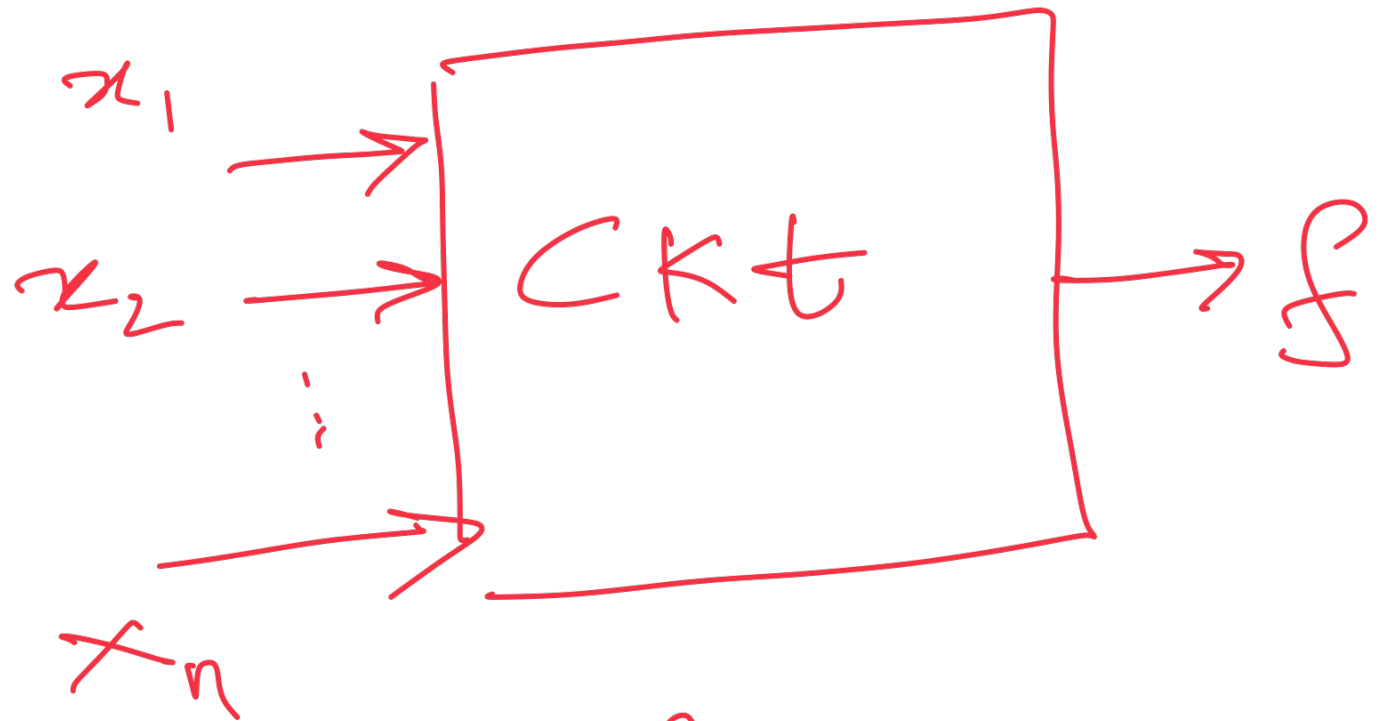- Algebra = set and operations on the elements of the set
- $\mathbb{B} = \{0,1\}$ is the Boolean domain
- Boolean function:
 $\mathbb{B}^n \rightarrow \mathbb{B}$
- Logic circuits implement Boolean functions






$$f: \mathbb{B}^n \rightarrow \mathbb{B}$$

$$f = 0 \text{ or } 1$$

Boolean functions: Truth Tables

   - Simple Boolean functions: AND and OR functions
- Set complement: NOT function
- *AND* : $f = x_1 \cdot x_2 = x_1 \wedge x_2$
- *OR* : $f = x_1 + x_2 = x_1 \vee x_2$
- *NOT*: $f = \neg x_1 = x_1' = \bar{x}_1$



x_1	x_2	$x_1 \cdot x_2$	$x_1 + x_2$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

AND

OR

Boolean functions

- Boolean functions: can have arbitrary inputs

- *AND* : $f = x_1 \cdot x_2 \cdot x_3$

n-inputs = 2ⁿ input possibilities

- *OR*: $f = x_1 + x_2 + x_3$

x_1	x_2	x_3	$x_1 \cdot x_2 \cdot x_3$	$x_1 + x_2 + x_3$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1



 



Figure 2.7 Three-input AND and OR operations.

 

(a) AND gates

 


(b) OR gates

 


(c) NOT gate

Figure 2.8 The basic gates.

 

NAND and NOR Functions

 - We saw AND and OR functions
- Invert them, and you get NAND and NOR functions



x_1	x_2	x_3	And $x_1 \cdot x_2 \cdot x_3$	OR $x_1 + x_2 + x_3$	Nand $x_1 \cdot x_2 \cdot x_3$	NOR $x_1 + x_2 + x_3$
0	0	0	0	0	0	1
0	0	1	0	1	0	0
0	1	0	0	1	0	0
0	1	1	0	1	0	0
1	0	0	0	1	0	0
1	0	1	0	1	0	0
1	1	0	0	1	0	0
1	1	1	1	1	1	0

Figure 2.7 Three-input AND and OR operations.


Exclusive-OR (XOR) and XNOR functions

- XOR and XNOR functions in two variables
- XOR: the function is true when the inputs are mutually exclusive: denoted $f = x_1 \oplus x_2$
- XNOR: $f = \overline{x_1 \oplus x_2} = x_1 \oplus x_2$

x_1	x_2	$x_1 \oplus x_2$	$\overline{x_1 \oplus x_2}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

Boolean Algebra Axioms


 
- ✓ 1a. $0 \cdot 0 = 0$
- 1b. $1 + 1 = 1$
- 2a. $1 \cdot 1 = 1$
- 2b. $0 + 0 = 0$
- ✓ 3a. $0 \cdot 1 = 1 \cdot 0 = 0$
- 3b. $1 + 0 = 0 + 1 = 1$
- 4a. If $x = 0$, then $\bar{x} = 1$
- 4b. If $x = 1$, then $\bar{x} = 0$




$$0 \cdot x = 0$$



$$1 \cdot x = x$$

  

NOT operators

 


$$x \cdot x = x$$

$$x + x = x$$

$$x \cdot \bar{x} = 0$$

$$x + \bar{x} = 1$$

 

"redundancies in
logic design"

Design Problem: Going from a Specification to a circuit implementation

- Design a circuit with three inputs a , b , c and one output f
- Function $f = \text{TRUE}$ when majority of inputs are TRUE , FALSE otherwise
- First job = write a truth table
- Collect the product terms (input product) that evaluates $f = 1$
- SUM (OR) of all these product terms

Truth Table

	a	b	c	f
	0	0	0	0
	0	0	1	0
	0	1	0	0
x	0	1	1	1
	1	0	0	0
x	1	0	1	1
x	1	1	0	1
x	1	1	1	1



$$\bar{a} \cdot b \cdot c$$

+

$$a \cdot \bar{b} \cdot c$$

+

$$a \cdot b \cdot \bar{c}$$


=

f

+

$$a \cdot b \cdot c$$
 
$$f = \bar{a}bc + a\bar{b}c + ab\bar{c} + abc$$



later on: $f = ab + ac + bc$

Boolean Algebra Properties


10a. $x \cdot y = y \cdot x$

10b. $x + y = y + x$


11a. $x \cdot (y \cdot z) = (x \cdot y) \cdot z$

11b. $x + (y + z) = (x + y) + z$

Commutative

 


Associative

 

Boolean Algebra Properties

12a. $x \cdot (y + z) = x \cdot y + x \cdot z$

Distributive

 

Different structure, same function.

Boolean Algebra Properties

13a. $x + x \cdot y = x$

Absorption

$$\underline{x \cdot 1} + x \cdot y = x(1+y) = x \cdot 1 = x$$

13b. $x \cdot (x + y) = x$

$$= x \cdot x + x \cdot y$$

$$= x + xy$$

$$= x$$

DeMorgan's Law

- Break the line and change the sign
- Make the line and change the sign

$$\overline{x+y} = \bar{x} \cdot \bar{y}$$

$$\overline{x \cdot y} = \bar{x} + \bar{y}$$


x	y	$x \cdot y$	$\overline{x \cdot y}$	\bar{x}	\bar{y}	$\bar{x} + \bar{y}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

$\underbrace{\hspace{10em}}_{\text{LHS}} \quad \underbrace{\hspace{10em}}_{\text{RHS}}$

Logic Simplification

- Simplify $(x \cdot y + x \cdot y')$ and $(x + y)(x + y')$

$$x(y + y')$$

 

$$= x \cdot (1)$$

$$= x$$


$$\begin{aligned} & \underline{x \cdot x} + x\bar{y} + xy + y\bar{y} \\ = & x + x\bar{y} + xy + 0 \end{aligned}$$

$$= x(1 + \bar{y} + y)$$

$$= x(1 + \text{anything})$$
$$= x$$


Looking at Algebraic Simplification more Formally

- Consider an n -dimensional Boolean space
- Boolean variable: co-ordinate of the space
- Literal: occurrence of a variable: x or x'
- Minterm: product of all literals, denotes a point in the Boolean space
 - ON-set minterm = minterm where $f = 1$
 - OFF-set minterm = minterm where $f = 0$
- Cube is a product of literals that represents a point or a set of points in the design space
 - Hamming distance: how many bits are changing between any 2 points?

 

Looking at Algebraic Simplification more Formally

x	y	OR
0	0	0
0	1	1
1	0	1
1	1	1

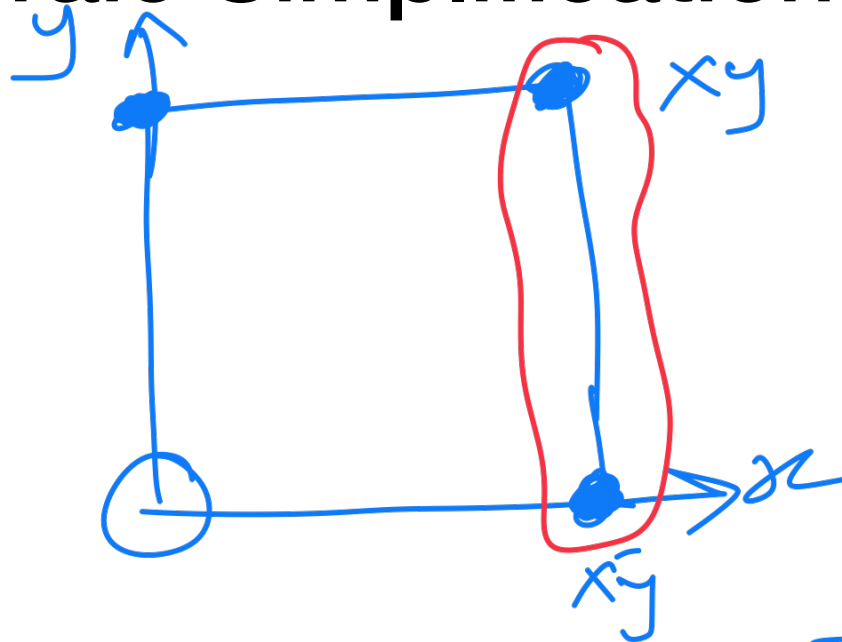

- Consider the OR function


- $f = xy' + x'y + xy \xrightarrow{??} x + y$

• = on-set point

○ = off set "

$$\begin{aligned}
 f &= \underline{\underline{xy'}} + \underline{\underline{x'y}} + \underline{\underline{xy}} \\
 &= \underline{\underline{xy}} + \underline{\underline{x(y+y')}} + \underline{\underline{xy}} \\
 &= \underline{\underline{xy}} + \underline{\underline{x(1)}} + \underline{\underline{xy}} \\
 &= \underline{\underline{y+x}} = \underline{\underline{x+y}}
 \end{aligned}$$

 Looking at Algebraic Simplification more Formally



- Consider the XOR function
- $f = x \oplus y = xy' + x'y$
- No simplification?

$$x\bar{y} + \bar{x}y = \text{no combination nor factorization}$$

Apply DeMorgan's Laws: XOR/XNOR

- Consider the XOR function

- $f = x \oplus y = xy' + x'y$

$$\bar{f} = \overline{xy' + x'y}$$

$$= \overline{xy'} \cdot \overline{x'y}$$

$$= (x' + y)(x + y')$$

- $= x'x + x'y' + xy + yy'$

$$= x'y' + xy = x \oplus y$$

x_1	x_2	$x_1 \oplus x_2$	$x_1 \oplus \overline{x_2}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

"Sum-of-product" form Boolean function.

Product = And gates

Sum = OR-gates

Interesting 3-variable Boolean functions

- 3-variable XOR, Majority Function, Multiplexors
- We've already seen the majority function
- 3-var XOR: $(x \oplus y) \oplus z$



x	y	z	Majority	XOR
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\begin{aligned}
 & \bar{x}(y \oplus z) + \\
 & x(y \oplus \bar{z}) \\
 = & \bar{x} \cdot A + x \cdot \bar{A} \\
 = & x \oplus A \\
 = & x \oplus y \oplus z
 \end{aligned}$$

Simplify the Majority Function

- $f = \underline{a'bc} + ab'c + abc' + abc$


- $= ab + bc + ac$

$= ac(b + \bar{b})$

$+ ab(c + \bar{c})$


$+ bc(a + \bar{a})$

$= ab + ac + bc$

 


Interesting 3-variable Boolean functions

 - Multiplexors = $\text{MUX}(x, y, z) = \bar{x}y + xz$
- When $x=0$, $f = y$
- When $x = 1$, $f = z$



x	y	z	\bar{x}	x	MUX
0	0	0	1	0	0
0	0	1	1	0	0
0	1	0	1	0	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	0	1	1
1	1	0	0	1	0
1	1	1	0	1	1

 

Use of Multiplexors

- MUX: multiplexer, multiplexor = multiple xor
- MUXes are everywhere


$$\text{xor} = \bar{x}y + x\bar{y}$$

$$\text{mux} \quad \bar{x}y + xz$$

$$x=0 \quad f = A+B$$



$$x=1 \quad f = A-B$$

Mux = if-then-else

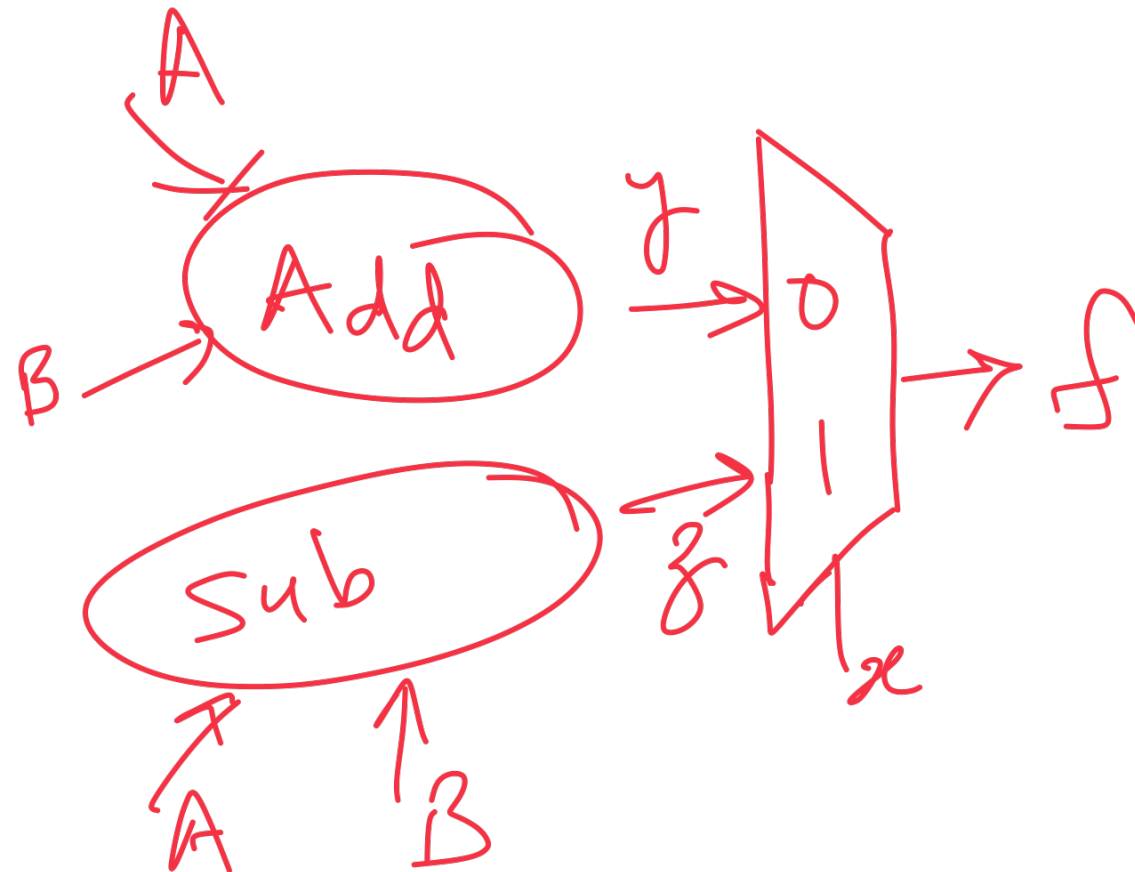


Use of Multiplexors

  - One-bit control, 2 data inputs
- 2-bit control, 4 data inputs
- N-bit control, 2^N data inputs



Logic Optimization: One more example

 

$$f = \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + \bar{a}b\bar{c} + \bar{a}bc + abc$$

$$= ac + \bar{b}c + \bar{b}\bar{c}$$





$$= ac + \bar{b}$$

Sum of Product (SOP) form of Boolean functions

- $F(x_1, \dots, x_n) =$ sum of ON-set minterms
- Simplify ON-set minterms into “larger cubes”: combine minterms that are one hamming distance apart, and keep on combining them as much as possible
 - Algebraically: factorize and simplify
- Identify a minimum number of largest cubes that cover all the ON-set minterms. [Often called a “minimum cover” of F]
- “Smallest” cover exists, find it!
- Larger cubes = smaller AND gates = fewer transistors = fewer literals
- Minimum number of cubes = smallest OR gate
- Smaller area, faster circuit (less RC to charge/discharge)
- **SOP form = two-level logic:** one-level of AND gates, and one-level of (possibly big!) OR-gate. [Ignore the level corresponding to inverters]

Simplify the Majority Function

   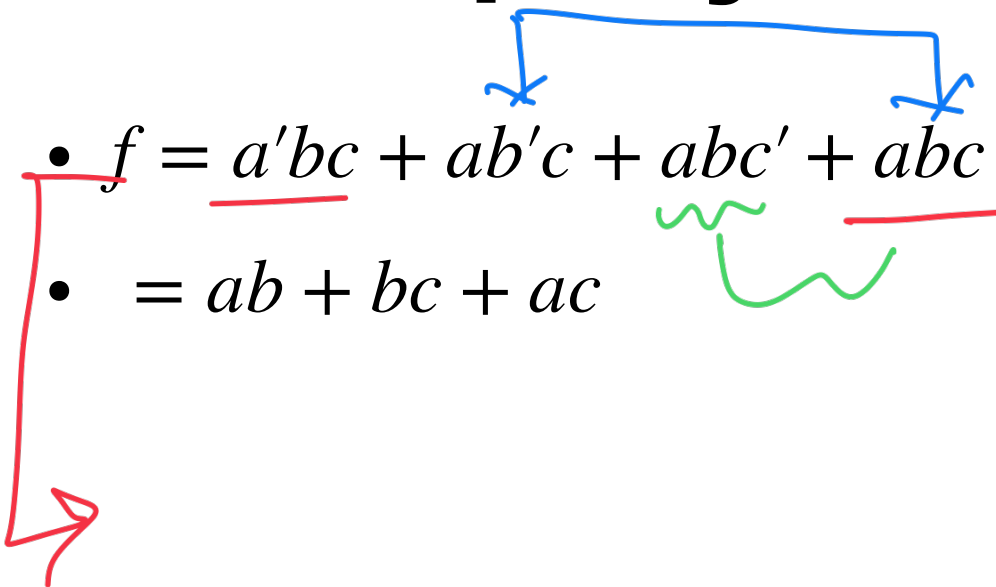- $f = \underline{a'bc} + ab'c + abc' + \underline{abc}$
- $= ab + bc + ac$



SOP-form, contd.

- Given $F(x_1, x_2, x_3, \dots)$, with variable order $x_1, x_2, x_3 \dots$

- F can be specified as a sum of ON-set minterms

- E.g., majority function:



- $$F(x_1, x_2, x_3) = \sum (m_3, m_5, m_6, m_7)$$

Row number	x_1	x_2	x_3	Minterm
0	0	0	0	$m_0 = \bar{x}_1 \bar{x}_2 \bar{x}_3$
1	0	0	1	$m_1 = \bar{x}_1 \bar{x}_2 x_3$
2	0	1	0	$m_2 = \bar{x}_1 x_2 \bar{x}_3$
3	0	1	1	$m_3 = \bar{x}_1 x_2 x_3$
4	1	0	0	$m_4 = x_1 \bar{x}_2 \bar{x}_3$
5	1	0	1	$m_5 = x_1 \bar{x}_2 x_3$
6	1	1	0	$m_6 = x_1 x_2 \bar{x}_3$
7	1	1	1	$m_7 = x_1 x_2 x_3$

- Self-study assignment for you: Sec 2.6.1, product of sum forms, and Maxterms

Two-level logic versus multi-level logic

- $f = ab + ac + bc = \text{SOP form} = \text{2-level}$
 - Objective: minimum number of largest cubes = minimum cover
- Factorize: $f = ab + c(a+b) = \text{factored form} \neq \text{SOP form}$
 - Multi-level logic: minimize the number of “literals”
- Some technologies are suitable for 2-level logic (such as PLAs), whereas others are suitable for multi-level logic (contemporary CMOS technologies)
 - We'll study this a little later, in appendix B, in the textbook!
- Multi-level logic optimization often utilizes 2-level optimization techniques, so study of 2-level SOP form minimization is a must!

  

With more variables, Logic simplification becomes infeasible using algebraic/symbolic manipulation. We need algorithmic techniques, which we'll study a bit later...

 


Figure 8.18 Representation of function f_3 from Figure 2.54

A 4-dimensional cube