

Combinational Circuit Verification using Strong Nullstellensatz

Overcoming the Complexity of Gröbner Bases for Efficient Verification,
and Verification of Integer Multipliers

Priyank Kalla



Associate Professor
Electrical and Computer Engineering, University of Utah
kalla@ece.utah.edu
<http://www.ece.utah.edu/~kalla>

Nov 22, 2021 - onwards

What we have learnt so far...

Theorem (Weak Nullstellensatz)

Let $\overline{\mathbb{F}}$ be an algebraically closed field. Given ideal $J \subset \overline{\mathbb{F}}[x_1, \dots, x_n]$, $V_{\overline{\mathbb{F}}}(J) = \emptyset \iff J = \overline{\mathbb{F}}[x_1, \dots, x_n] \iff 1 \in J \iff \text{reducedGB}(J) = \{1\}$.

Theorem (The Strong Nullstellensatz)

Over an algebraically closed field $I(V(J)) = \sqrt{J}$

Verification using Nullstellensatz over \mathbb{F}_q

We have two approaches to verify circuits using the Nullstellensatz

- Verify circuits using the miter model
- Construct a miter, and apply the **Weak Nullstellensatz**
- Construct ideal $J_m = \langle f_{spec}, f_1, \dots, f_s, f_m \rangle$
- Polynomials f_1, \dots, f_s are the polynomials from the circuit
- $J_0 =$ ideal of all vanishing polynomials
- Circuit \equiv Spec if and only if $GB(J_m + J_0) = \{1\}$.

 


Figure: The equivalence checking setup: miter.

Second Approach to Verification: Strong Nullstellensatz

- The **second** approach is based on Ideal Membership in $I(V(J))$
- Given a spec polynomial f_{spec} and an implementation circuit C
- Derive ideal $J = \langle f_1, \dots, f_s \rangle$, where $\{f_1, \dots, f_s\}$ are polynomials from the given circuit C
- It is **NOT** sufficient to check if $f_{spec} \in J$.
- It is **necessary and sufficient** to check if $f_{spec} \in J + J_0$, where $J_0 =$ ideal of all vanishing polynomials.
- Why? Because f_{spec} may vanish on the variety $V_{\mathbb{F}_q}(J)$
- So, $f \in I(V_{\mathbb{F}_q}(J))$. Remember $I(V(J))$?

$I(V)$

Let $J = \langle f_1, \dots, f_s \rangle \subset \mathbb{F}[x_1, \dots, x_n]$. Then:

$$I(V(J)) = \{f \in \mathbb{F}[x_1, \dots, x_n] : f(\mathbf{a}) = 0 \forall \mathbf{a} \in V(J)\}$$

- $I(V(J))$ is the set of all polynomials that vanish on $V(J)$
- If f vanishes on $V(J)$, then $f \in I(V(J))$

Nullstellensatz over \mathbb{F}_q

Theorem (Weak Nullstellensatz over \mathbb{F}_{2^k})

Let ideal $J = \langle f_1, \dots, f_s \rangle \subset \mathbb{F}_{2^k}[x_1, \dots, x_n]$ be an ideal. Let $J_0 = \langle x_1^{2^k} - x_1, \dots, x_n^{2^k} - x_n \rangle$ be the ideal of all vanishing polynomials. Then:

$$V_{\mathbb{F}_{2^k}}(J) = \emptyset \iff V_{\mathbb{F}_{2^k}}(J + J_0) = \emptyset \iff \text{reducedGB}(J + J_0) = \{1\}$$

Theorem ($J + J_0$ is radical)

Over Galois fields $\sqrt{J + J_0} = J + J_0$, i.e. $J + J_0$ is a radical ideal.

Theorem (Strong Nullstellensatz over \mathbb{F}_q)

$$I(V_{\mathbb{F}_q}(J)) = I(V_{\mathbb{F}_q}(J + J_0)) = \sqrt{J + J_0} = J + J_0$$


Verification Formulation: The Mathematical Problem

- Given **specification polynomial**: $f : Z = A \cdot B \pmod{P(x)}$ over \mathbb{F}_{2^k} , for given k , and given $P(x)$, s.t. $P(\alpha) = 0$
- Given **circuit implementation** C
 - Primary inputs: $A = \{a_0, \dots, a_{k-1}\}, B = \{b_0, \dots, b_{k-1}\}$
 - Primary Output $Z = \{z_0, \dots, z_{k-1}\}$
 - $A = a_0 + a_1\alpha + a_2\alpha^2 + \dots + a_{k-1}\alpha^{k-1}$
 - $B = b_0 + b_1\alpha + \dots + b_{k-1}\alpha^{k-1}, Z = z_0 + z_1\alpha + \dots + z_{k-1}\alpha^{k-1}$
- Does the circuit C implement f ?

Mathematically:

- Model the circuit (gates) as polynomials: f_1, \dots, f_s
 $J = \langle f_1, \dots, f_s \rangle \subset \mathbb{F}_{2^k}[x_1, \dots, x_n]$
- Does f agree with solutions to $f_1 = f_2 = \dots = f_s = 0$?
- Does f **vanish** on the **Variety** $V_{\mathbb{F}_q}(J)$?
- Is $f \in I(V_{\mathbb{F}_q}(J)) = J + J_0$ or is $f \xrightarrow{GB(J+J_0)}_+ 0$?

Example Formulation

 

Gates as polynomials

$\mathbb{F}_2 \subset \mathbb{F}_{2^k}$:

Ideal J :

$$z_0 = s_0 + s_3; \mapsto f_1 : z_0 + s_0 + s_3$$

$$s_0 = a_0 \cdot b_0; \mapsto f_2 : s_0 + a_0 \cdot b_0$$

\vdots

$$A + a_0 + a_1\alpha; B + b_0 + b_1\alpha; Z + z_0 + z_1\alpha$$

Ideal J_0 :

$$z_0^2 - z_0, s_0^2 - s_0,$$

\vdots

$$A^{2^k} - A, B^{2^k} - B, \\ Z^{2^k} - Z$$

Complexity of Gröbner Basis

- Complexity of Gröbner basis
 - Degree of polynomials in G is bounded by $2(\frac{1}{2}d^2 + d)^{2^{n-1}}$ [1]
 - Doubly-exponential in n and polynomial in the degree d
- This is the complexity of the GB problem, not of Buchberger's algorithm – that's still a mystery
- For $J \subset \mathbb{F}_q[x_1, \dots, x_n]$, Complexity $GB(J + J_0) : q^{O(n)}$ (Single exponential)
- Improving Buchberger's algorithm:
 - Improve term ordering (heuristics)
 - Get to all $S(f, g) \xrightarrow{G} 0$ quickly; i.e. arrive at a GB quickly (hard to predict)
 - Improve the implementation of polynomial division; ideas proposed by *Faugère* in the F_4 algorithm

Complexity of Gröbner Basis and Term Orderings

- For $J \subset \mathbb{F}_q[x_1, \dots, x_n]$, Complexity $GB(J + J_0) : q^{O(n)}$
- GB complexity very sensitive to **term ordering**
- A term order has to be imposed for systematic polynomial computation

Let $f = 2x^2yz + 3xy^3 - 2x^3$

- LEX $x > y > z$: $f = -2x^3 + 2x^2yz + 3xy^3$
- DEGLEX $x > y > z$: $f = 2x^2yz + 3xy^3 - 2x^3$
- DEGREVLEX $x > y > z$: $f = 3xy^3 + 2x^2yz - 2x^3$

Recall, S-polynomial depends on term ordering:

$$S(f, g) = \frac{L}{lt(f)} \cdot f - \frac{L}{lt(g)} \cdot g; \quad L = \text{LCM}(lm(f), lm(g))$$

The Product Criteria

If $lm(f) \cdot lm(g) = LCM(lm(f), lm(g))$, then $S(f, g) \xrightarrow{G'}_+ 0$.

LEX: $x_0 > x_1 > x_2 > x_3$

- $f = x_0x_1 + x_2$, $g = x_1x_2 + x_3$
- $lm(f) = x_0x_1$; $lm(g) = x_1x_2$
- $S(f, g) \xrightarrow{G'}_+ x_0x_3 + x_2^2$

LEX: $x_3 > x_2 > x_1 > x_0$

- $f = x_2 + x_0x_1$, $g = x_3 + x_1x_2$
- $lm(f) = x_2$; $lm(g) = x_3$, $S(f, g) \xrightarrow{G'}_+ 0$

“Obviate” Buchberger's algorithm... really?


Find a “term order” that makes ALL $\{lm(f), lm(g)\}$ relatively prime.

Recall Buchberger's theorem

The set $G = \{g_1, \dots, g_t\}$ is a Gröbner basis **iff** for all pairs $(f, g) \in G$, $S(f, g) \xrightarrow{G}_+ 0$

- If we can make leading monomials of all pairs $lm(f), lm(g)$ relatively prime, then all $Spoly(f, g)$ reduce to 0
- This would imply that the polynomials already constitute a Gröbner basis
- No need to compute a GB, **may be able to circumvent** the GB complexity issues
- Can a term order be derived that makes leading monomials of all polynomials relatively prime?
 - For an “acyclic” circuit, make the gate output variable x_i greater than all variables x_j that are inputs to the gate

 For Circuits, such an order can be derived



$$\begin{array}{lll}
 f_1 : s_0 + a_0 \cdot b_0; & f_2 : s_1 + a_0 \cdot b_1; & f_3 : s_2 + a_1 \cdot b_0; \\
 f_4 : s_3 + a_1 \cdot b_1; & f_5 : r_0 + s_1 + s_2; & f_6 : z_0 + s_0 + s_3 \\
 f_7 : z_1 + r_0 + s_3; & f_8 : A + a_0 + a_1\alpha; & f_9 : B + b_0 + b_1\alpha \\
 & f_{10} : Z + z_0 + z_1\alpha; &
 \end{array}$$

- Perform a Reverse Topological Traversal of the circuit, order the variables according to their reverse topological levels
- LEX with $Z > \{A > B\} > \{z_0 > z_1\} > \{r_0 > s_0 > s_3\} > \{s_1 > s_2\} > \{a_0 > a_1 > b_0 > b_1\}$
- This makes every gate output a leading term, and $\{f_1, \dots, f_{10}\}$ is a Gröbner basis

Using the Topological Term Order:

- $F = \{f_1, \dots, f_s\}$ is a Gröbner Basis of $J = \langle f_1, \dots, f_s \rangle$
- $F_0 = \{x_1^q - x_1, \dots, x_n^q - x_n\}$ is also a Gröbner basis of J_0 (these polynomials also have relatively prime leading terms)
- But we have to compute a Gröbner Basis of $J + J_0 = \langle f_1, f_2, \dots, f_s, x_1^q - x_1, \dots, x_n^q - x_n \rangle$
- It turns out that $\{f_1, f_2, \dots, f_s, x_1^q - x_1, \dots, x_n^q - x_n\}$ is a Gröbner basis!!
- From our circuit: $f_i = x_i + \text{tail}(f_i) = x_i + P$
- Vanishing polynomials $x_i^q - x_i$ with same variable x_i
- Only pairs to consider: $S(f_i, x_i^q - x_i)$ in Buchberger's Algorithm
- All other pairs will have relatively prime leading terms, which will reduce to 0 modulo G

This term order renders a Gröbner basis by construction

So, let us compute $S(f_i = x_i + P, x_i^q - x_i)$:

$$S(f_i = x_i + P, x_i^q - x_i) = x_i^{q-1}P + x_i$$

$$x_i^{q-1}P + x_i \xrightarrow{x_i+P} x_i^{q-2}P^2 + x_i \xrightarrow{x_i+P} \dots \xrightarrow{x_i+P} P^q - P \xrightarrow{J_0} + 0$$

Since $P^q - P$ is a vanishing polynomial, $P^q - P \in J_0$ and $P^q - P \xrightarrow{J_0} + 0$

Conclusion: The set of polynomials

$F \cup F_0 = \{f_1, \dots, f_s, x_i^q - x_i, \dots, x_n^q - x_n\}$ is itself a Gröbner basis due to the reverse topological term order derived from the circuit!

Our Minimal Gröbner Basis

Conclusion:

- Our term order makes $G = \{f_1, \dots, f_s, x_1^q - x_1, \dots, x_n^q - x_n\}$ a Gröbner Basis
- This $GB(J + J_0)$ can be further simplified (made minimal)
 - Two types of polynomials: $f_i = x_i + P$, $g_i = x_i^q - x_i$
 - Primary inputs bits are never a leading term of any polynomial
 - Primary inputs are not the output of any gate
- For $x_i \notin$ primary inputs, $f_i = x_i + P$ divides $x_i^q - x_i$; remove $x_i^q - x_i$
- Keep $J_0 = \langle x_i^2 - x_i : x_i \in \text{primary input bits} \rangle$

Our term order makes $G = \{f_1, \dots, f_s, x_{PI}^2 - x_{PI}\}$ a **minimal** Gröbner basis **by construction!**

Verify the circuit only by a reduction: $f \xrightarrow{G}_+ 0?$

Our Overall Approach

- Given the circuit, perform reverse topological traversal
- Derive the term order to represent the polynomials for every gate, call it the Reverse Topological Term Order (RTTO) $>$
- The set: $\{F, F_0\} = \{f_1, \dots, f_s, x_i^2 - x_i : x_i \in X_{PI}\}$ is a minimal Gröbner Basis
- Obtain: $f \xrightarrow{F, F_0} r$
- If $r = 0$, the circuit is verified correct
- If $r \neq 0$, then r contains only the **primary input variables**
- Any SAT assignment to $r \neq 0$ generates a counter-example
- Counter-example found in no time as r is simplified by Gröbner basis reduction

Move the complexity to that of Polynomial Division

Is this Magic? Or have I told you the full story?

- Reduce x^n modulo $\langle x + P \rangle$, how many cancellations?
 - Requires raising P to the n^{th} power
 - P is the $\text{tail}(f_i)$
 - Depending upon n , this can become complicated
- **Reduce** this **minimal** GB $G = \{F, F_0\}$, what does it look like?
 - $f_i = x_i + \text{tail}(f_i)$, where $\text{tail}(f_i) = P(x_j)$, $x_i > x_j$
 - There exists $f_j = x_j + \text{tail}(f_j)$, where $f_j \mid P(x_j)$
 - All non-PI variables x_j can be canceled in this reduction
 - Reduction results in GB G with only primary input variables, potentially explosive

This approach should work for specification polynomials f with low degree terms

Experiments: Correctness Proof, Miter Mastrovito v/s Montgomery Multipliers

Table: Verification Results of SAT, SMT, BDD, ABC.

	Word size of the operands k -bits		
Solver	8	12	16
MiniSAT	22.55	<i>TO</i>	<i>TO</i>
CryptoMiniSAT	7.17	16082.40	<i>TO</i>
PrecoSAT	7.94	<i>TO</i>	<i>TO</i>
PicoSAT	14.85	<i>TO</i>	<i>TO</i>
Yices	10.48	<i>TO</i>	<i>TO</i>
Beaver	6.31	<i>TO</i>	<i>TO</i>
CVC	<i>TO</i>	<i>TO</i>	<i>TO</i>
Z3	85.46	<i>TO</i>	<i>TO</i>
Boolector	5.03	<i>TO</i>	<i>TO</i>
SimplifyingSTP	14.66	<i>TO</i>	<i>TO</i>
ABC	242.78	<i>TO</i>	<i>TO</i>
BDD	0.10	14.14	1899.69

Experimental Results: Correctness Proof


Verify a specification polynomial f against a circuit C by performing the test $f \xrightarrow{J+J_0} 0?$

Table: Verify bug-free and buggy Mastrovito multipliers. SINGULAR computer algebra tool used for division.

Size k -bits	32	64	96	128	160	163
#variables	1155	4355	9603	16899	26243	27224
#polynomials	1091	4227	9411	16643	25923	26989
#terms	7169	28673	64513	114689	179201	185984
Compute-GB:	93.80	<i>MO</i>	<i>MO</i>	<i>MO</i>	<i>MO</i>	<i>MO</i>
Ours: Bug-free	1.41	112.13	758.82	3054	9361	16170
Ours: Bugs	1.43	114.86	788.65	3061	9384	16368

Why does Compute-GB (SINGULAR) run out of memory?

Limitations of RTTO-based GB-reduction

 


For XOR logic:

$$f_1 : z + f + d \quad f_2 : f + e + c \quad f_3 : e + b + a$$


The reduction procedure $z \xrightarrow{f_1, f_2, f_3} r$ will be computed as follows:

- $z \xrightarrow{z+f+d} f + d$
- $(f + d) \xrightarrow{f+e+c} e + d + c$
- $(e + d + c) \xrightarrow{e+b+a} d + c + b + a$

 Limitations of GB-Reduction: OR-gates explode



(c) XOR logic

 

(d) OR logic

For OR logic:

$$f_1 : z + fd + f + d \quad f_2 : f + ec + e + c \quad f_3 : e + ba + b + a$$

The reduction procedure, $z \xrightarrow{f_1, f_2, f_3} r$ is now computed as:

- $z \xrightarrow{z+fd+f+d} fd + f + d$
- $(fd + f + d) \xrightarrow{f+ec+e+c} f + edc + ed + dc + d;$
 $(f + edc + ed + dc + d) \xrightarrow{f+ec+e+c} edc + ed + ec + e + dc + d + c$
- $(edc + ed + ec + e + dc + d + c) \xrightarrow{e+ba+b+a} r$
 $dcba + dc + db + da + d + cba + cb + ca + c + ba + b + a$

Verification of Integer Multipliers

- Use the same ideal membership approach to verify integer multipliers
- Consider a 2-bit (integer multiplier) circuit. Prove that it is an integer multiplier! Or prove that it is buggy.

 


Figure: Integer multiplier circuit

Integer Arithmetic Verification Model

- What is the spec?
- Output word: $z_0 + 2z_1 + 4z_2 + 8z_3$, z_i are bits $\{0, 1\}$
- Input words: $a_0 + 2a_1$, $b_0 + 2b_1$.
- $f_{spec} : z_0 + 2z_1 + 4z_2 + 8z_3 = (a_0 + 2a_1)(b_0 + 2b_1)$
- In polynomial form: $f_{spec} : z_0 + 2z_1 + 4z_2 + 8z_3 - (a_0 + 2a_1)(b_0 + 2b_1)$
- Note f_{spec} has coefficients in \mathbb{Z} , but \mathbb{Z} is NOT a field, so we cannot apply Nullstellensatz!
- Trick: Model the problem over $\mathbb{Q}[x_1, \dots, x_n]$, BUT, use the same RTTO order (important)
- How to model Boolean logic gates over \mathbb{Q} ?

Model Logic Gates over \mathbb{Q}

$$z = \neg a \mapsto z = 1 - a \mapsto z - 1 + a$$

$$z = a \wedge b \mapsto z = a \cdot b \mapsto z - a \cdot b$$

$$z = a \vee b \mapsto z = a + b - a \cdot b \mapsto z - a - b + ab$$

$$z = a \oplus b \mapsto z = a + b - 2 \cdot a \cdot b \mapsto z - a - b + 2ab$$

- This requires that every variable take **binary** values: $a^2 = a$ or $J_0 = \langle a^2 - a, b^2 - b, \dots, z^2 - z \rangle$
- Construct ideal J from logic gates, add bit-level vanishing polynomials J_0
- What is the leading term of polynomials in J under RTTO?
- Gate output is the leading term, and leading coefficient = 1
- Divide by $lc(f) = 1$, division will NEVER produce fractions!

Verification $f_{spec} \pmod{J + J_0}$ under RTTO

$$\begin{aligned}
 Z &= 8z_3 + 4z_2 + 2z_1 + z_0 \\
 &= \underline{8x_1x_2x_3} + (4x_1 + \underbrace{4x_2x_3 - 8x_1x_2x_3}) \\
 &\quad + (2x_2 + 2x_3 - \underbrace{4x_2x_3}) + x_4 \\
 &= 4x_1 + 2x_2 + 2x_3 + x_4
 \end{aligned}$$

 


Figure: Integer multiplier circuit

- Ring $R = 0, (z_3, z_2, z_1, z_0, x_5, x_1, x_2, x_3, x_4, a_0, a_1, b_0, b_1), lp;$
- Circuit is an integer multiplier if $f_{spec} \xrightarrow{J+J_0} + 0$.

The Key to Success in Design Automation

- Build algorithms and techniques on solid theoretical foundations
- Use all of the mathematical tools at your disposal
- Make sure to exploit circuit structure
- Develop domain-specific implementations
- That's what SAT, BDDs, AIGs do too!



T. W. Dube, “The Structure of Polynomial Ideals and Gröbner bases,”
SIAM Journal of Computing, vol. 19, no. 4, pp. 750–773, 1990.